
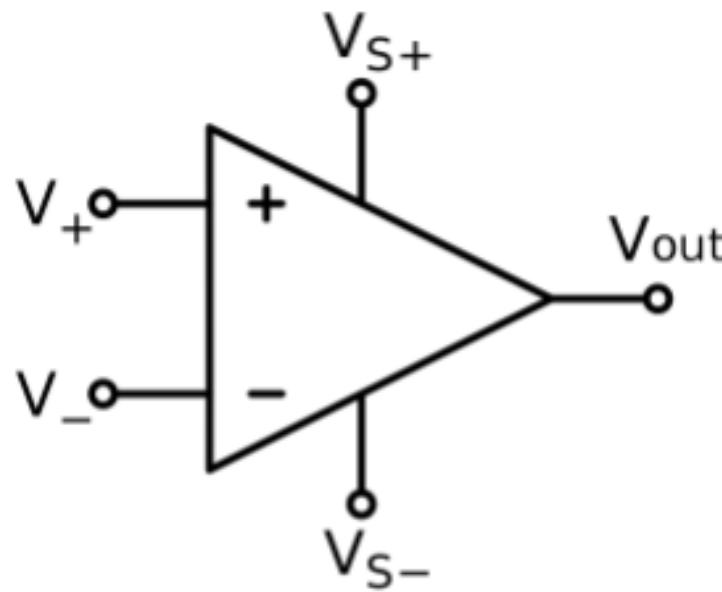


# Introduction to op-amps

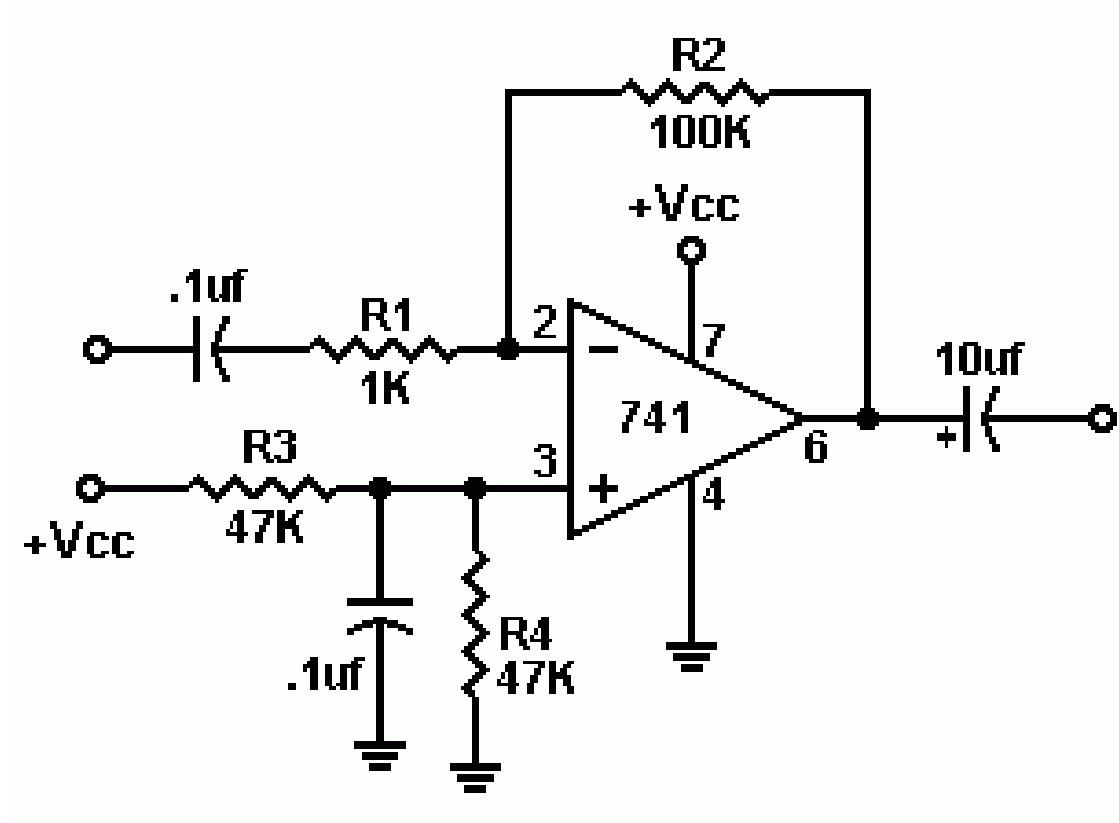


# Uses of op-amps

- Amplifiers




# Uses of op-amps




- Amplifiers
- **Buffers**

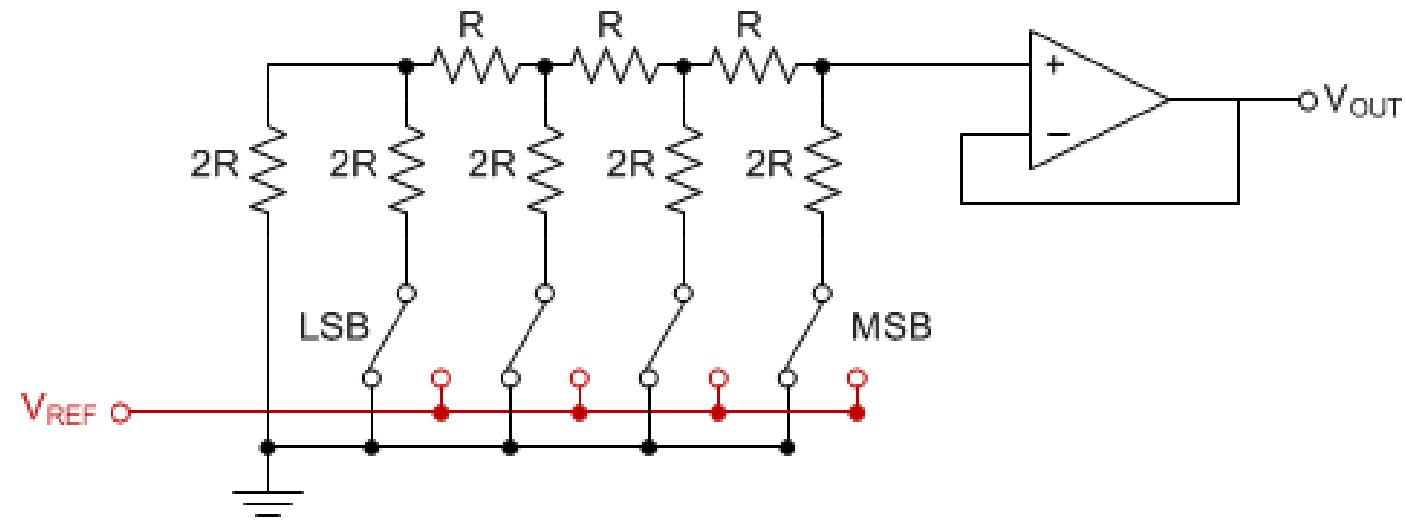


# Uses of op-amps

- Amplifiers
- Buffers
- Filters

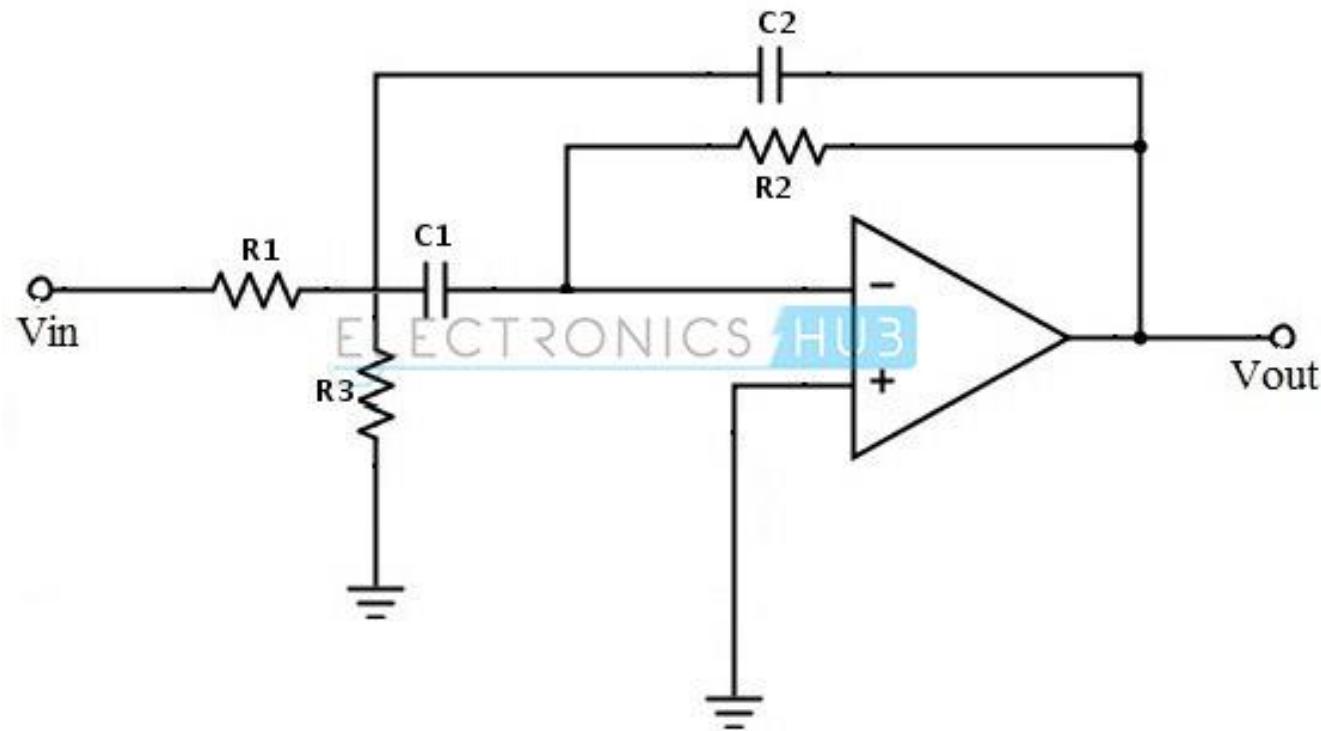


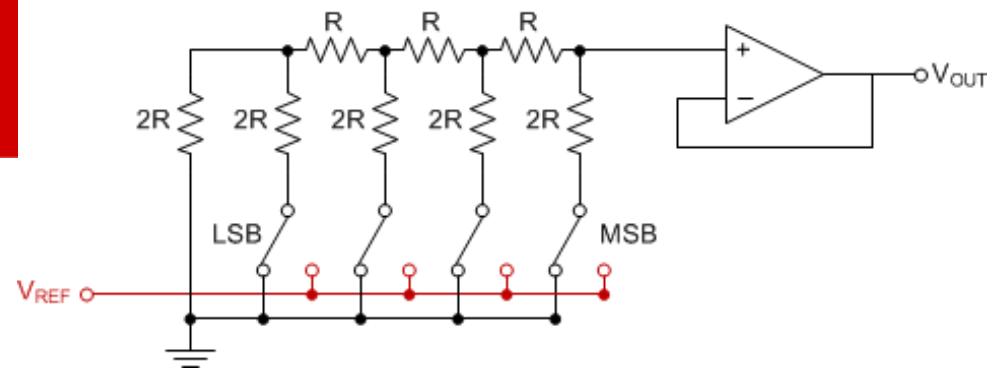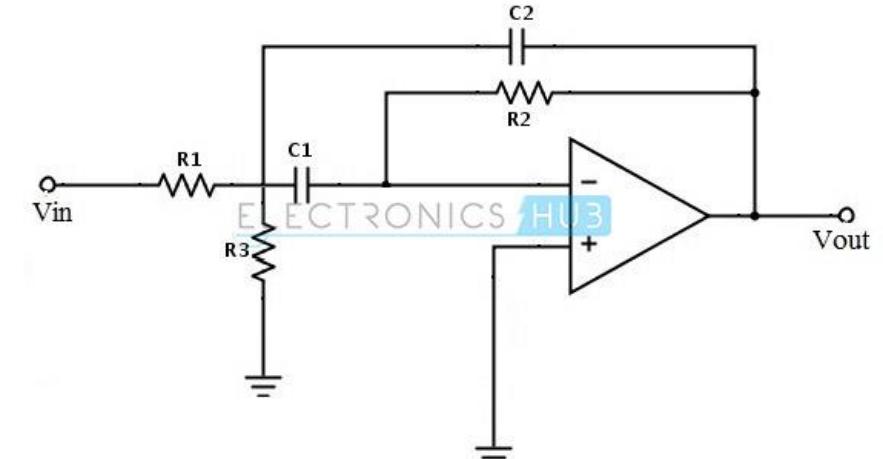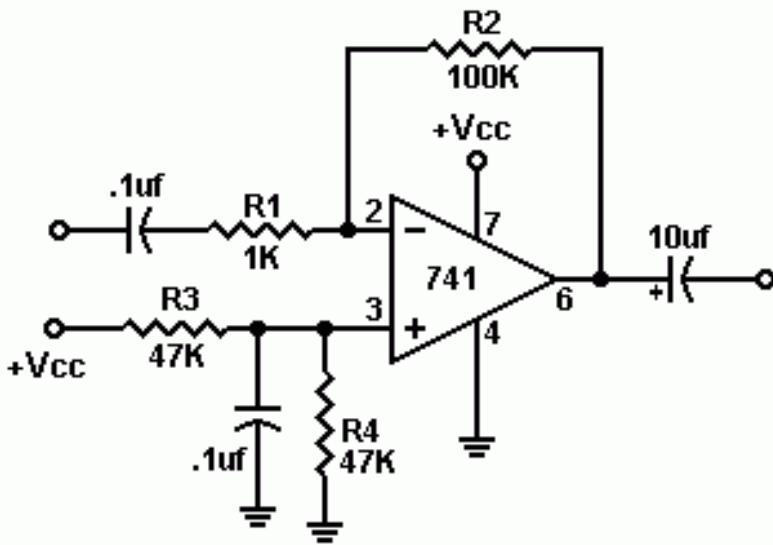


Quick review: What is  $V_A$ ?

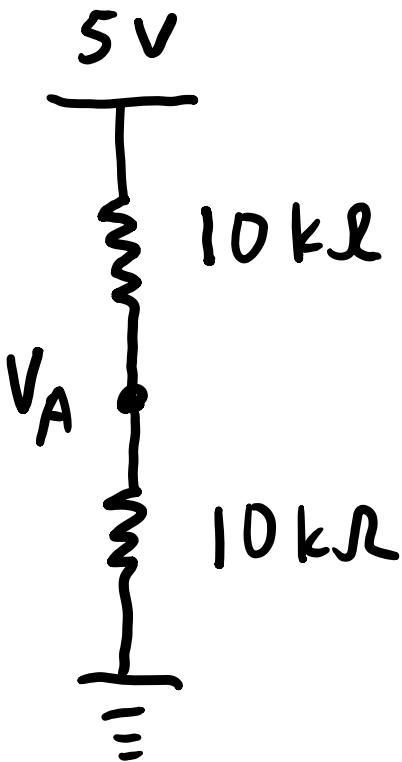



Now what is  $V_A$ ?

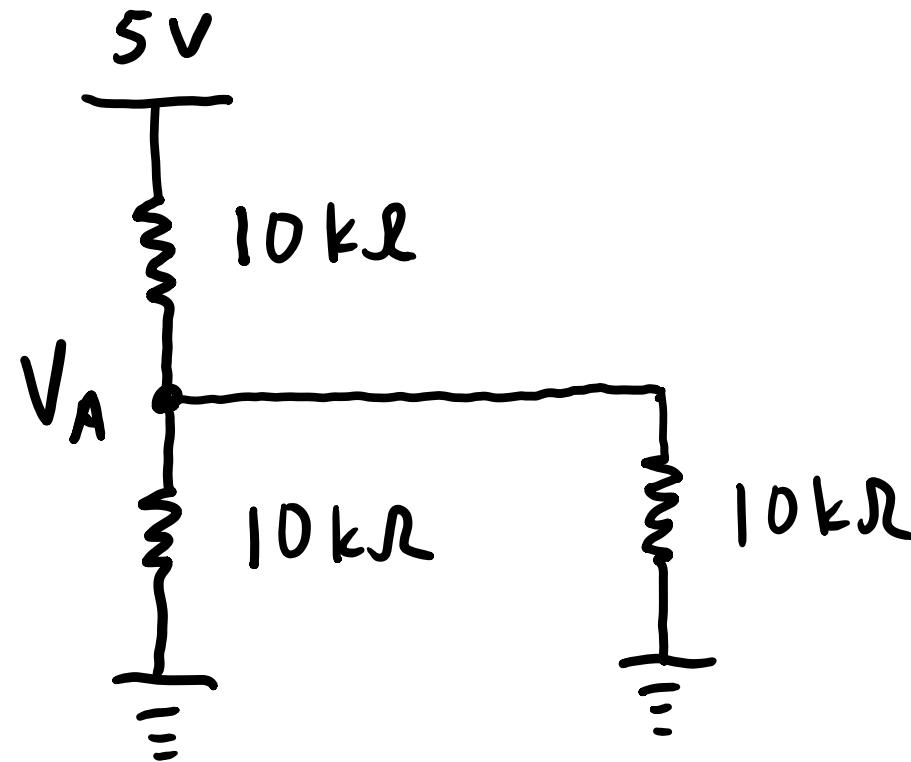

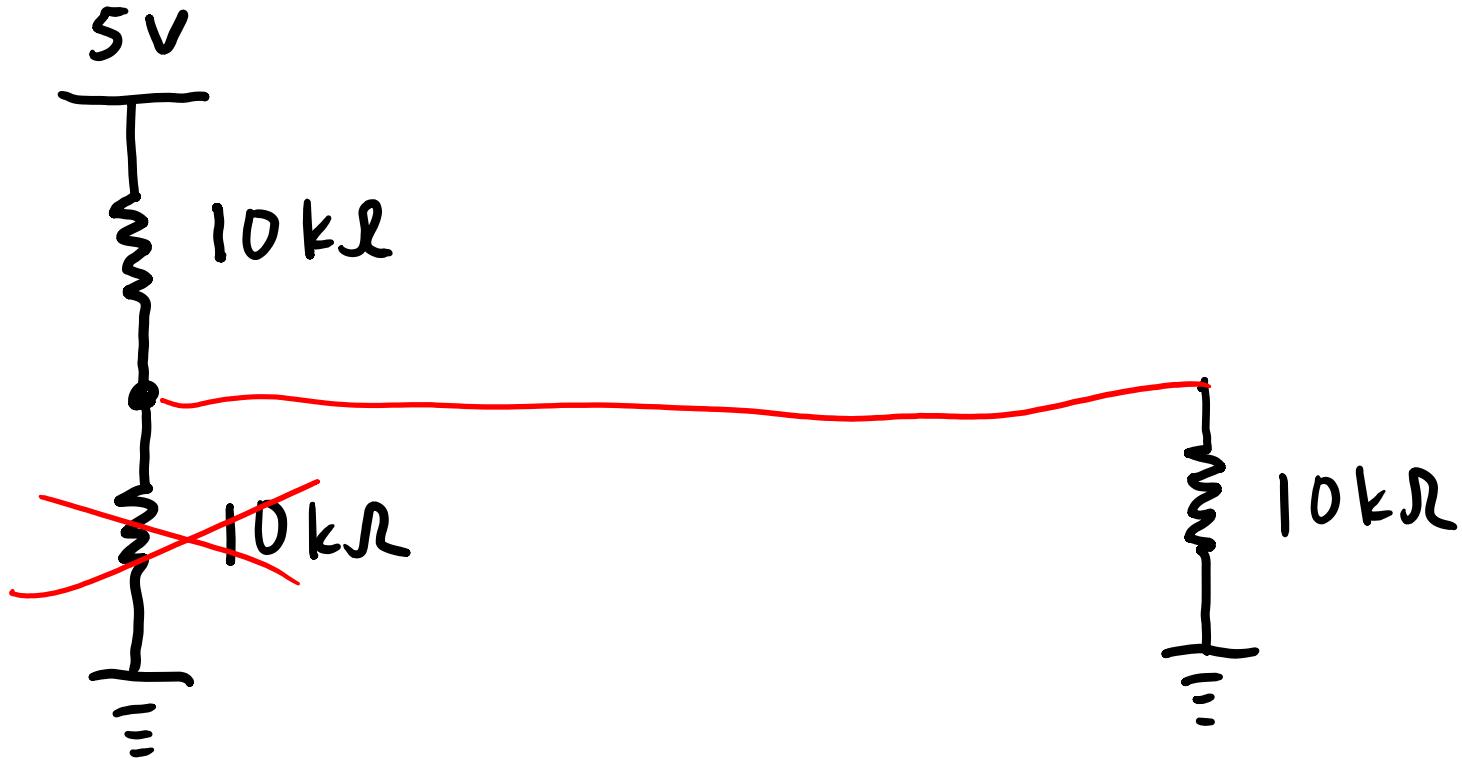
But what if we want to drive a load with 2.5V?



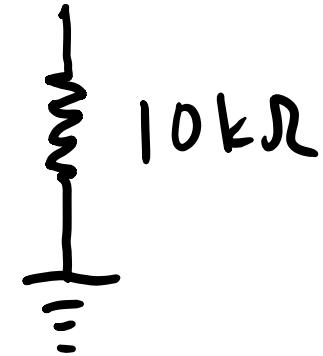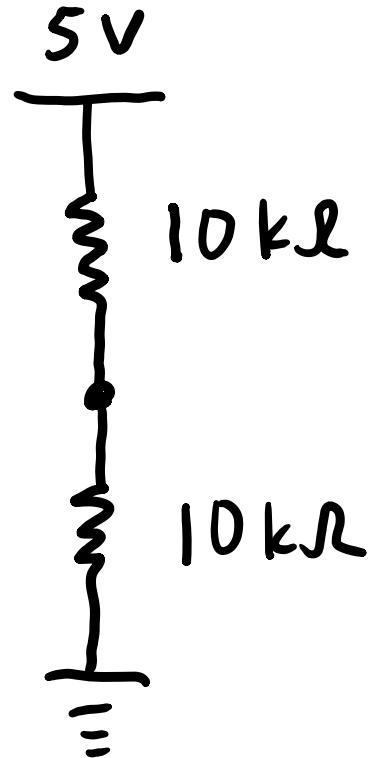
But what if we want to drive a load with 2.5V?



Let's use an op-amp!

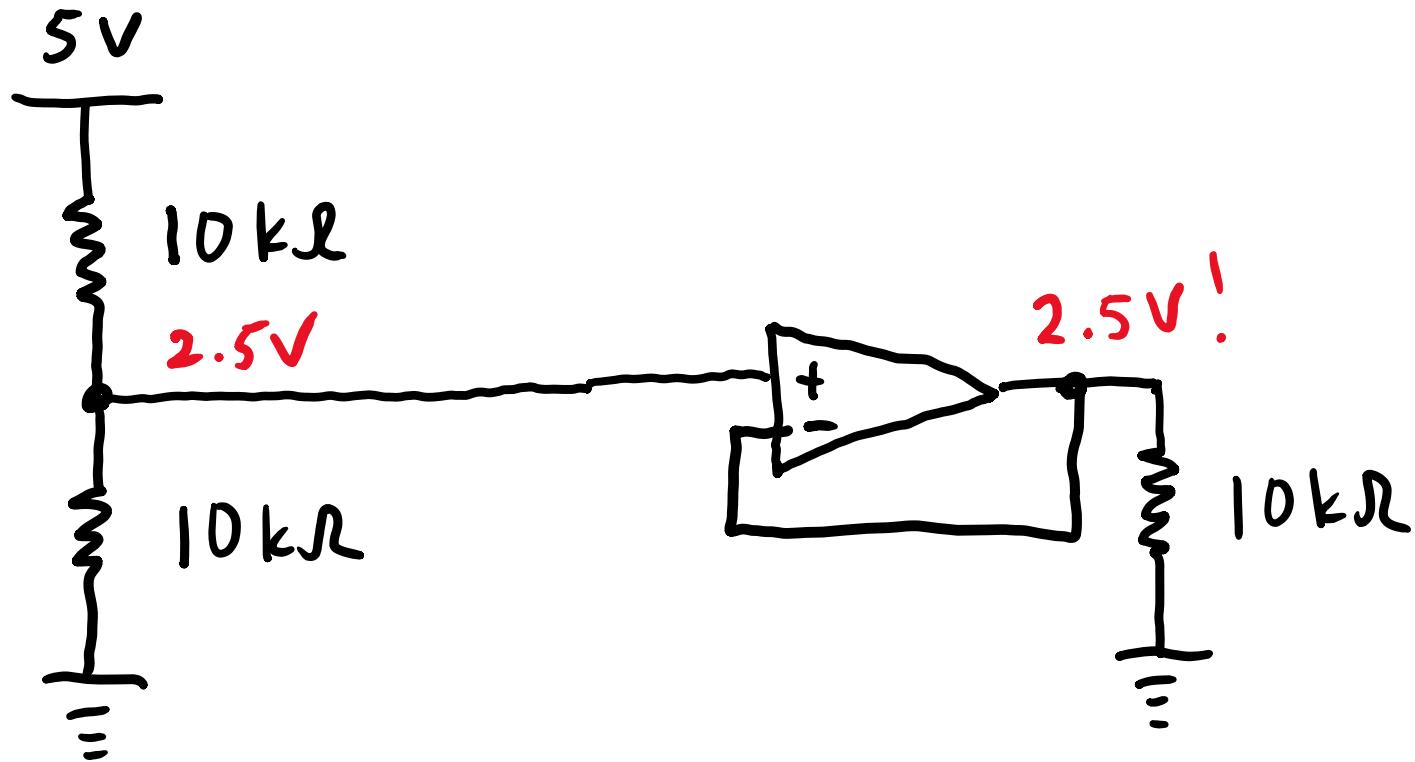

# Op-amp fundamentals: open loop

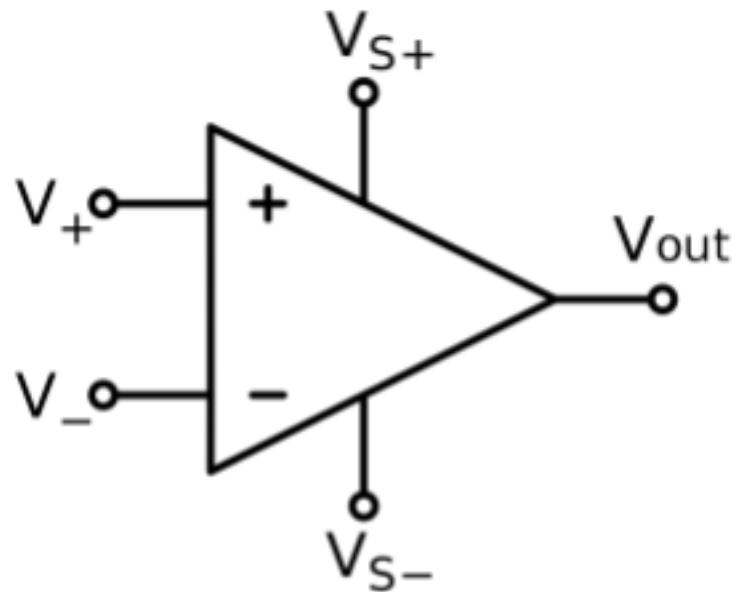


$$V_{out} = G [V_+ - V_-]$$

In technical terms, the gain,  $G$ , is *really, really big*.

For an *ideal* op-amp,  $G$  is infinite!


# Op-amp fundamentals: open loop

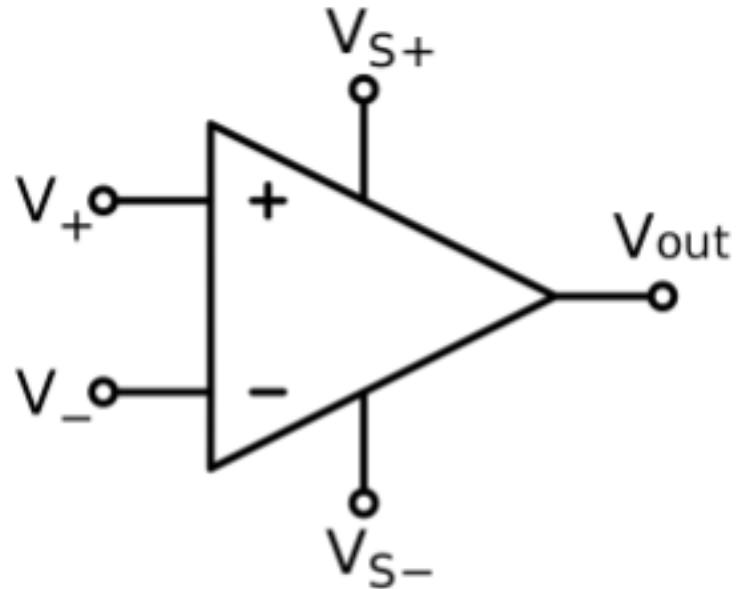

$$V_{out} \approx \begin{cases} V_{s+} & \text{if } V_+ > V_- \\ V_{s-} & \text{if } V_+ < V_- \end{cases}$$

$G$  is infinite, but we can't have infinite voltages. In practice, the output voltage is limited by the *rails*.


# Op-amp as a comparator

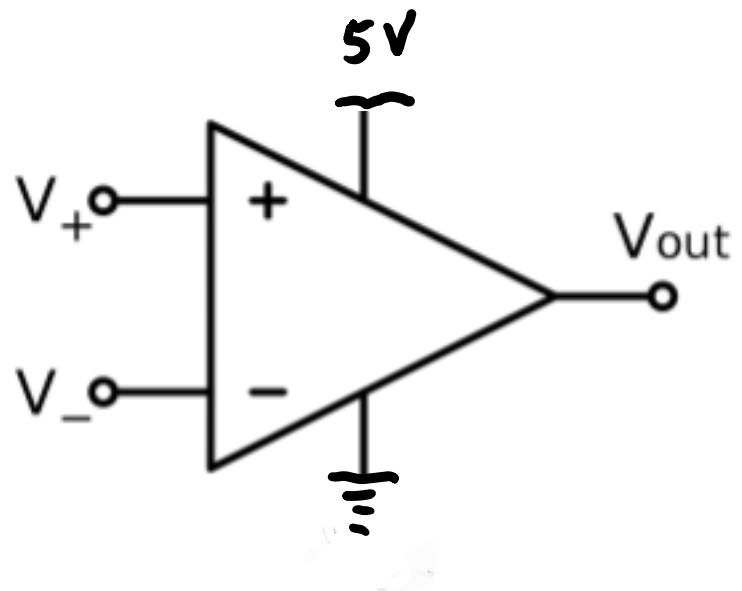

$$V_{out} \approx \begin{cases} 5\text{v} & \text{if } V_+ > V_- \\ 0\text{v} & \text{if } V_+ < V_- \end{cases}$$


When used in an open-loop, the op-amp acts as a *comparator*.

For example, an op-amp as a light switch

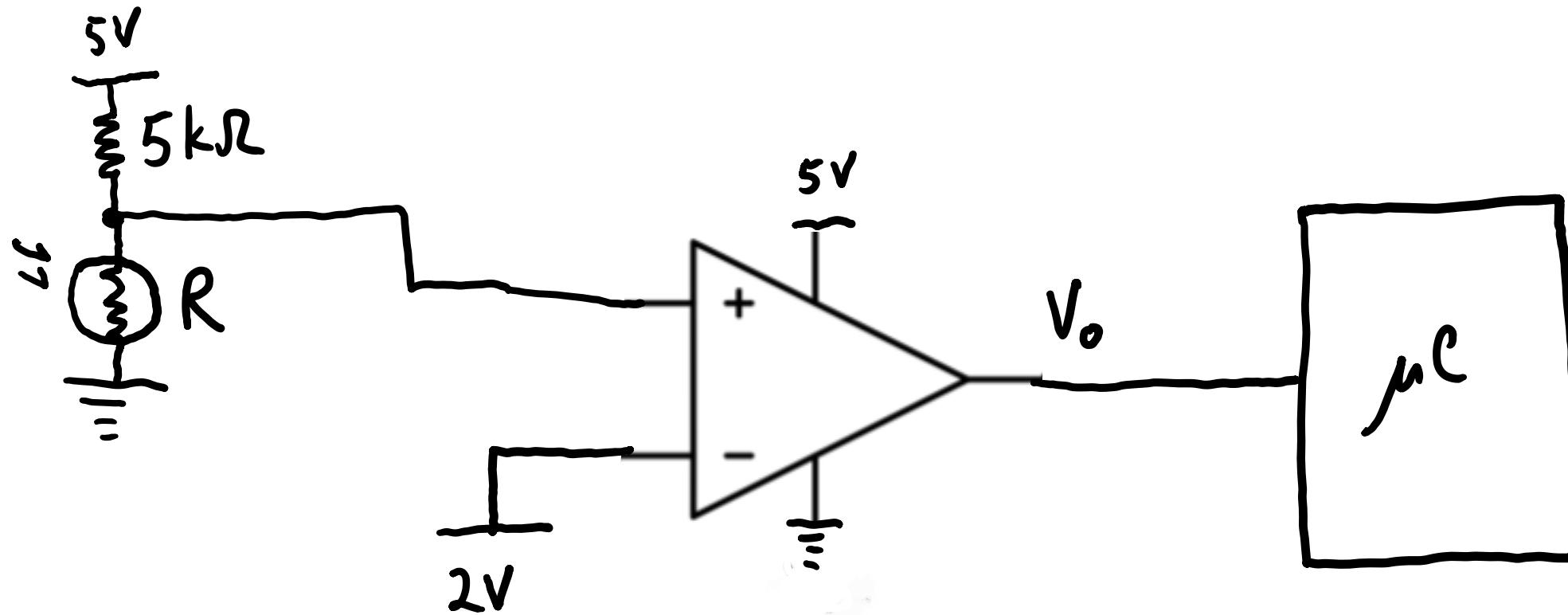

What values of R will produce a HIGH output and what will produce LOW?

For example, an op-amp as a light switch

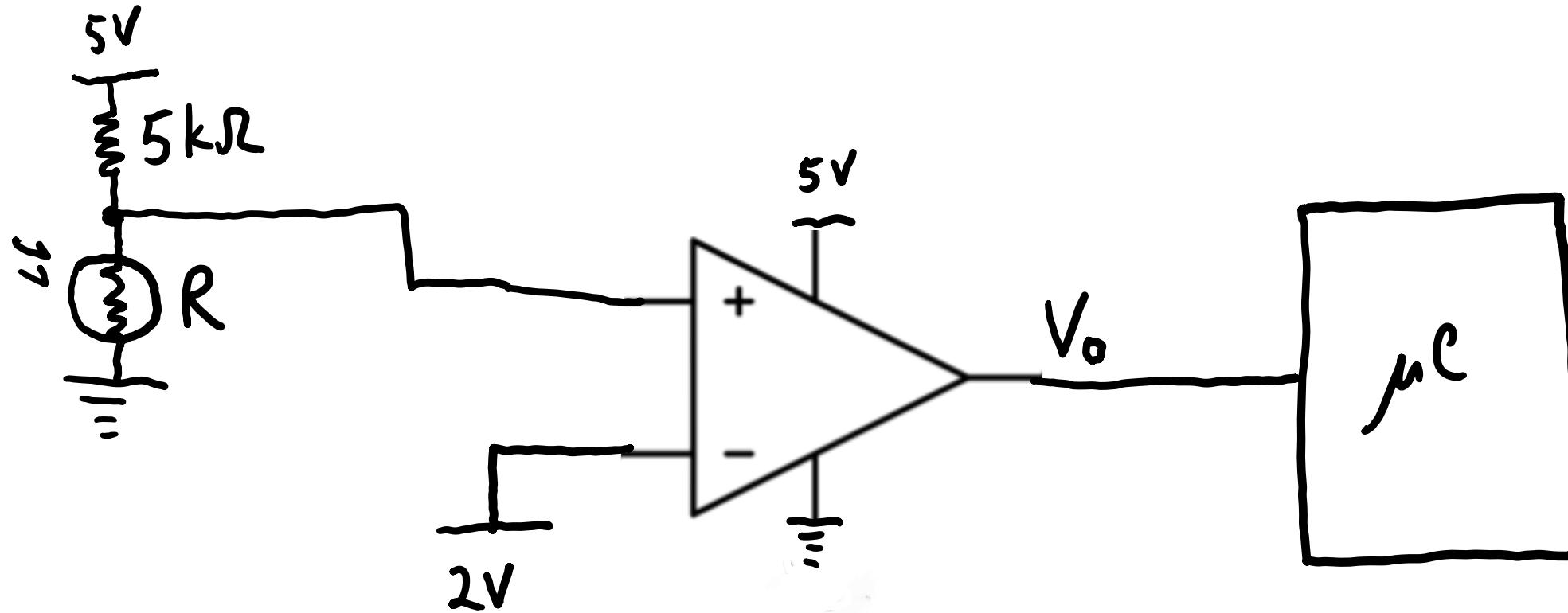


When  $R = 0 \text{ Ohm}$ , what is  $V_o$ ?

What about when  $R = 5 \text{ Ohm}$ ?


Where does the output switch?

For example, an op-amp as a light switch

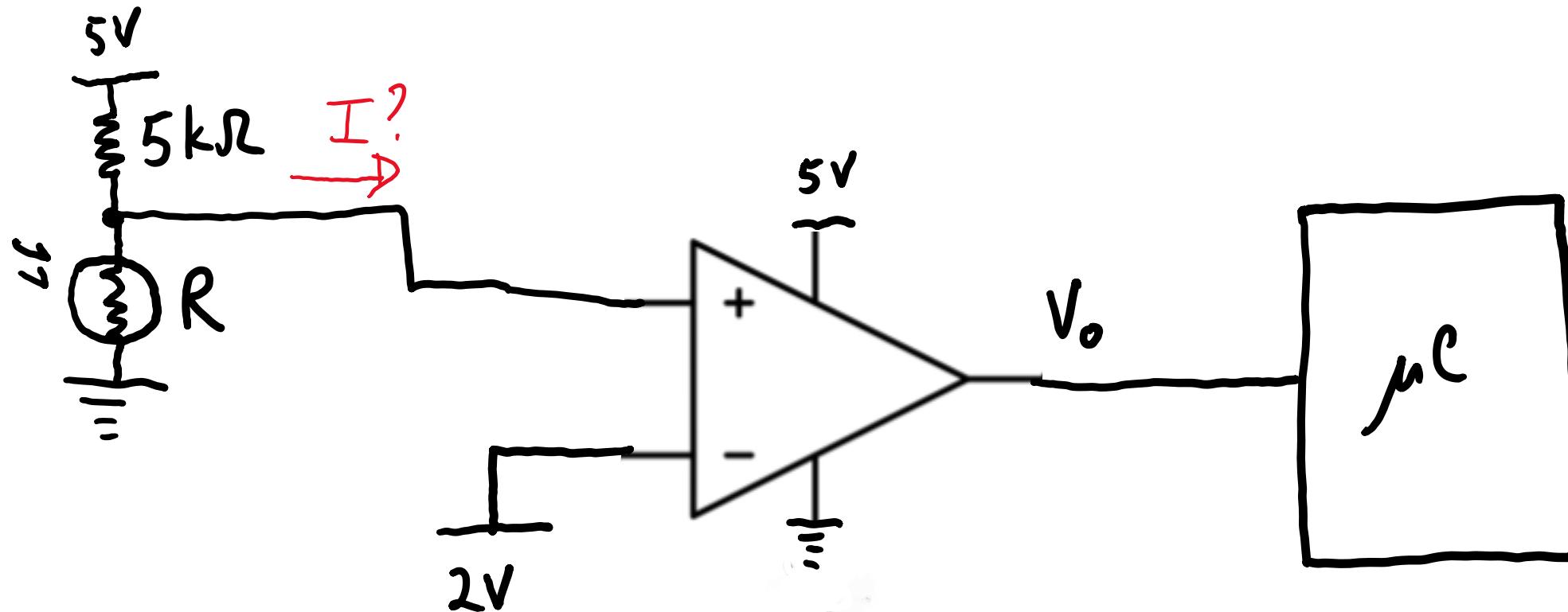



*Waitaminute, waitaminute.* Don't we have to assume that no current flows out of the voltage divider?

# Golden Rule #1

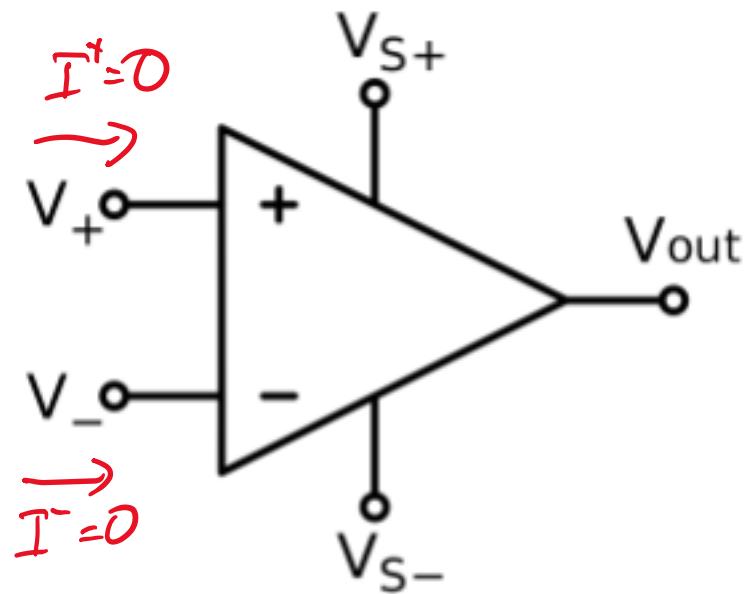


For an ideal op-amp, we assume that **no current flows into or out of the  $V_+$  and  $V_-$  terminals!**

# Comparator example

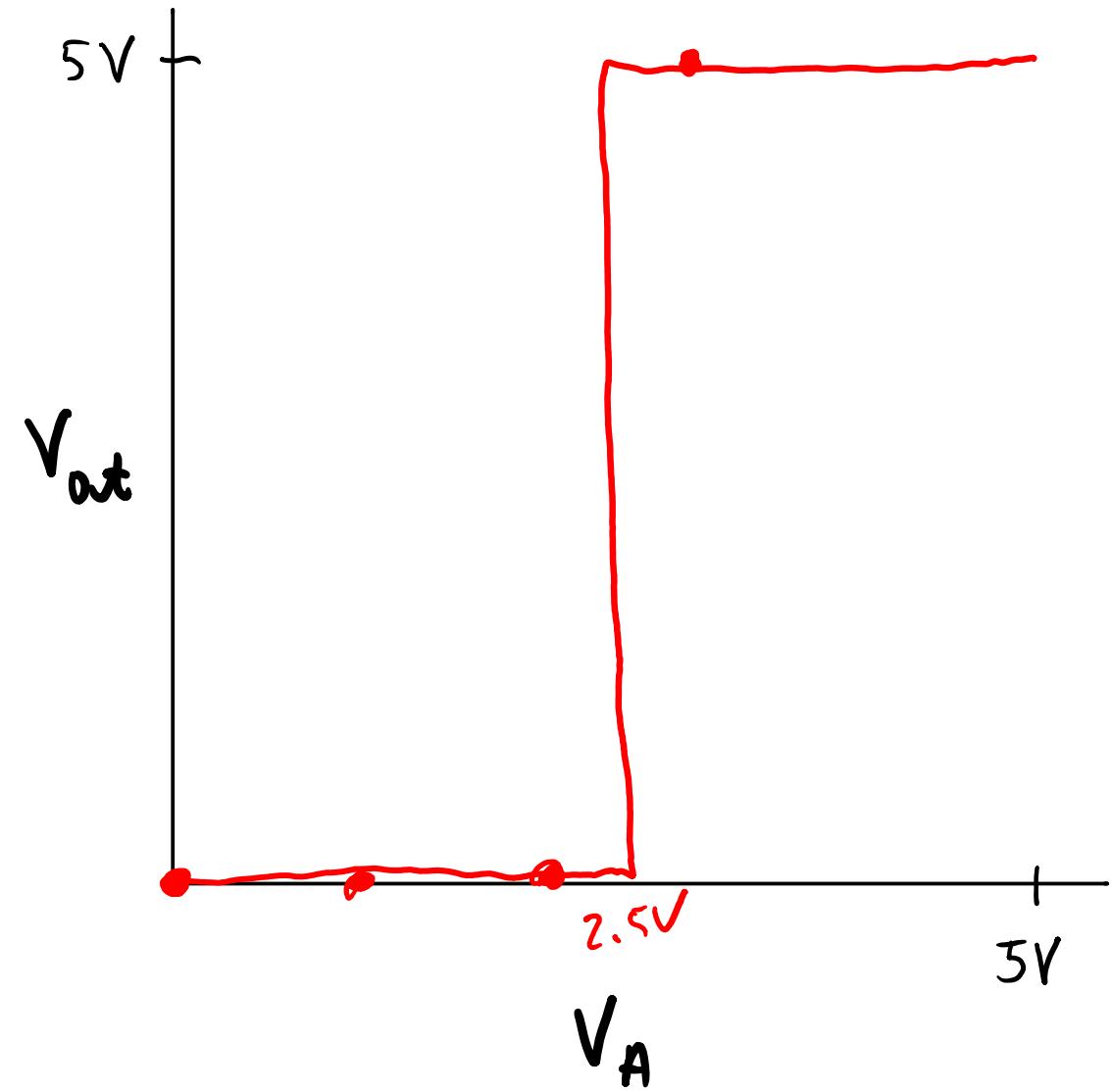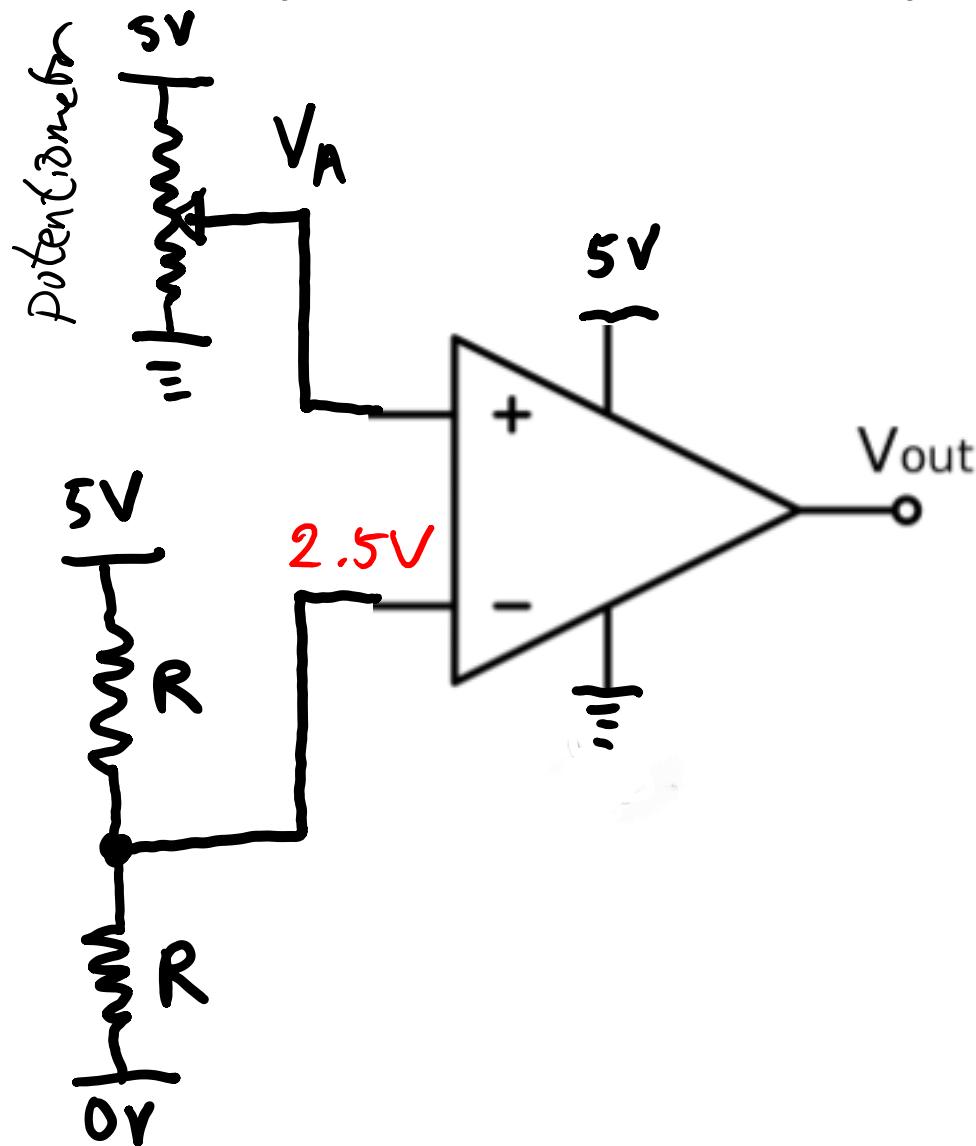


Returning to the earlier problem

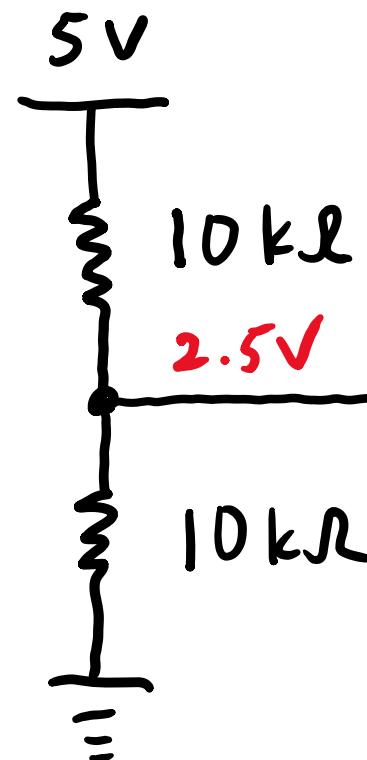


$$V_{out} = V_{in} \left[ 1 + \frac{R_f}{R_i} \right]$$

D

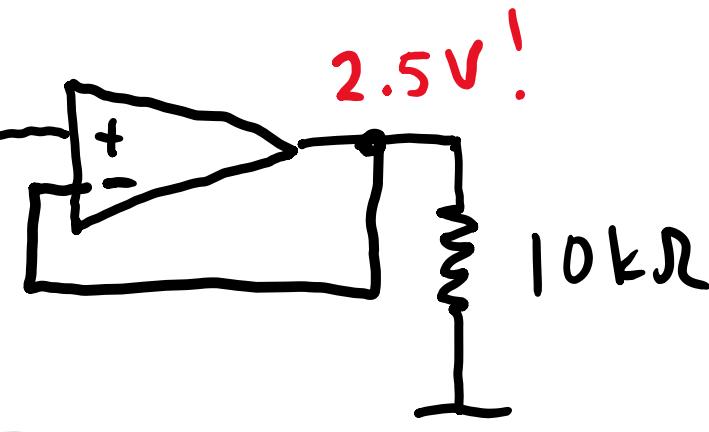

voltage buffer  $\Rightarrow$   $V_{out} = V_{in}$

# Op-amp as a voltage follower

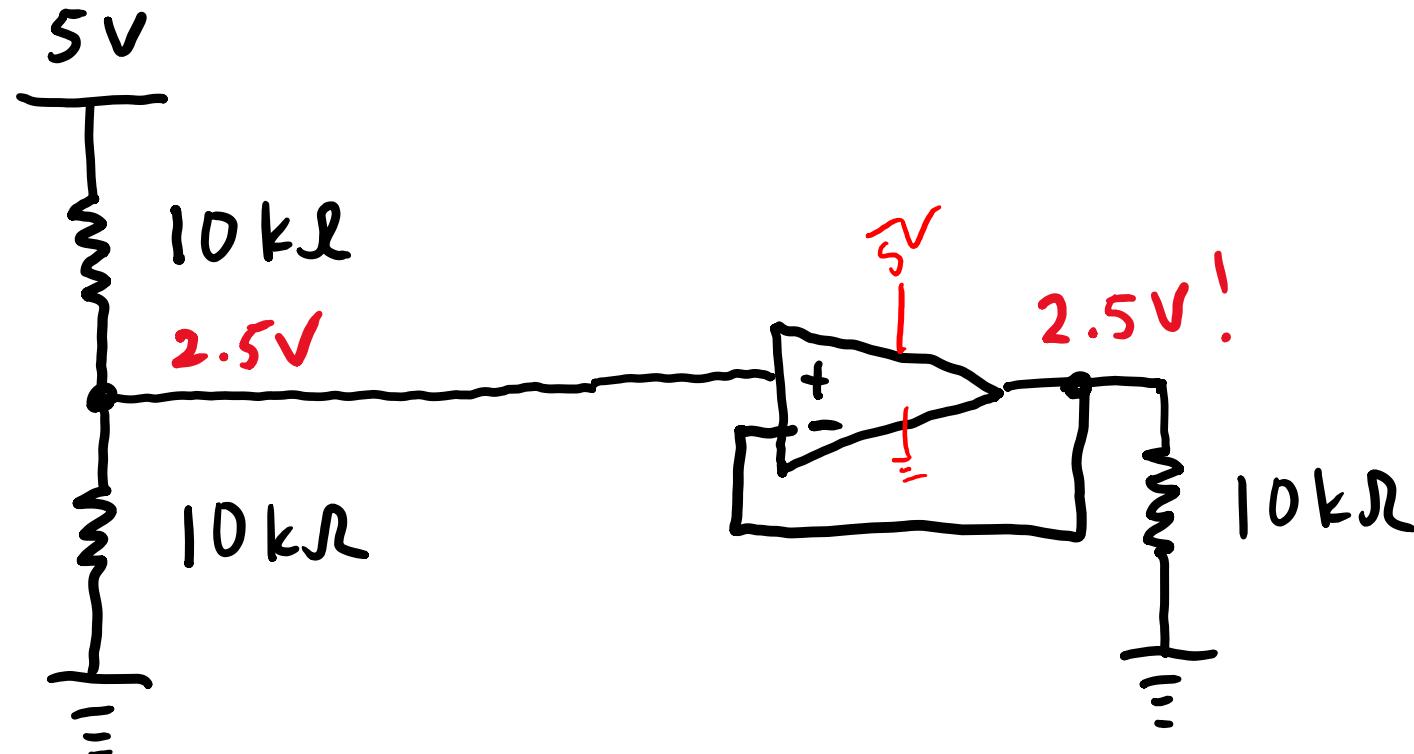

$$V_o = G(V^+ - V^-)$$


$$= G(V^+ - V_o)$$

$$\Rightarrow V_o[1 + G] = GV^+$$

$$V_o = V^+ \frac{G}{1+G} = V^+$$

$\approx 1 + \infty$

# Golden Rule #2

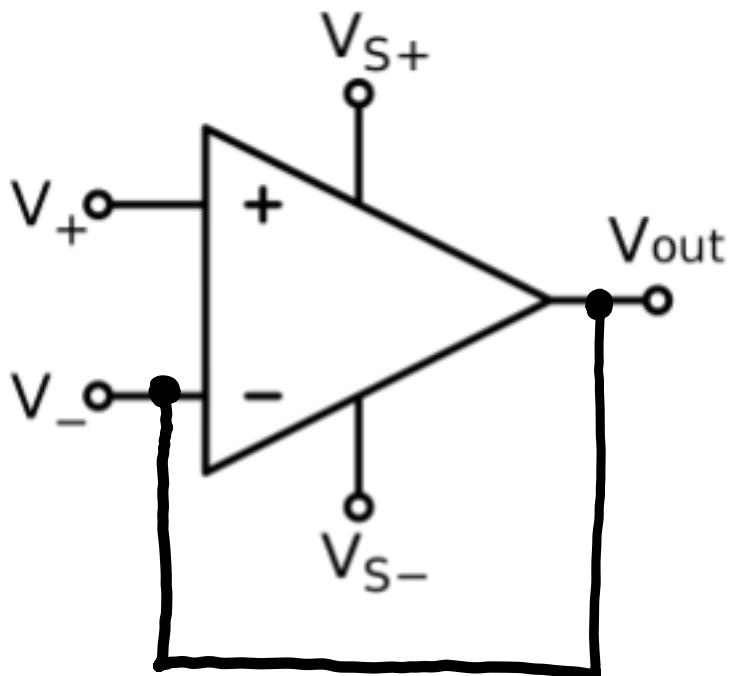


When wired in a negative feedback loop, the op-amp will “do whatever it takes” to make  $V_-$  equal to  $V_+$ .


Say you have a light sensor that returns 0 V at 0 lux and 1 V at 100 lux. You want to increase the sensitivity such that it reads 5 V at 100 lux. That is, you want to increase the sensitivity from 10 mV / lux to 50 mV / lux.

**What does a budding roboticist do?**


Let's see what happens with this

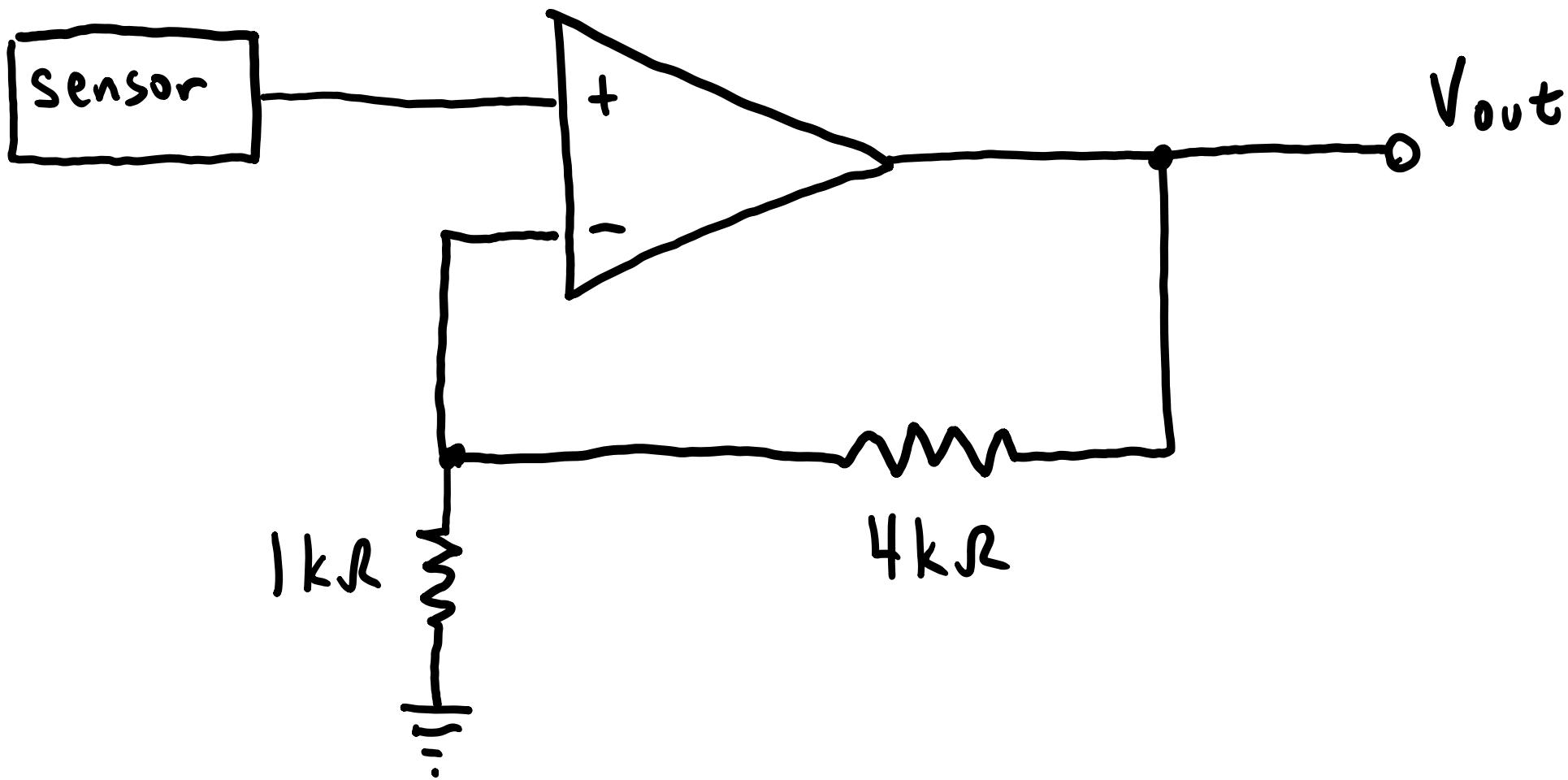


Let's see what happens with this

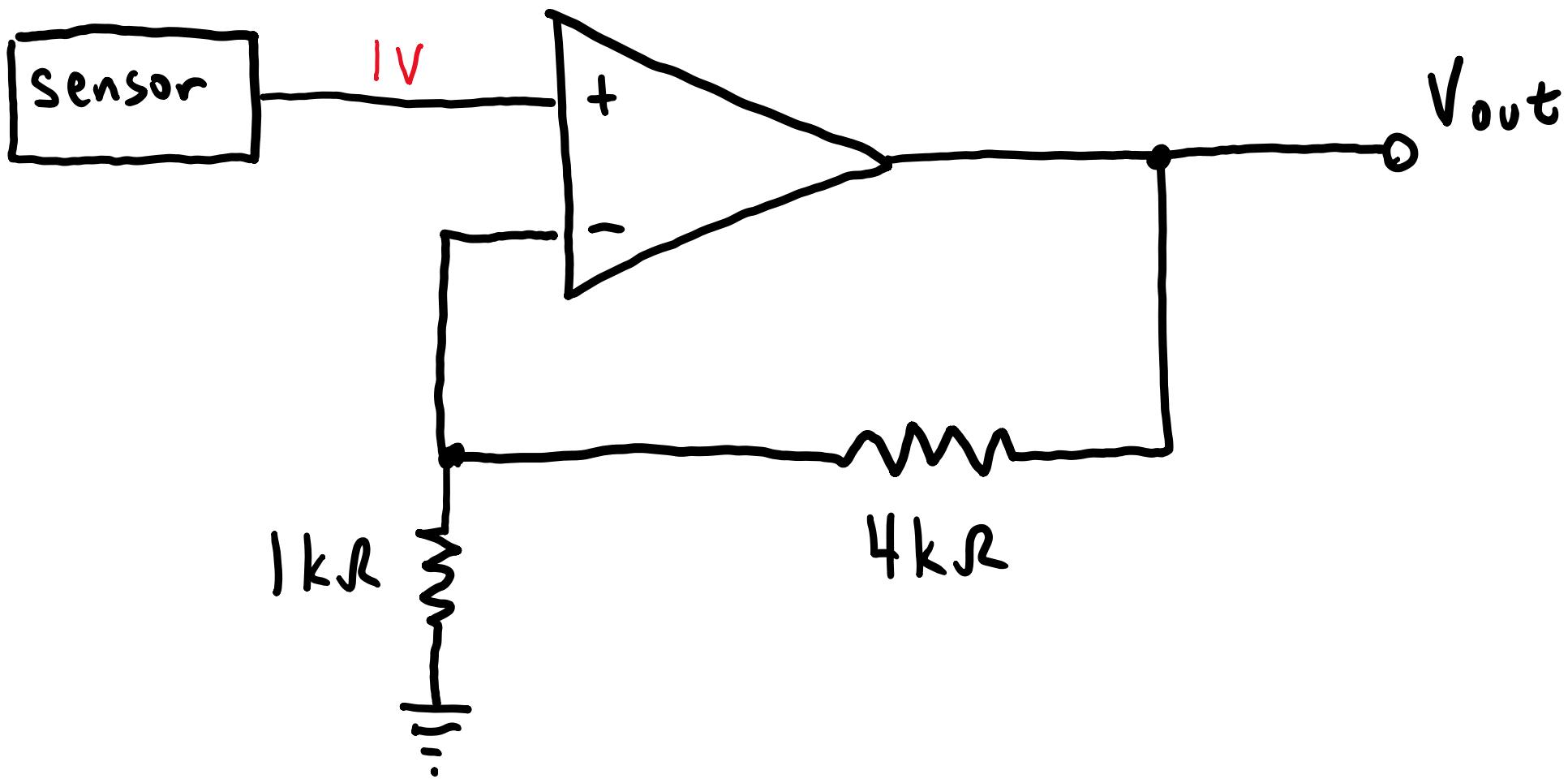


Let's see what happens with this

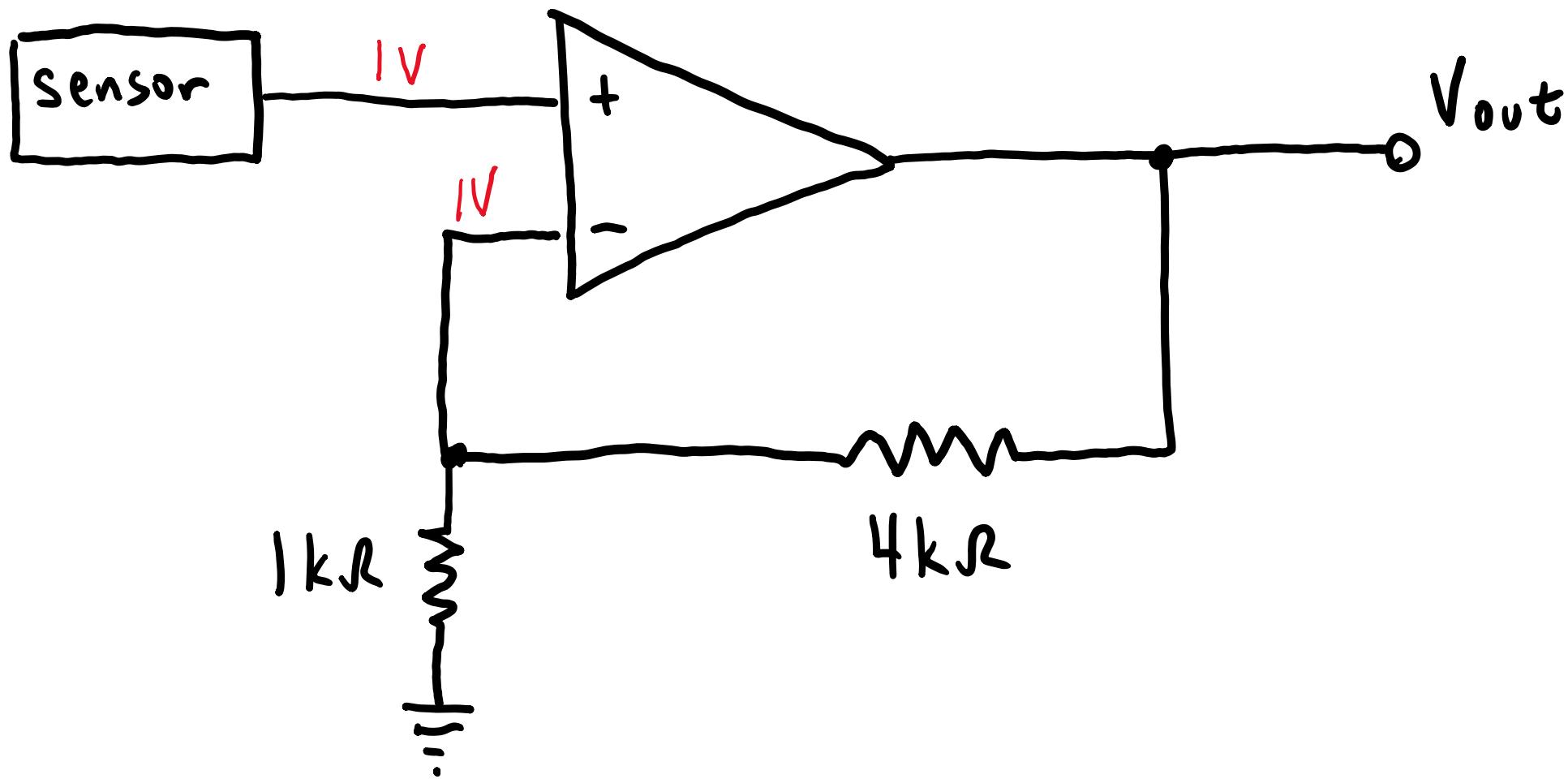


Let's see what happens with this


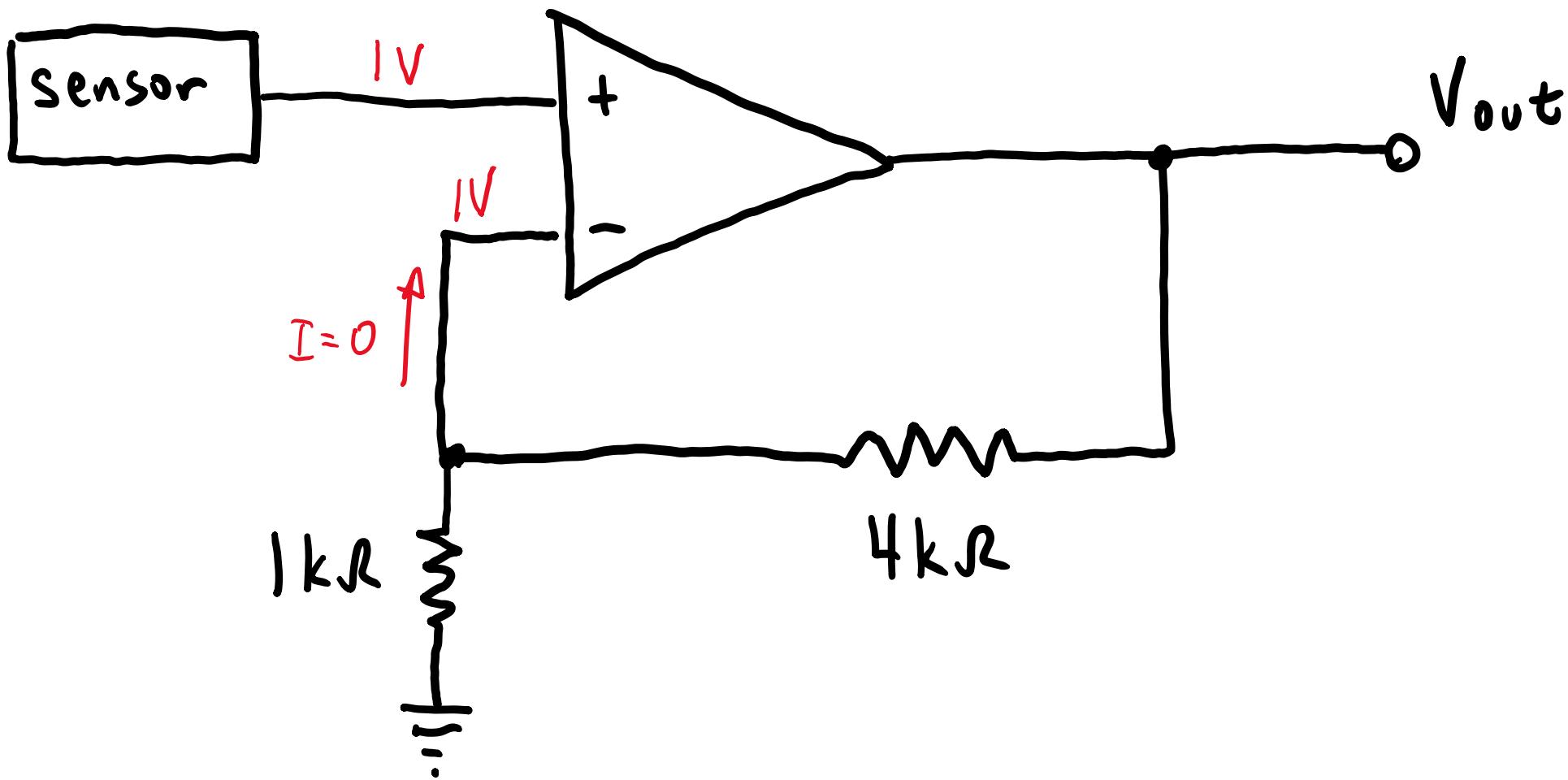


Let's see what happens with this

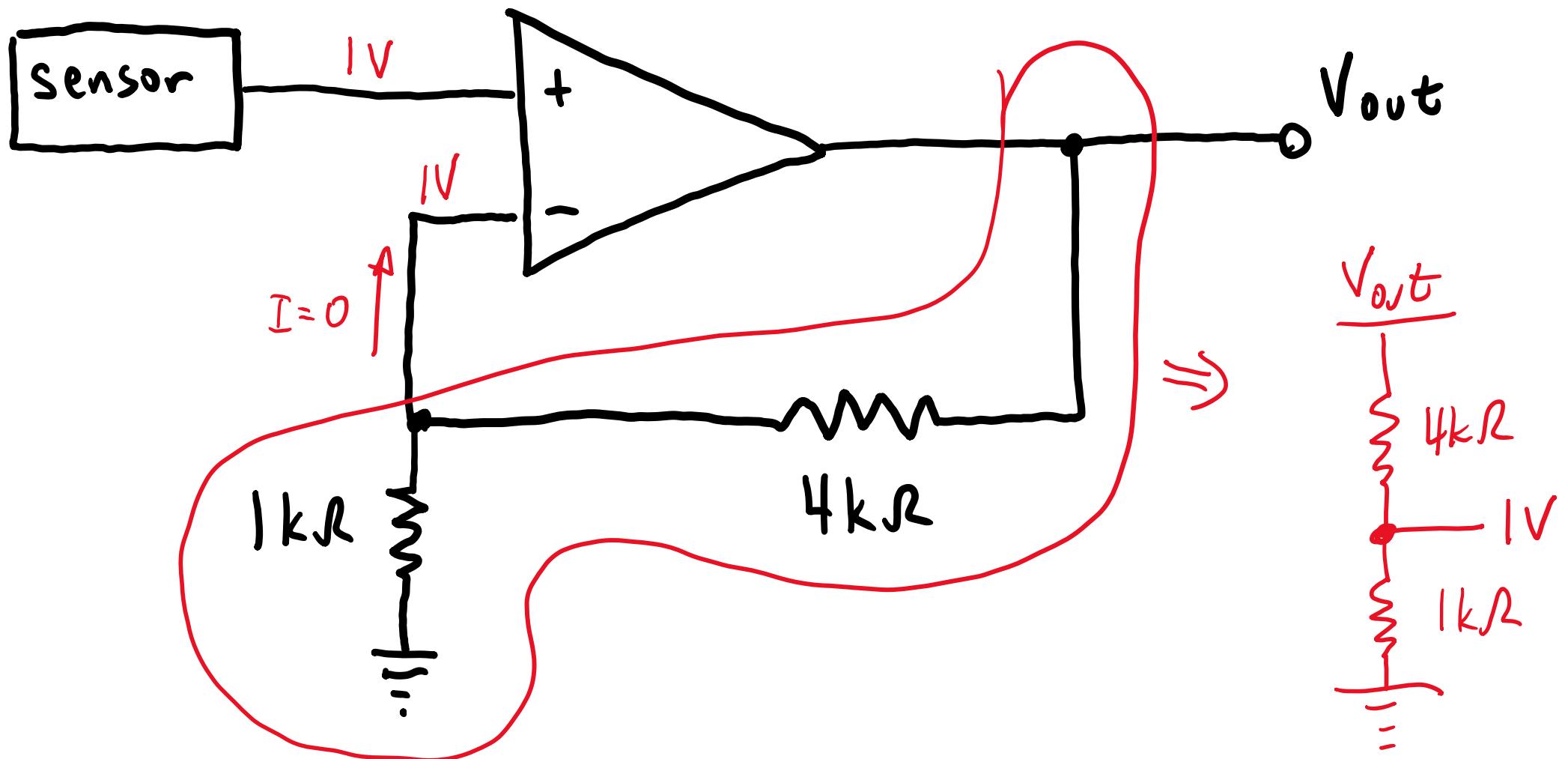


Your turn!

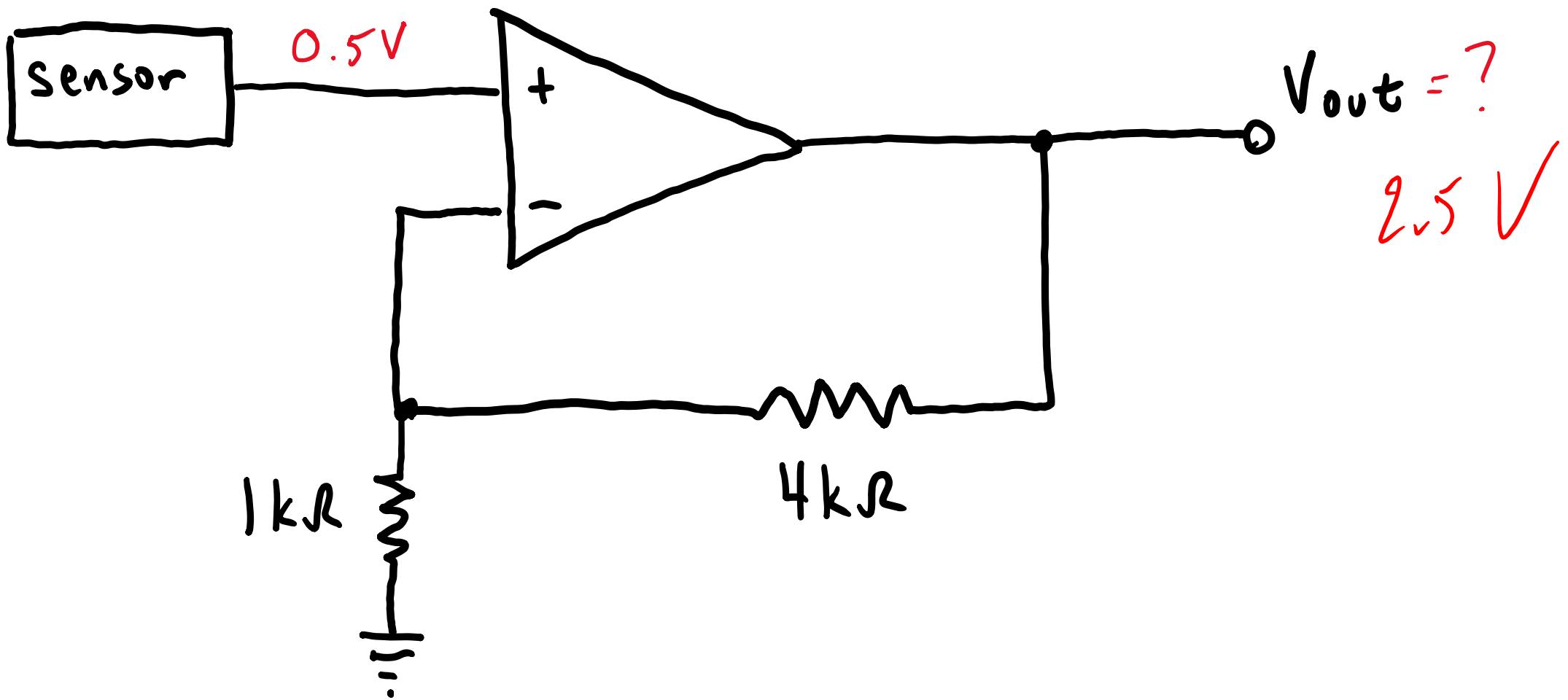


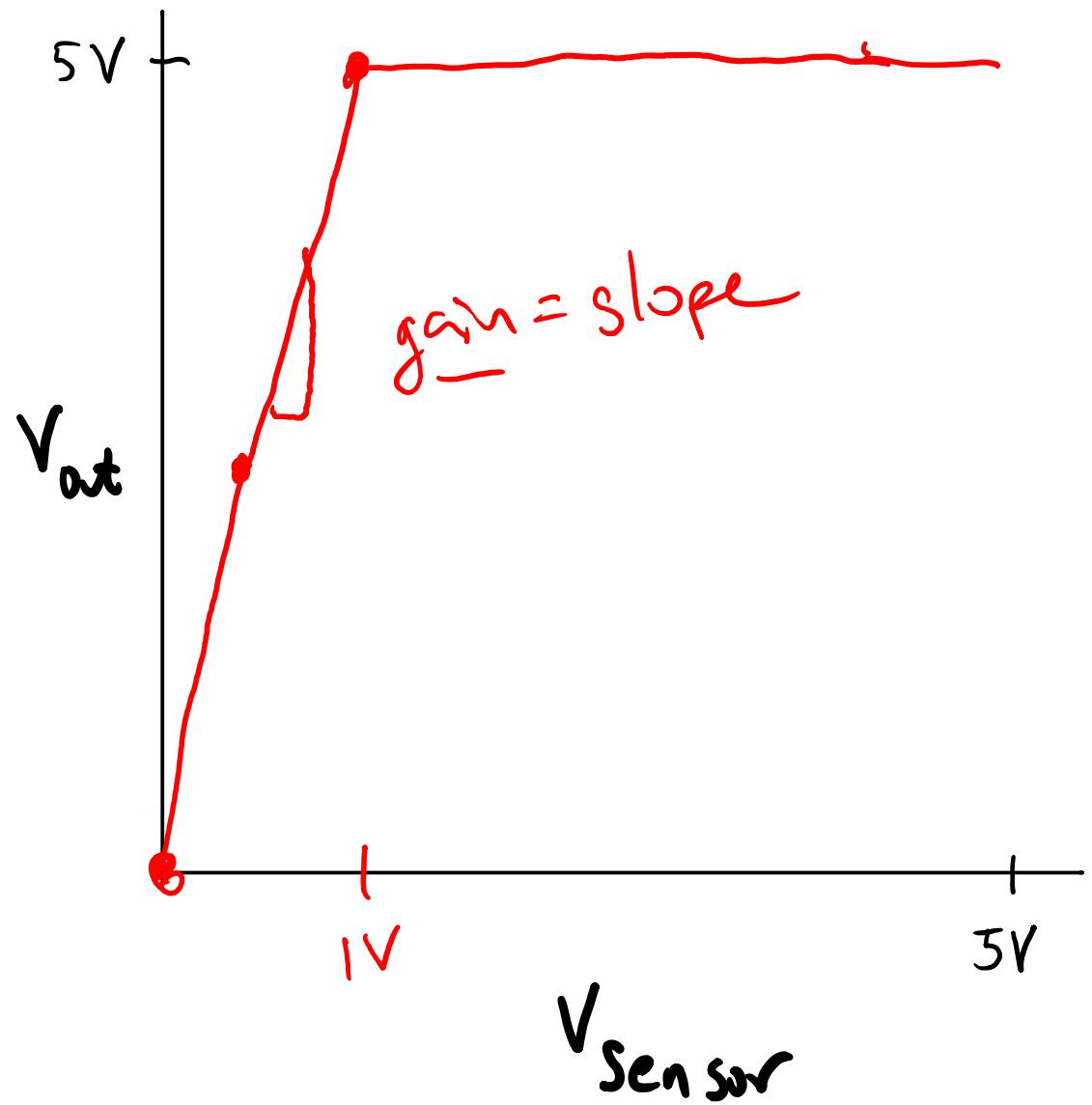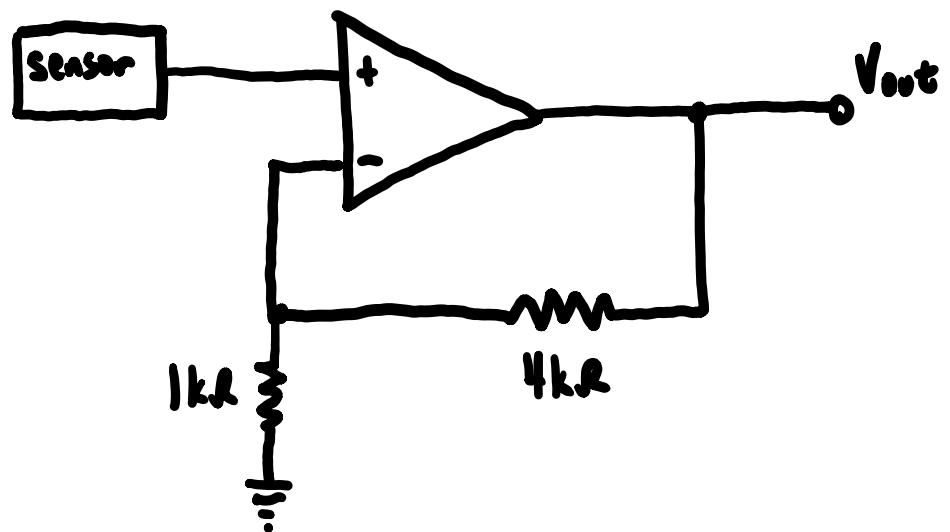

# What is “gain”?

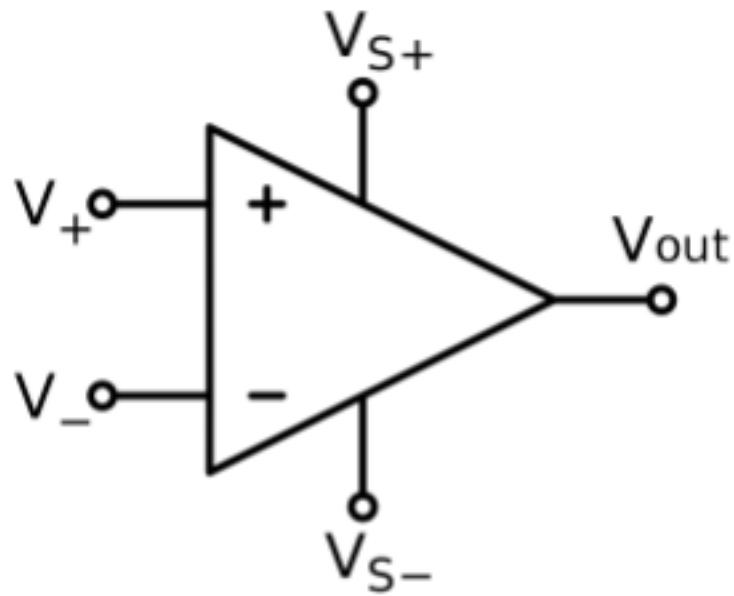


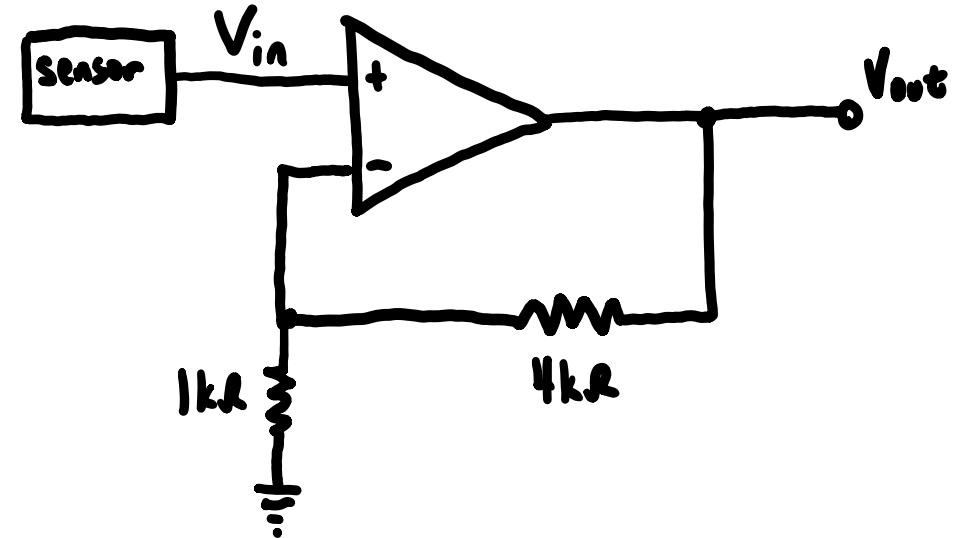The gain of a ‘bare’ op-amp is very large...




...but the usefulness of an op-amp comes from putting it in a circuit.

# What is “gain”?

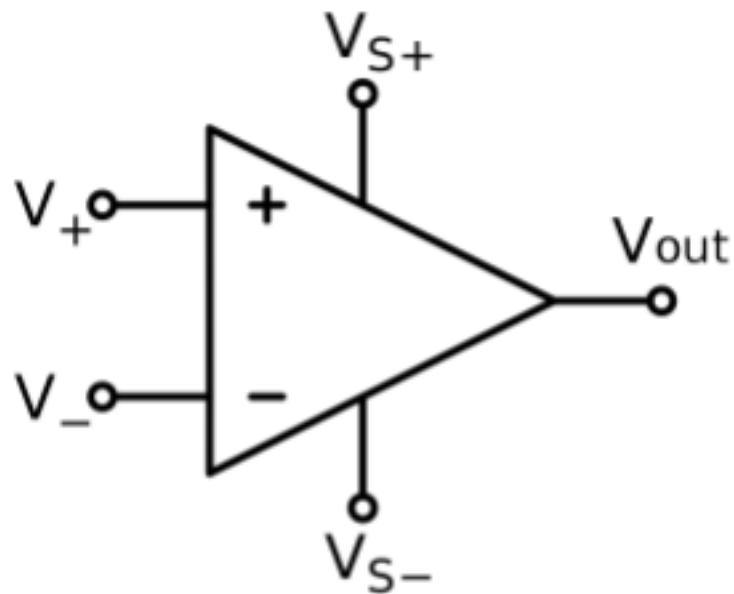

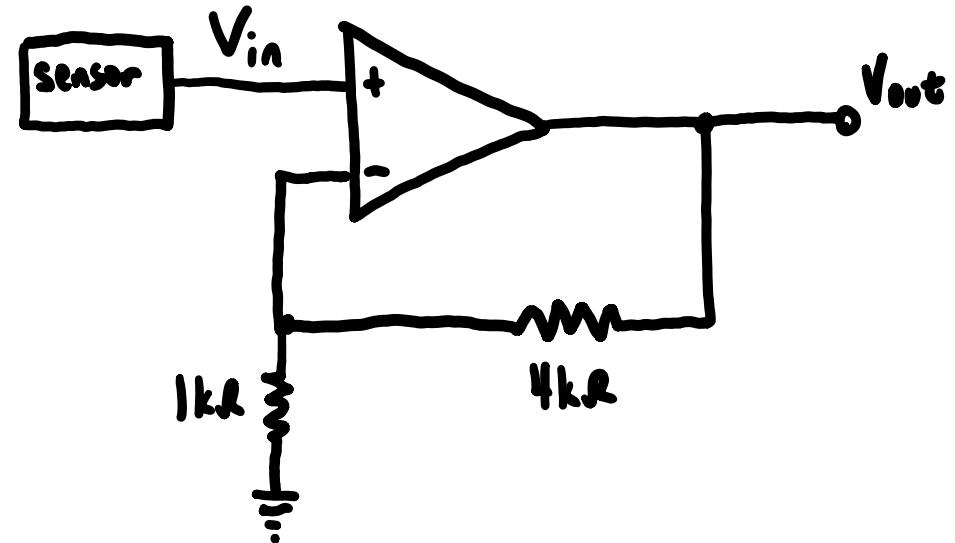
So the gain of an op-amp is just for reference.





In practice, you need to be able to find the *relationship between input and output voltages*. The slope of that relationship is the gain of the circuit.

$$\text{gain} = \frac{dV_{out}}{dV_{in}}$$

# Revisiting the non-inverting op-amp


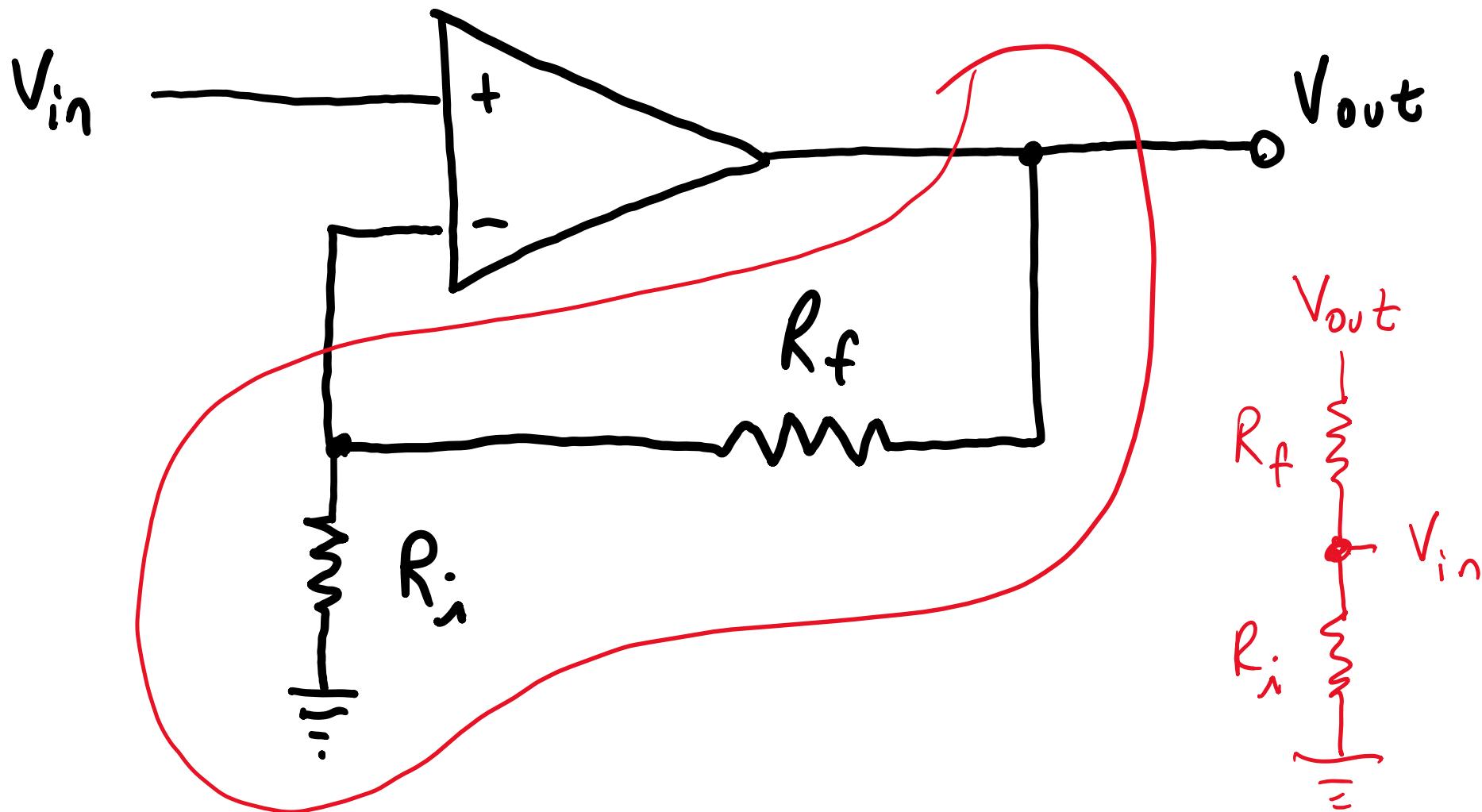


# Non-inverting op-amp

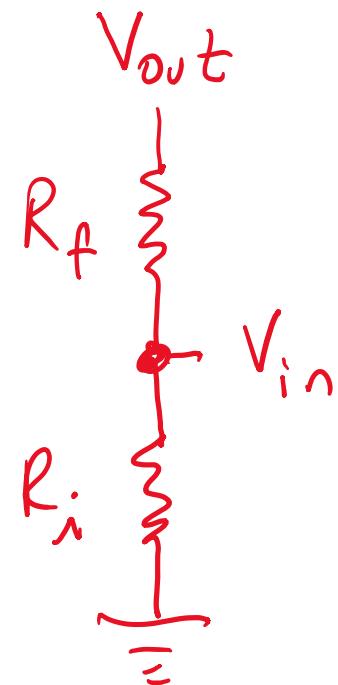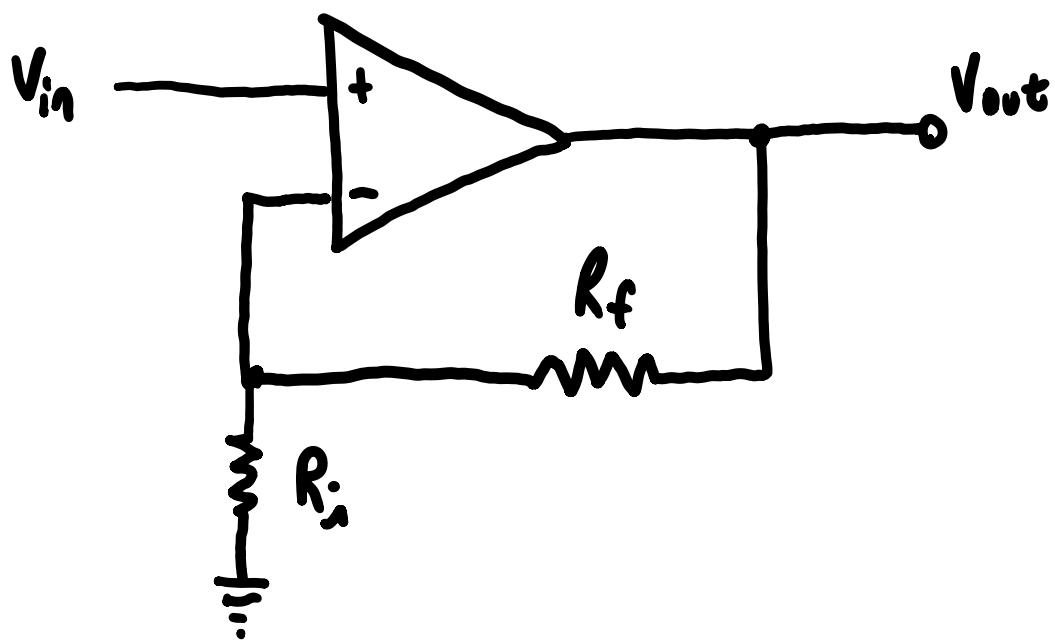

$$V_{in} = V_{out} \frac{R_i}{R_i + R_f}$$



# Non-inverting op-amp

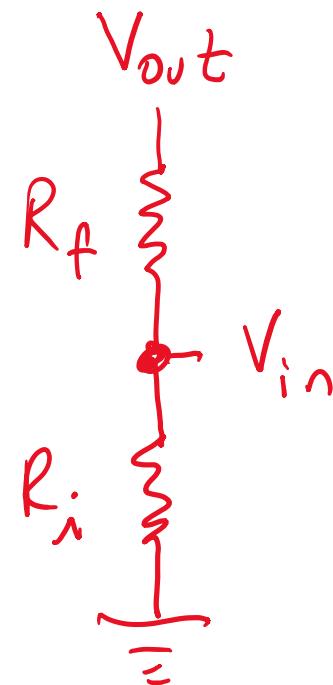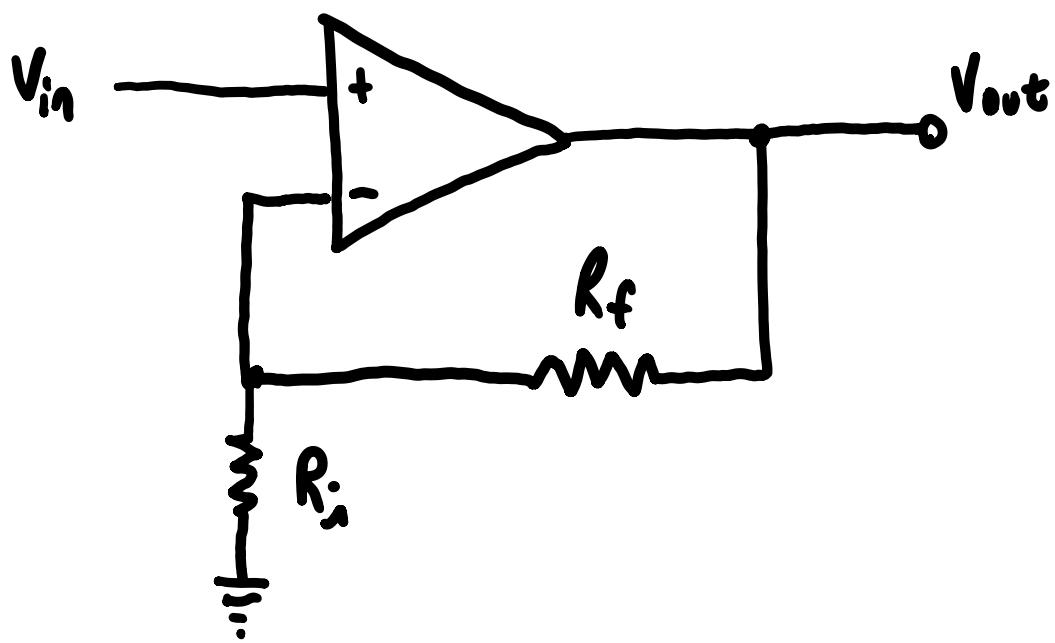

$$V_{in} = V_{out} \frac{R_i}{R_i + R_f}$$

$$V_{out} = V_{in} \frac{R_i + R_f}{R_i}$$

# Non-inverting op-amp

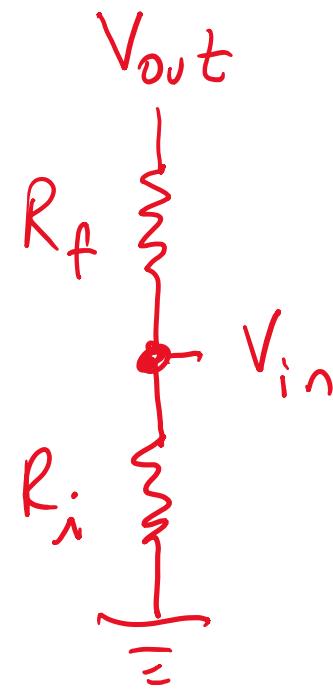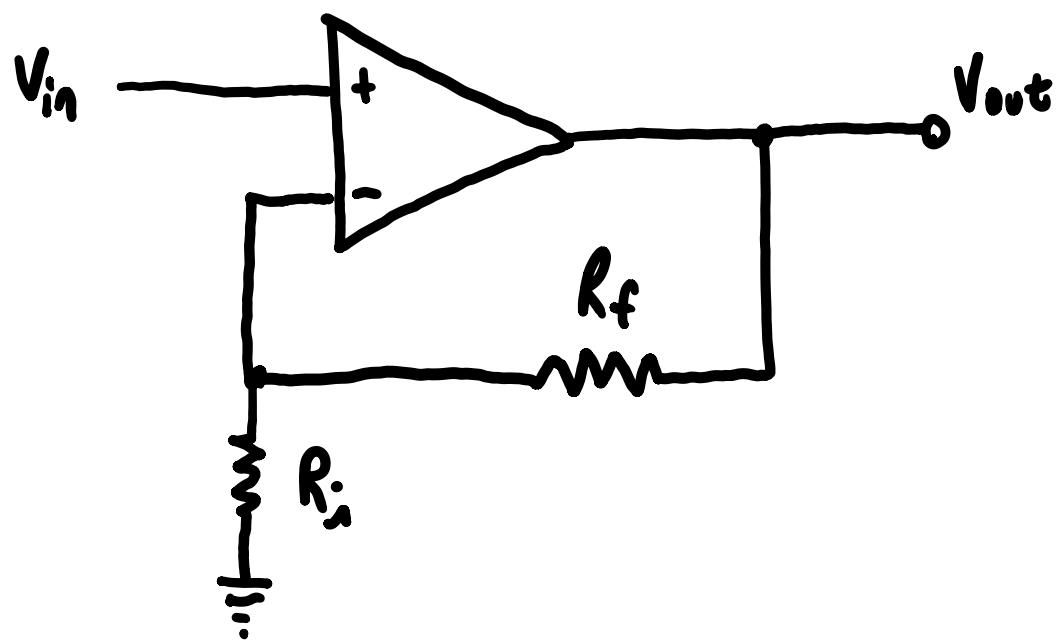


$$V_{in} = V_{out} \frac{R_i}{R_i + R_f}$$

$$V_{out} = V_{in} \frac{R_i + R_f}{R_i}$$


$$V_{out} = V_{in} \left[ 1 + \frac{R_f}{R_i} \right]$$

GAIN



# The inverting op-amp circuit

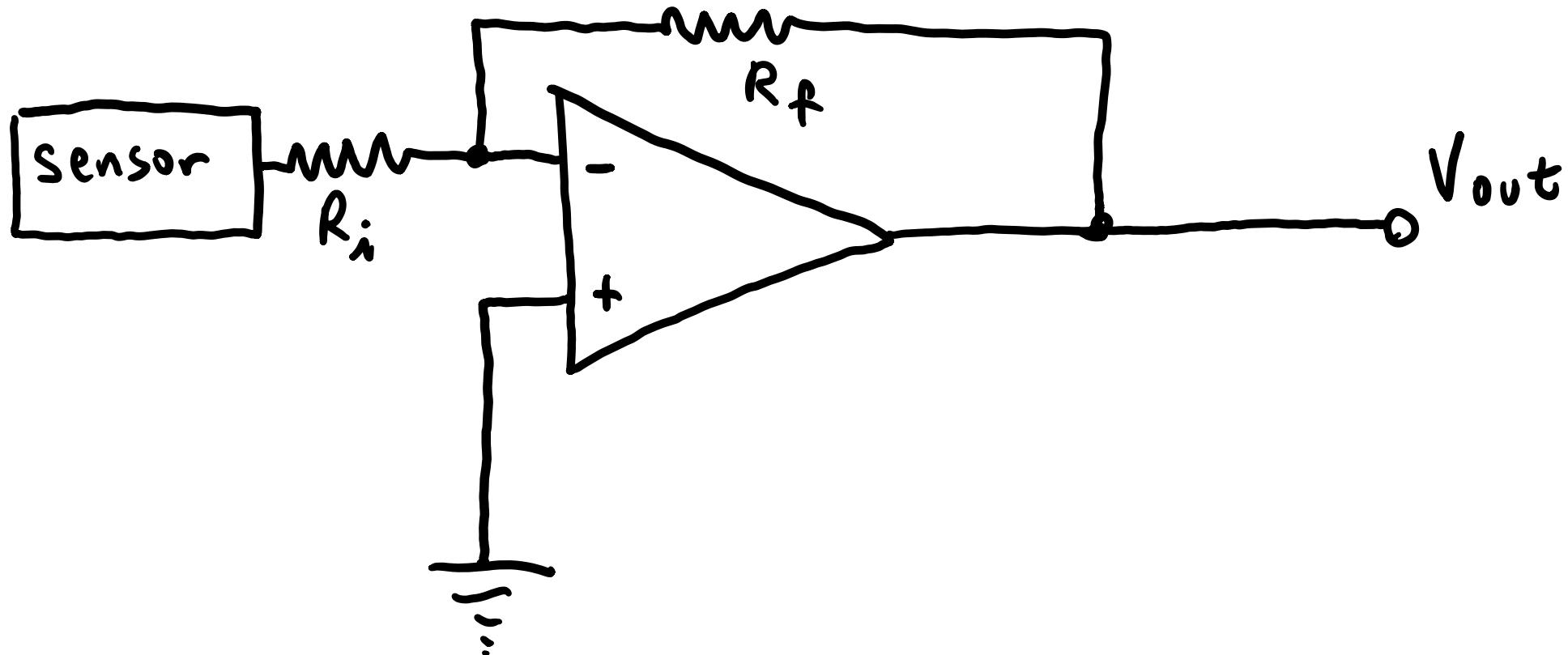

# The inverting op-amp circuit


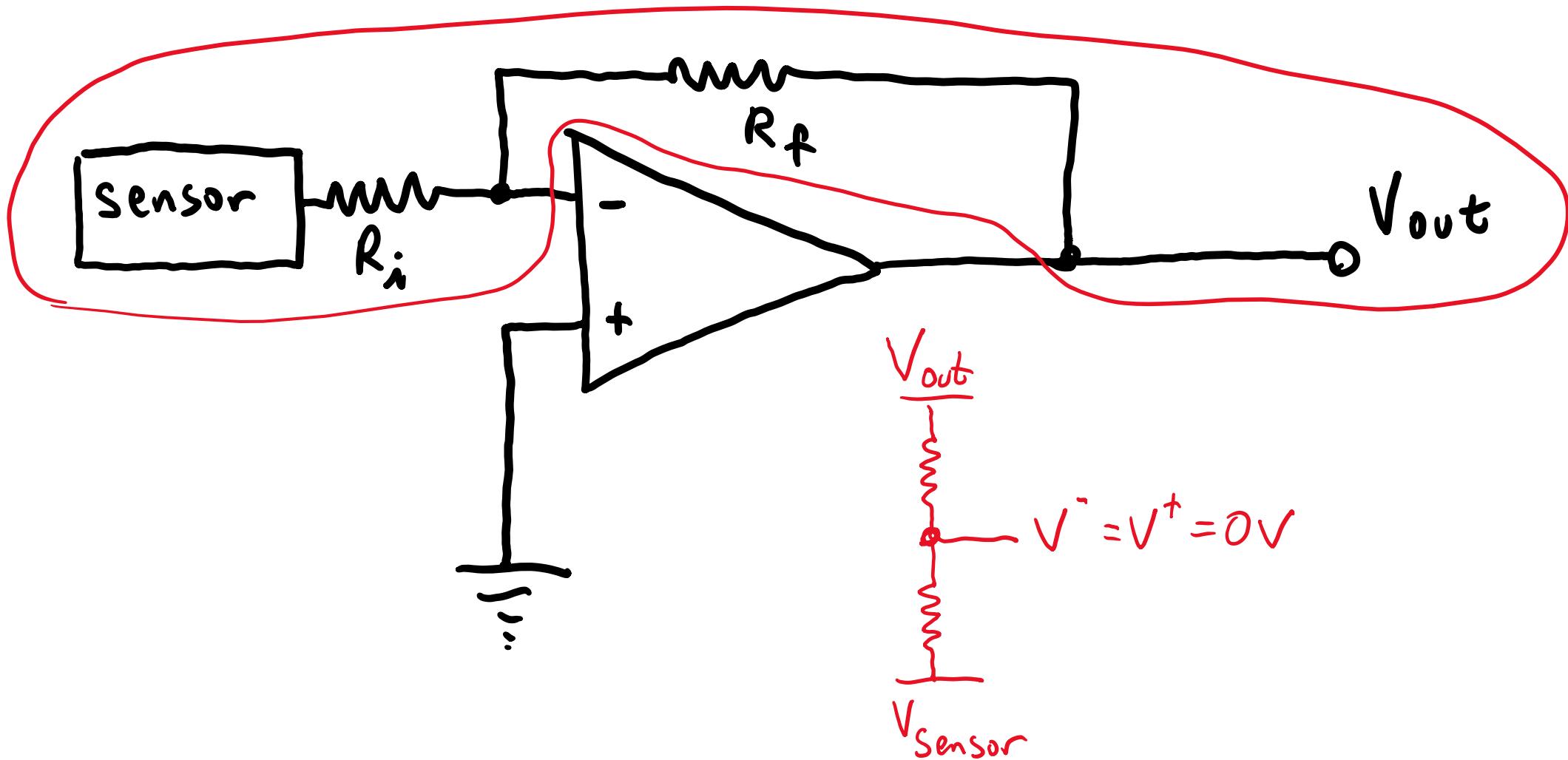


# The inverting op-amp circuit

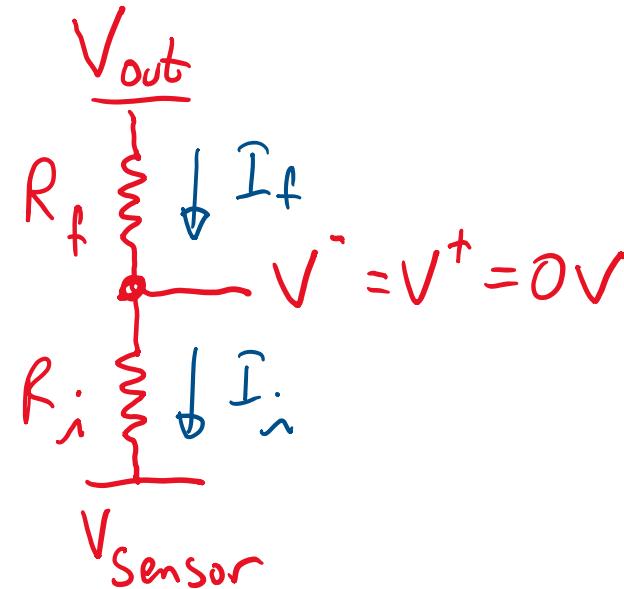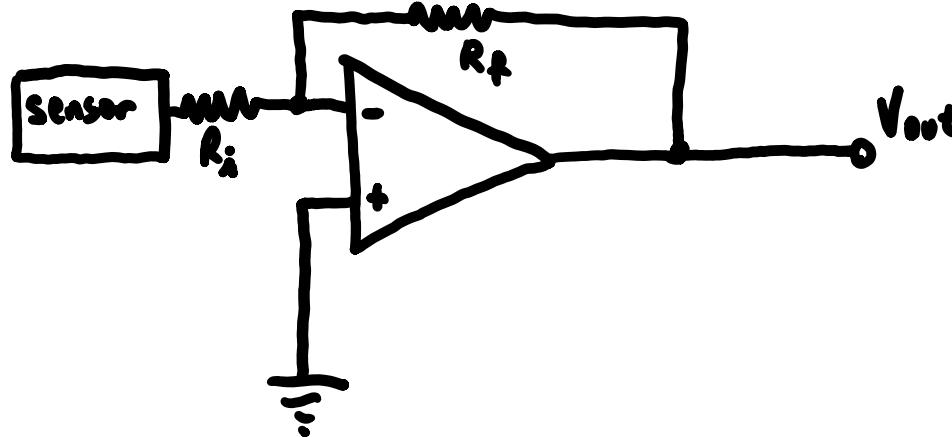



$$\frac{V_{out}}{R_f} = -\frac{V_{Sensor}}{R_i} \Rightarrow$$

# The inverting op-amp circuit

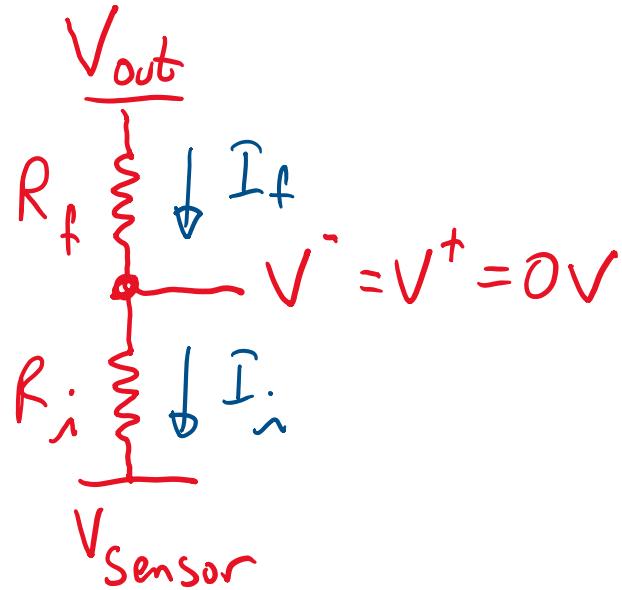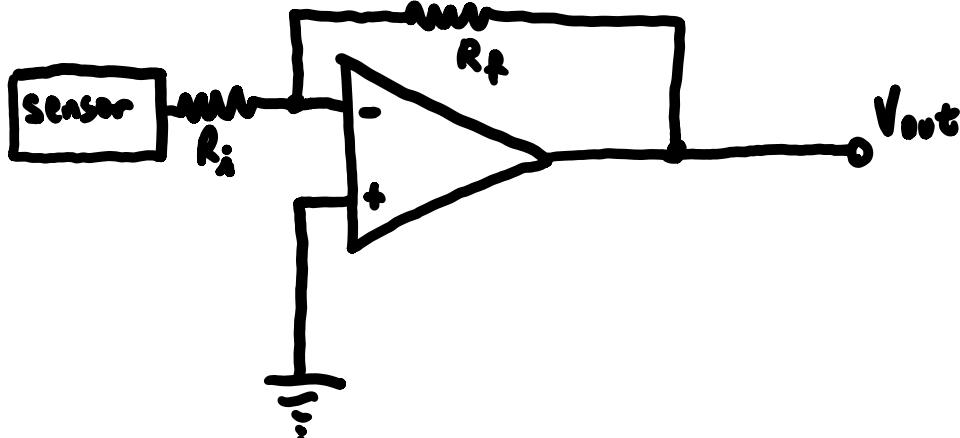

$$\frac{V_{out}}{R_f} = -\frac{V_{Sensor}}{R_i} \Rightarrow V_{out} = -\frac{R_f}{R_i} V_{Sensor}$$


# The inverting op-amp circuit

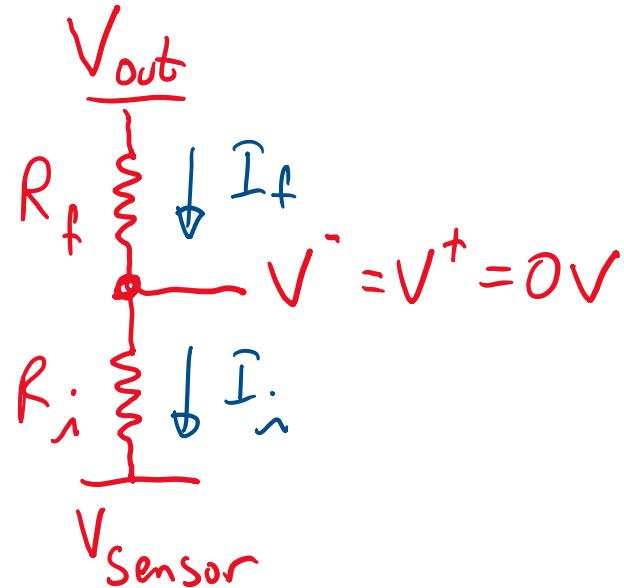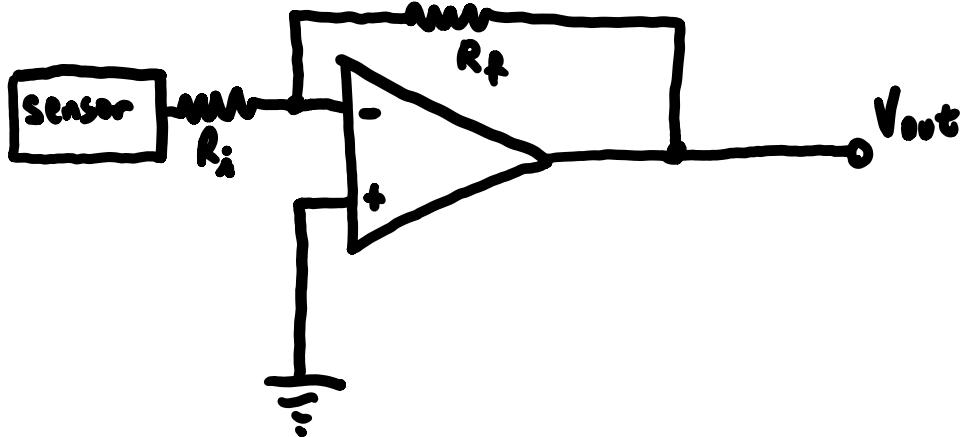



gain < 0!


$$\frac{V_{out}}{R_f} = -\frac{V_{Sensor}}{R_i} \Rightarrow V_{out} = -\frac{R_f}{R_i} V_{Sensor}$$

There's nothing magic about ground

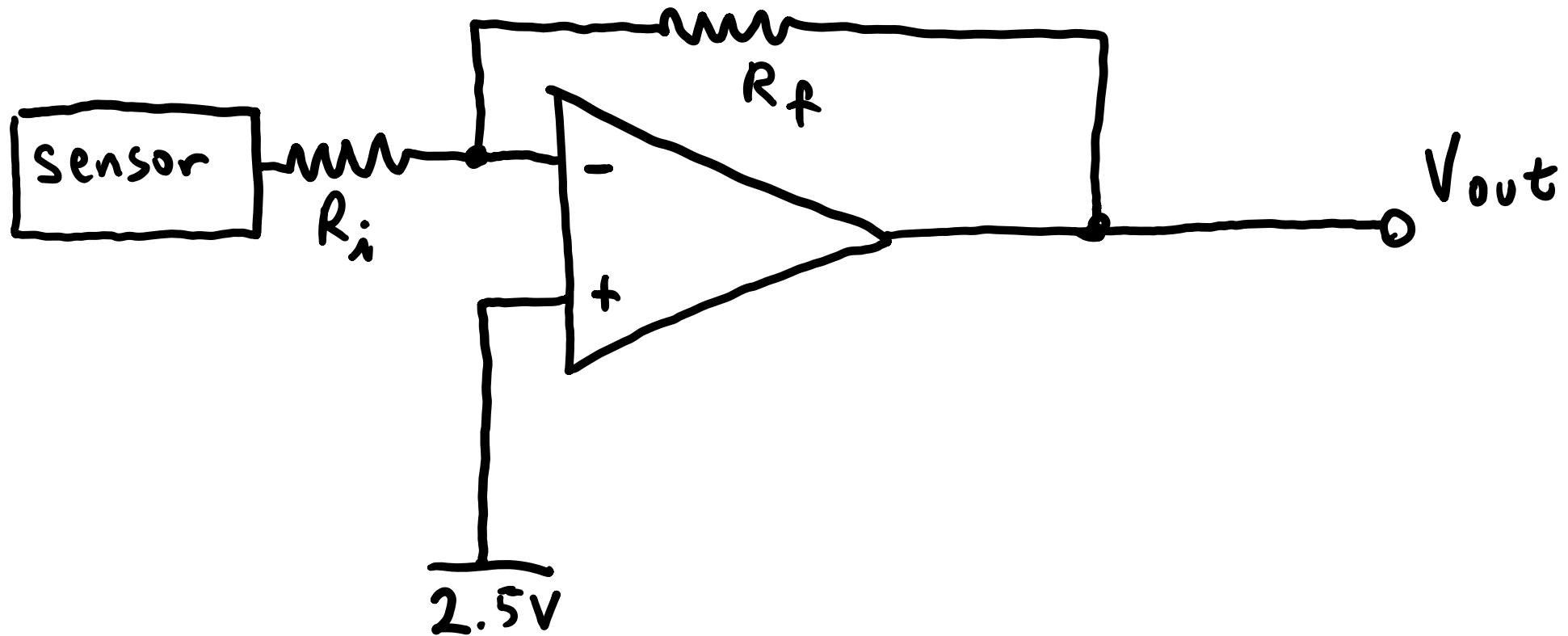



# The inverting op-amp circuit

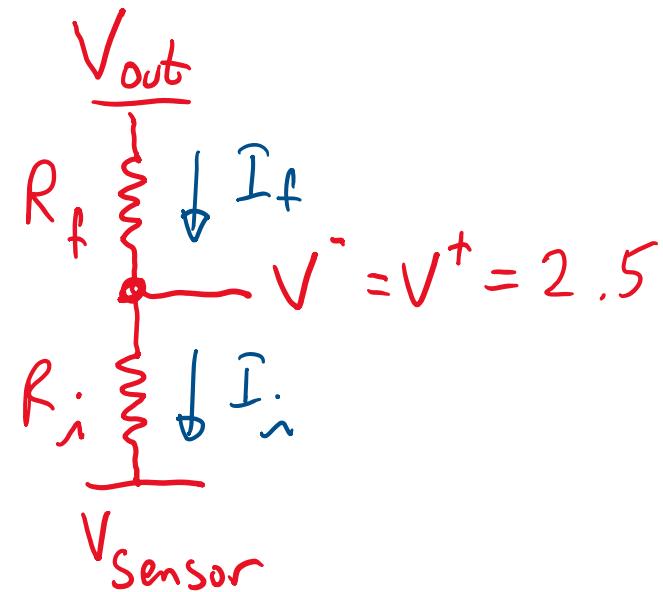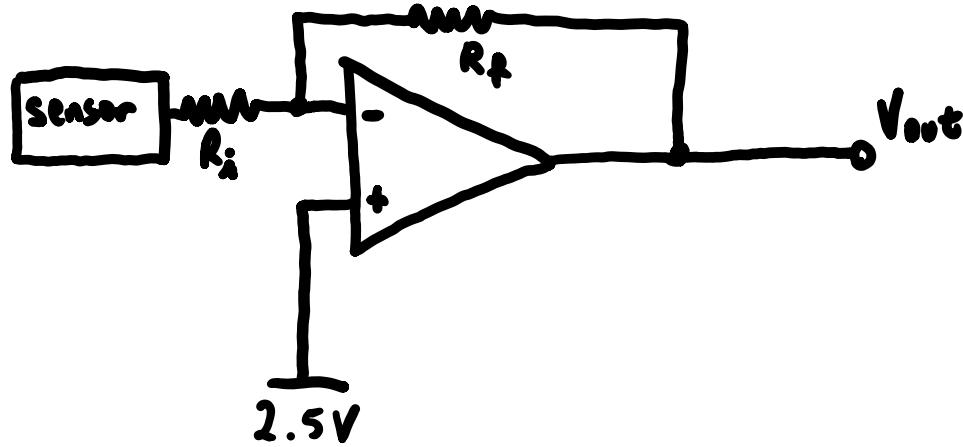

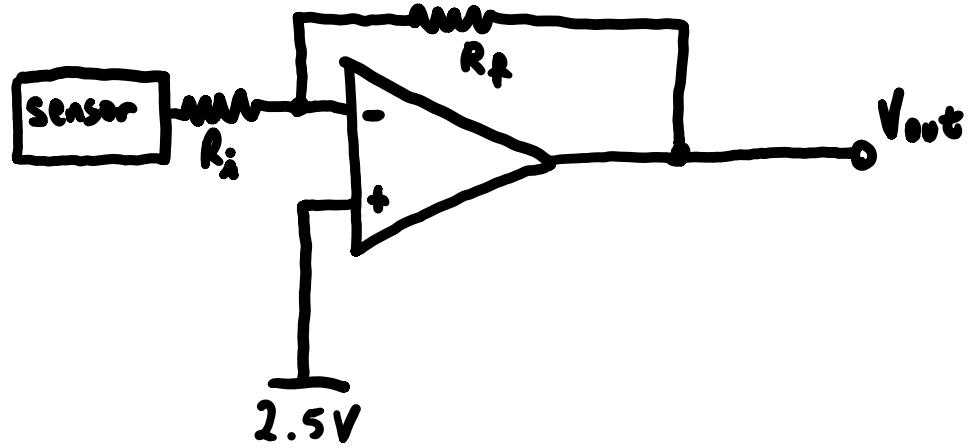
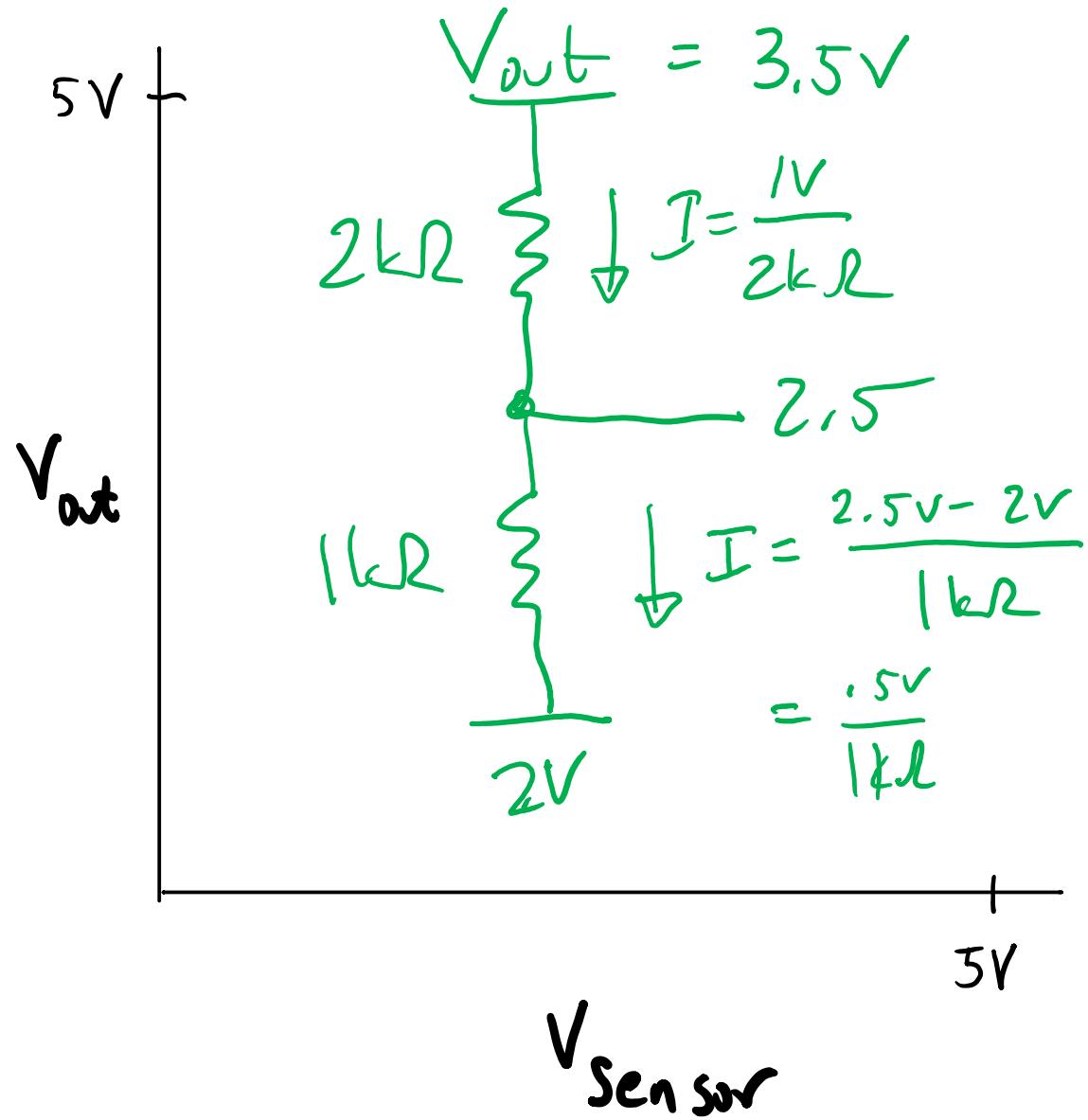
$$2k\Omega = R_f \downarrow I_f \quad V^+ = V^+ = 2.5$$
$$1k\Omega = R_i \downarrow I_i \quad V_{Sensor}$$




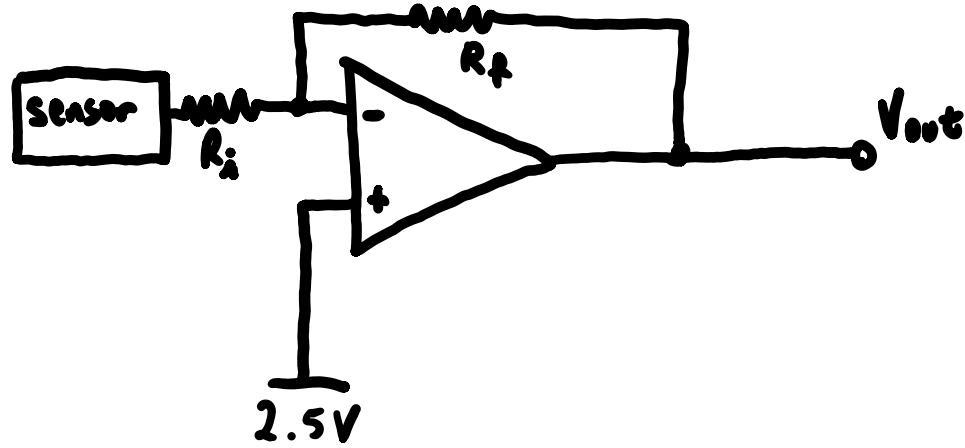


$$2k\Omega = R_f \downarrow I_f \quad V^+ = V^+ = 2.5$$


$$1k\Omega = R_i \downarrow I_i \quad V_{Sensor}$$

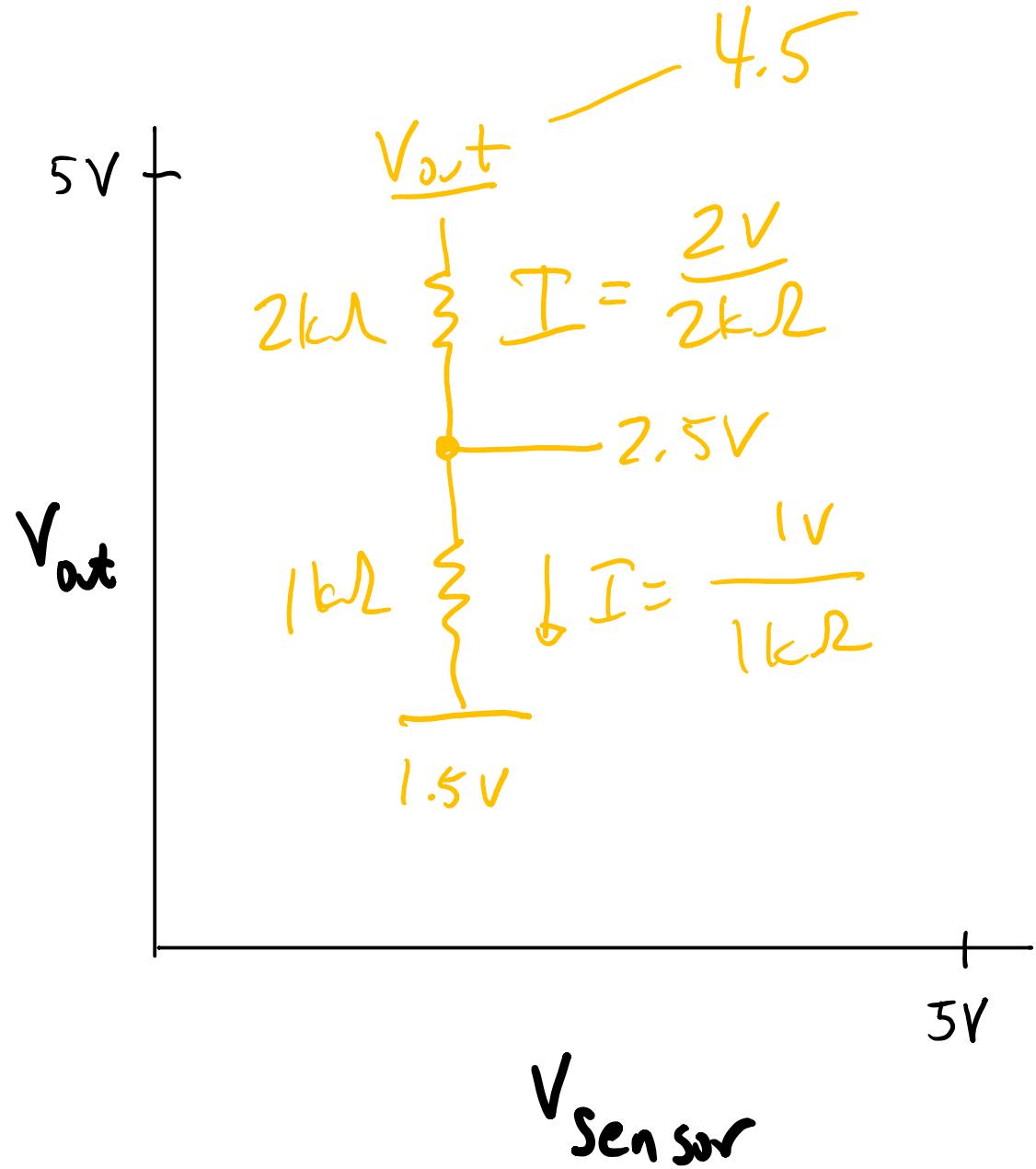
Two equations are shown. The first relates the output voltage \$V\_{out}\$ to the feedback resistor \$R\_f\$ and current \$I\_f\$. The second relates the sensor voltage \$V\_{Sensor}\$ to the input resistor \$R\_i\$ and current \$I\_i\$.



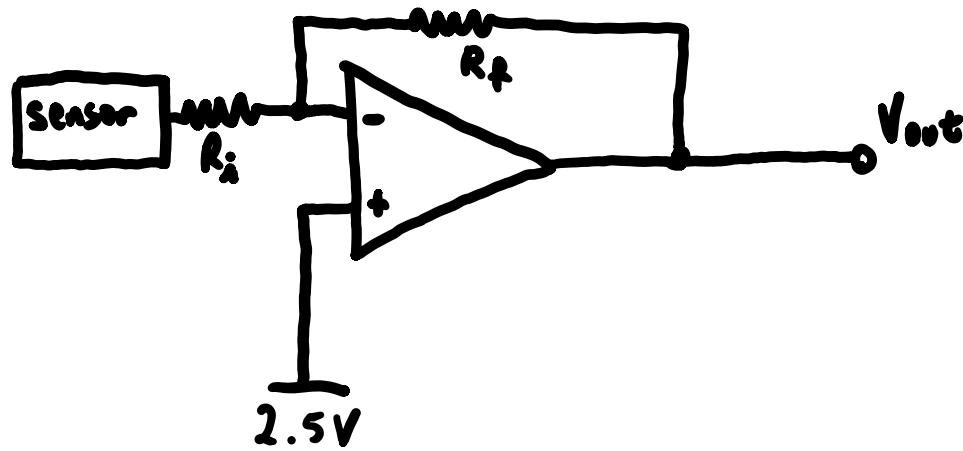
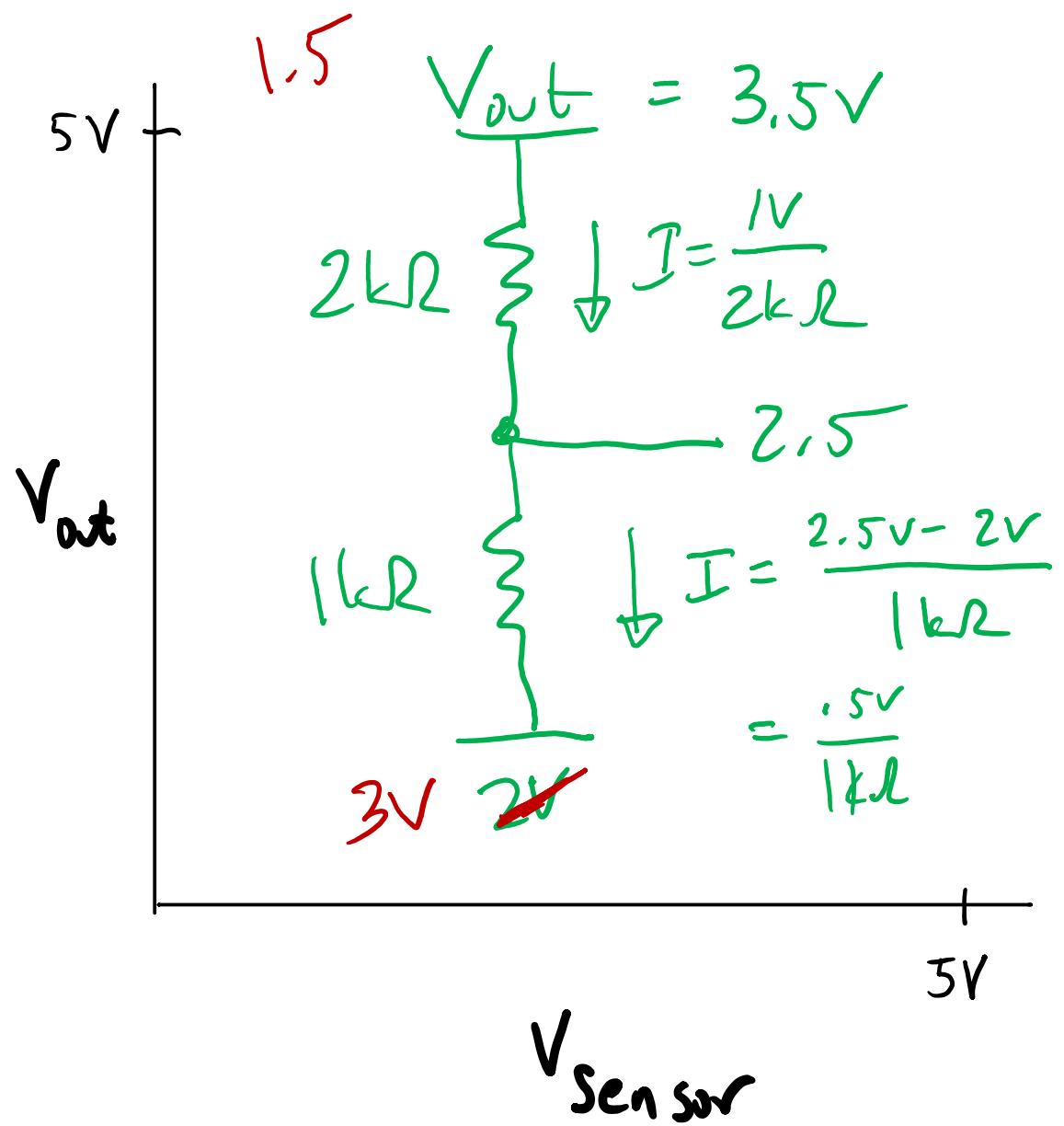
$$2kR = R_f \frac{V_{out}}{I_f} \quad V^- = V^+ = 2.5$$



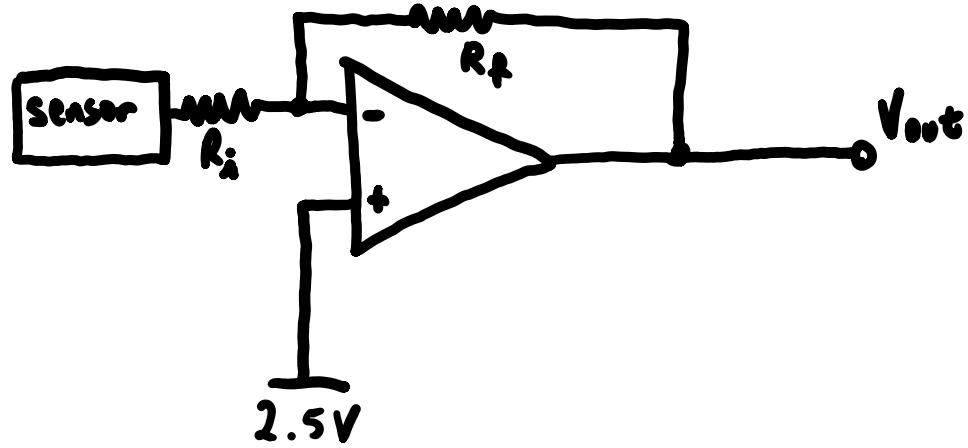

$$2k\Omega = R_f \downarrow I_f \quad V^+ = V^+ = 2.5$$
$$1k\Omega = R_i \downarrow I_i \quad V_{Sensor}$$

