

# Voltage Dividers and Analog-to-Digital Conversion

# How hot is it?




Hint: it's 2173


# Agenda

- Review voltage dividers
- Show a useful example related to sensing
- Analog-to-digital conversion

# Sensor interfaces

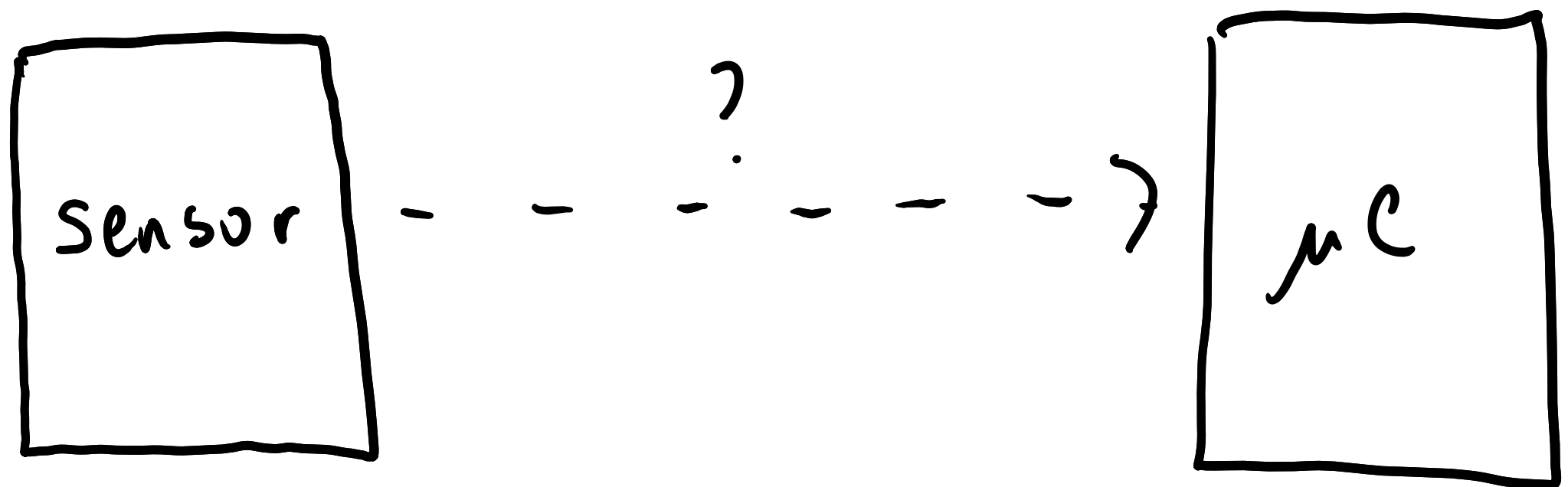

# Sensor interfaces

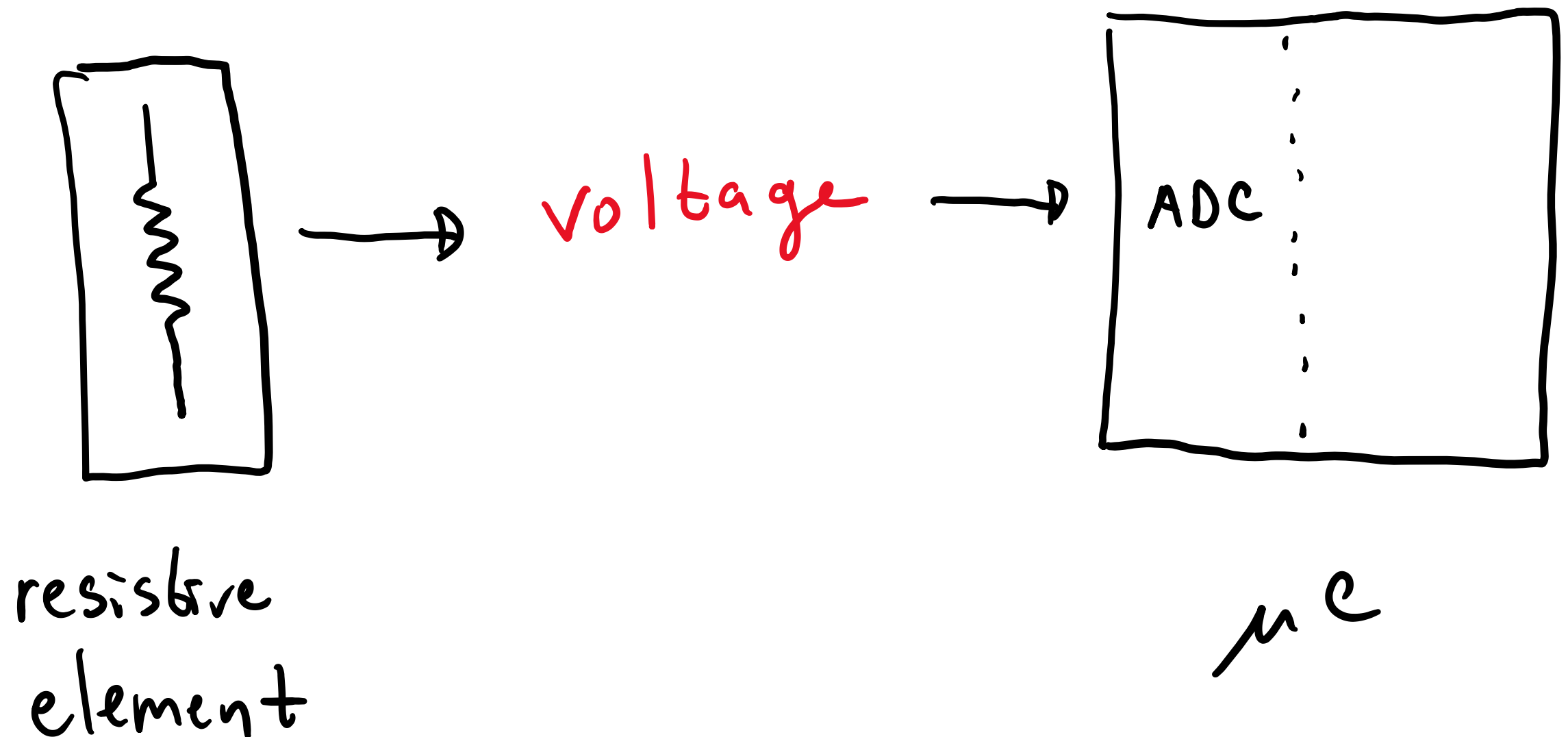


# The voltage divider

(The simplest case)

- When no current flows from the junction, for the “simple” voltage divider shown, the *output voltage* is:

$$V_{out} = \frac{R_1}{R_1 + R_2} \cdot V^+$$

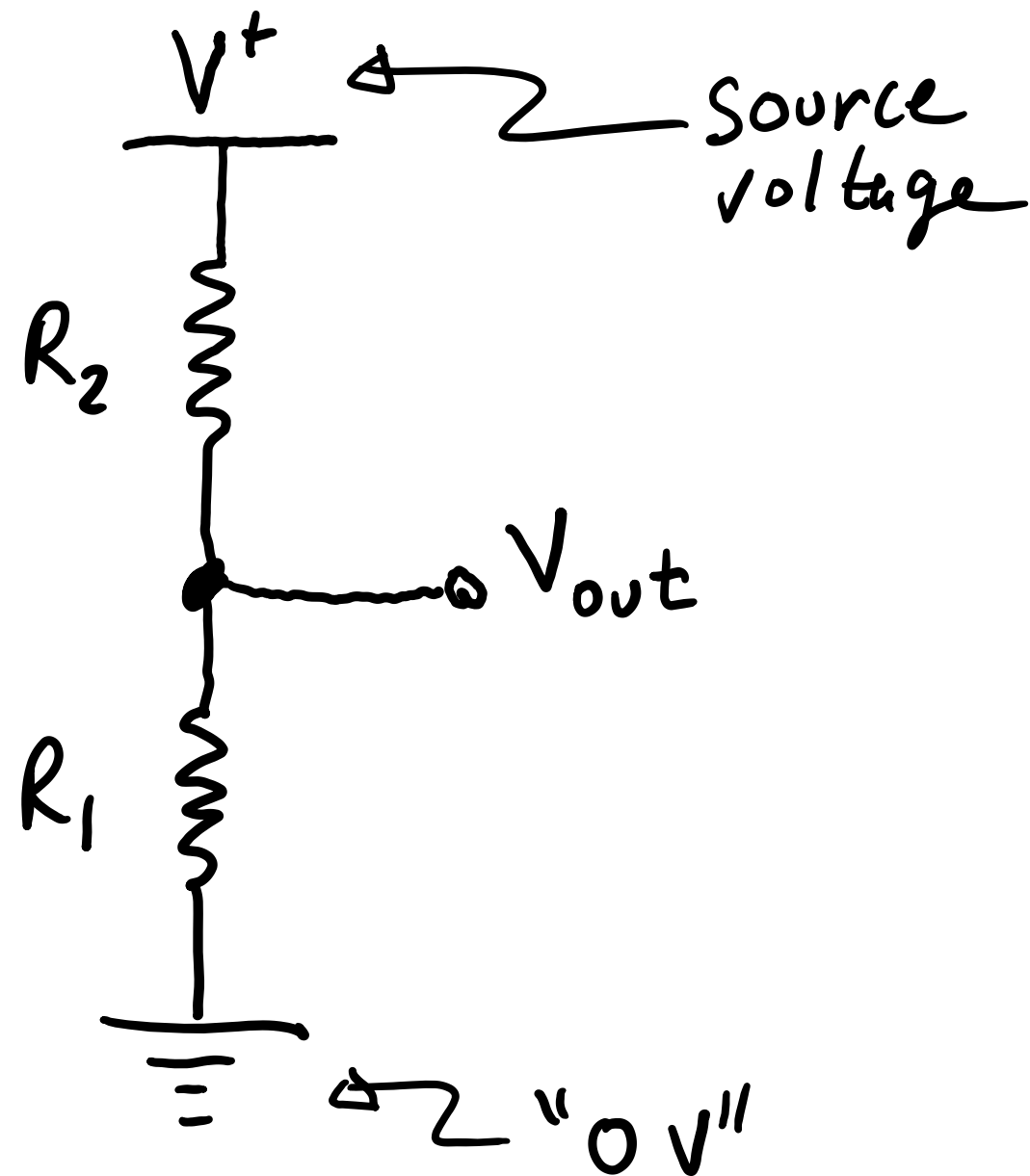That is, the output voltage is just a linear interpolation of the source voltage




# The voltage divider

(The simplest case)

$$\sum I_A = 0$$
$$\therefore I_1 = I_2$$
$$\frac{V_{out}}{R_1} = \frac{V^+ - V_{out}}{R_2}$$
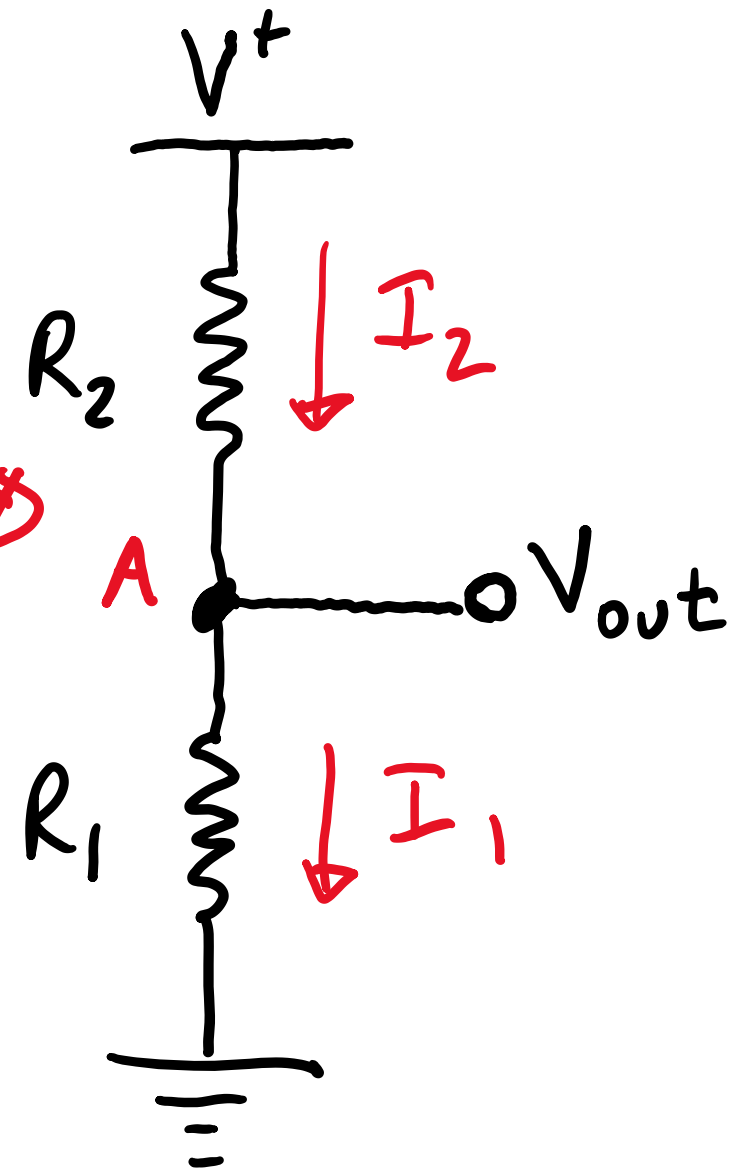
$$V_{out} = \frac{R_1}{R_1 + R_2} \cdot V^+$$




# The voltage divider

- Be careful if the low voltage side is not ground!

$$V_{out} = V^- + \frac{R_1}{R_1 + R_2} \cdot (V^+ - V^-)$$

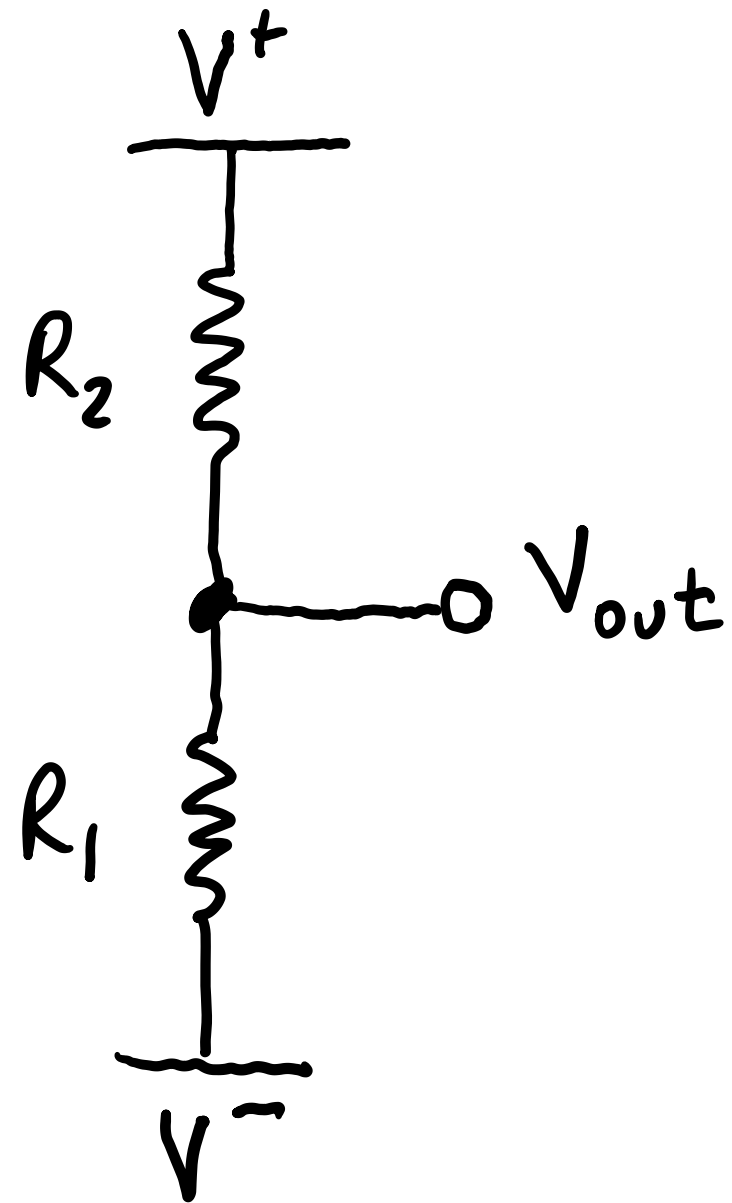(This will show up later this week, but it's generally best to go back to the current analysis.)





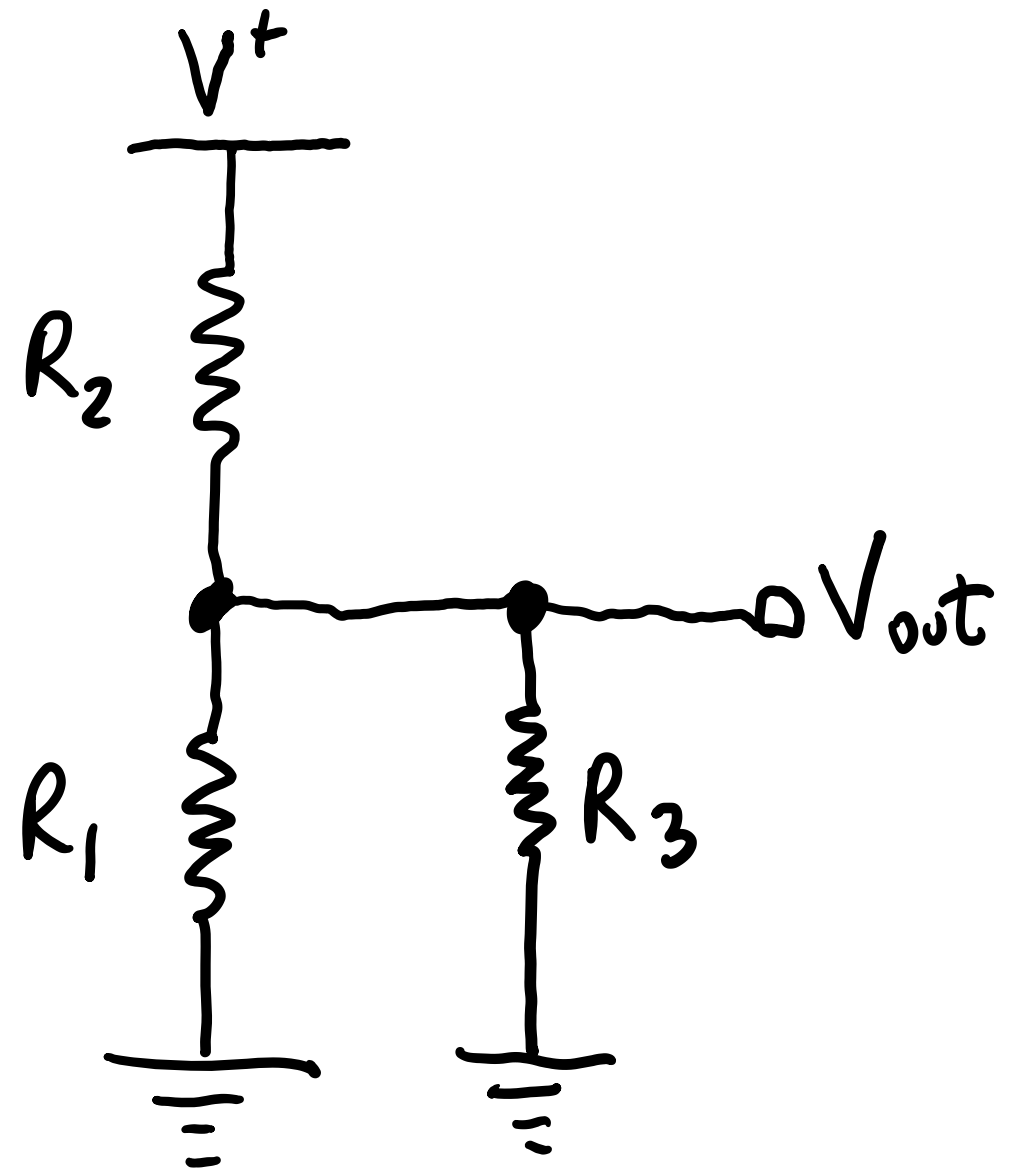
# The voltage divider

- Be careful that no current flows out at the junction!

$$V_{out} = \frac{R_1}{R_1 + R_2} \cdot V^+$$




# The voltage divider

$$\sum I_A = 0.$$

$$\therefore I_2 = I_1 + I_3$$
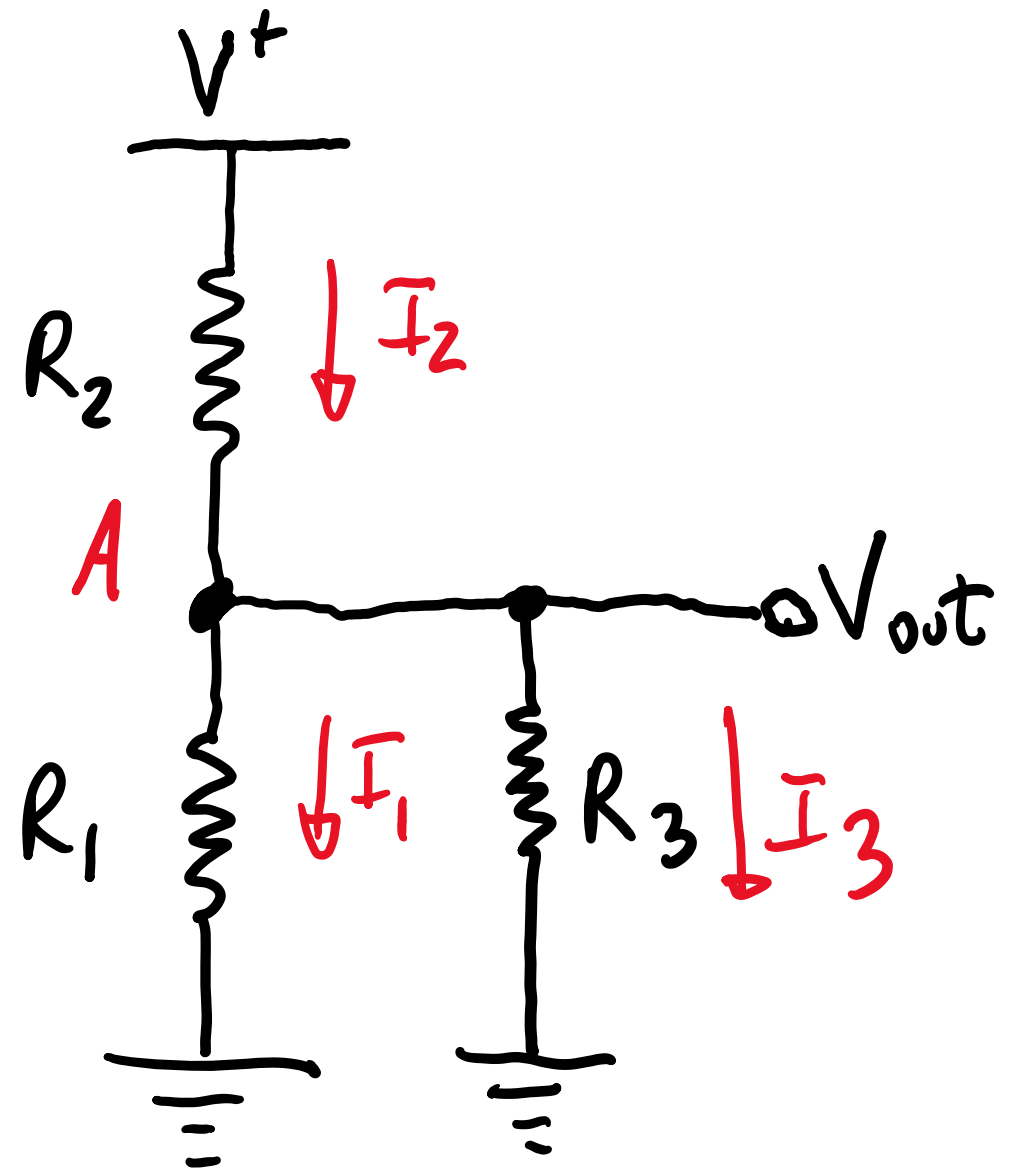
$$V_{out} = \frac{R_1}{R_1 + R_2} \cdot V^+$$



You can always find the voltage at point A, but be careful not to apply the standard equation without verifying the assumptions!

# How is this useful?

- Many sensors react to their environment by changing resistance
  - Photoresistors
  - Humidity sensors
  - Thermistors
  - Accelerometers
  - Many, many more

# Thermistors

- The resistance of a thermistor is a function of temperature, for example,

$$R = R_0 e^{-B\left(\frac{1}{T_0} - \frac{1}{T}\right)}$$

where the temperatures are in Kelvin and B is some constant specified by the manufacturer.  $R_0$  is the nominal resistance at the reference temperature,  $T_0$ .

# How is this useful?


(Microcontrollers can't read resistance directly.)

# How is this useful?

(Microcontrollers can't read resistance directly.)

**They do, however, read voltages.**
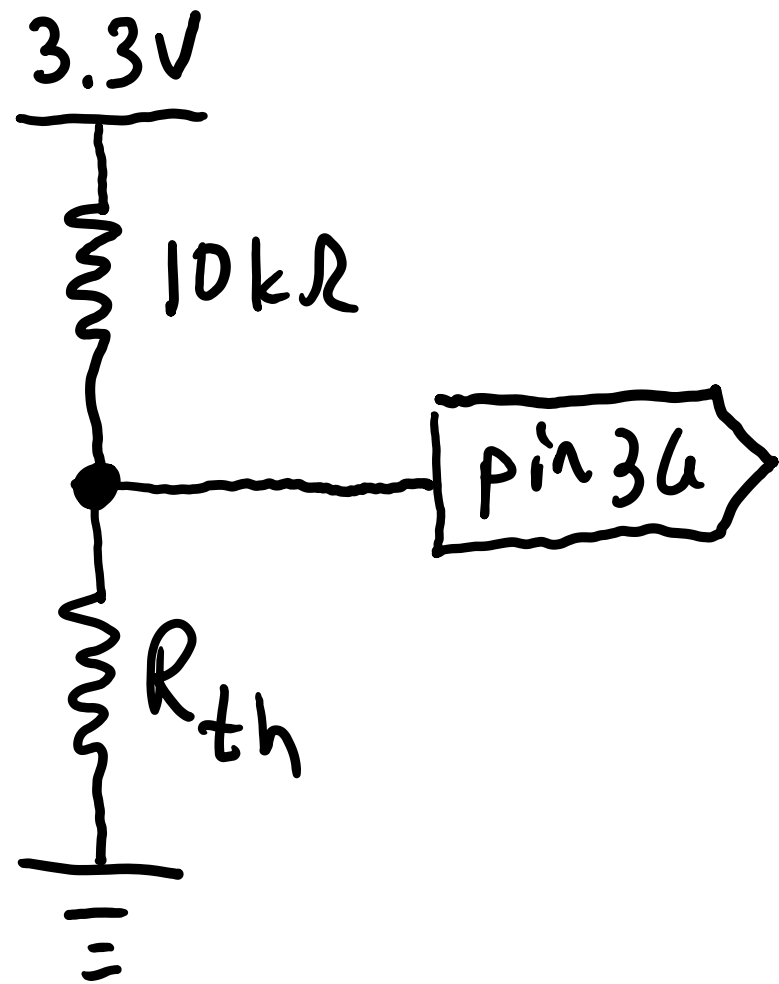
# So let's put the thermistor in a voltage divider!



$$V_{out} = \frac{R_{th}}{R_{th} + 10k\Omega} * 3.3V$$

# So...

Let  $T = 25\text{ C}$ . What is the voltage at the junction of the voltage divider?

$$R = R_0 e^{-B\left(\frac{1}{T_0} - \frac{1}{T}\right)}$$

$$V_{out} = \frac{R_{th}}{R_{th} + 10k\Omega} * 3.3V$$



# From the datasheet

- $T_0 = 25\text{ C}$ ;  $R_0 = 10\text{ kOhms}$ ;  $B = 4300\text{ K}$

Temperature (C)	Resistance (ohms)
17.5	14514
20	12792
22.5	11298
25	10000
27.5	8869
30	7881
32.5	7017

# So...

Let  $T = 25\text{ C}$ . What is the voltage at the junction of the voltage divider?

$$R = R_0 e^{-B\left(\frac{1}{T_0} - \frac{1}{T}\right)} = 10\text{ k}\Omega$$

$$V_{out} = \frac{R_{th}}{R_{th} + 10\text{ k}\Omega} * 3.3\text{ V} = \frac{1}{2} * 3.3\text{ V}$$

$10\text{ k}\Omega$   $= 10\text{ k}\Omega$

$$= \boxed{1.65\text{ V}}$$


# So...

Let  $T = 30\text{ C}$ . What is the voltage at the junction of the voltage divider?

$$R = R_0 e^{-B\left(\frac{1}{T_0} - \frac{1}{T}\right)} = 7881\ \Omega$$


$$V_{out} = \frac{R_{th}}{R_{th} + 10k\Omega} * 3.3V$$

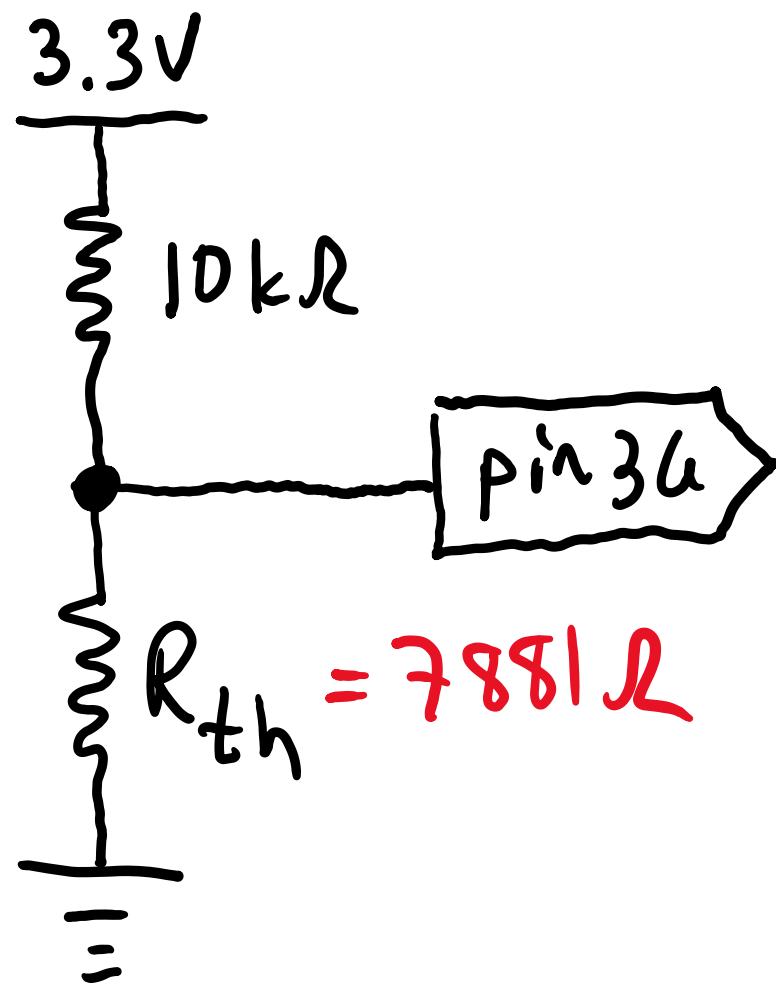**Will  $V_{out}$  be higher or lower than 1.65 V?**



$$V_{out} = \frac{R_{th}}{R_{th} + 10k\Omega} * 3.3V$$
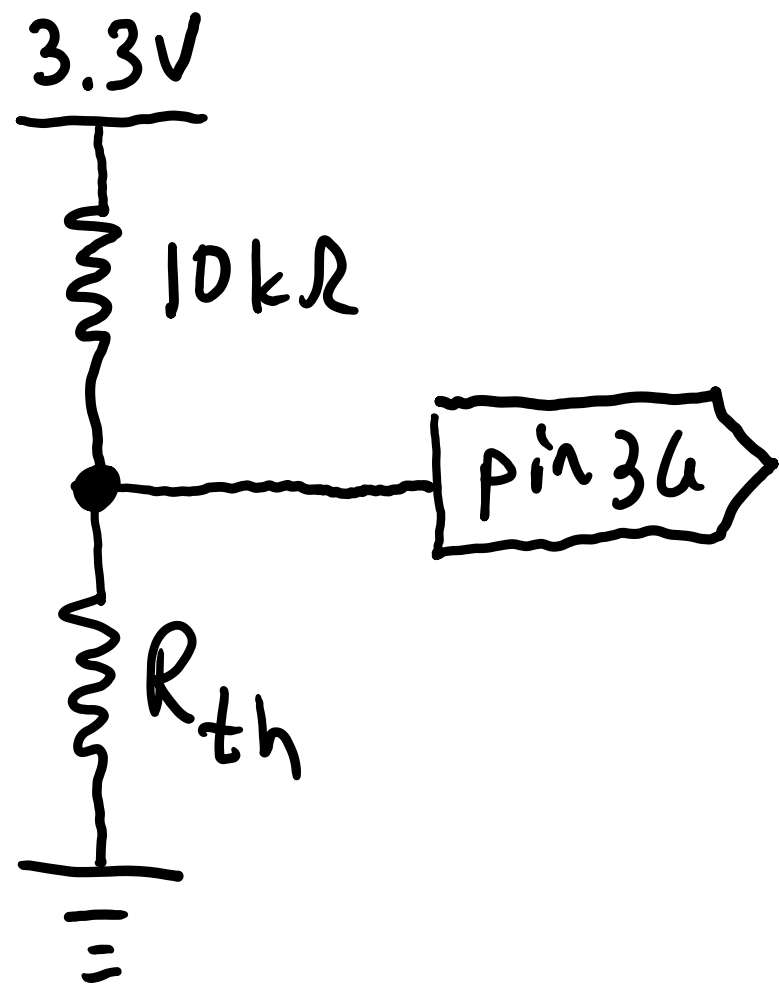
# So let's put the thermistor in a voltage divider!




$$V_{out} = \frac{R_{th}}{R_{th} + 10k\Omega} * 3.3V$$

If  $R_{th} \downarrow$ , there is less voltage drop than across the 10kΩ resistor, so  $V_{out} \downarrow$

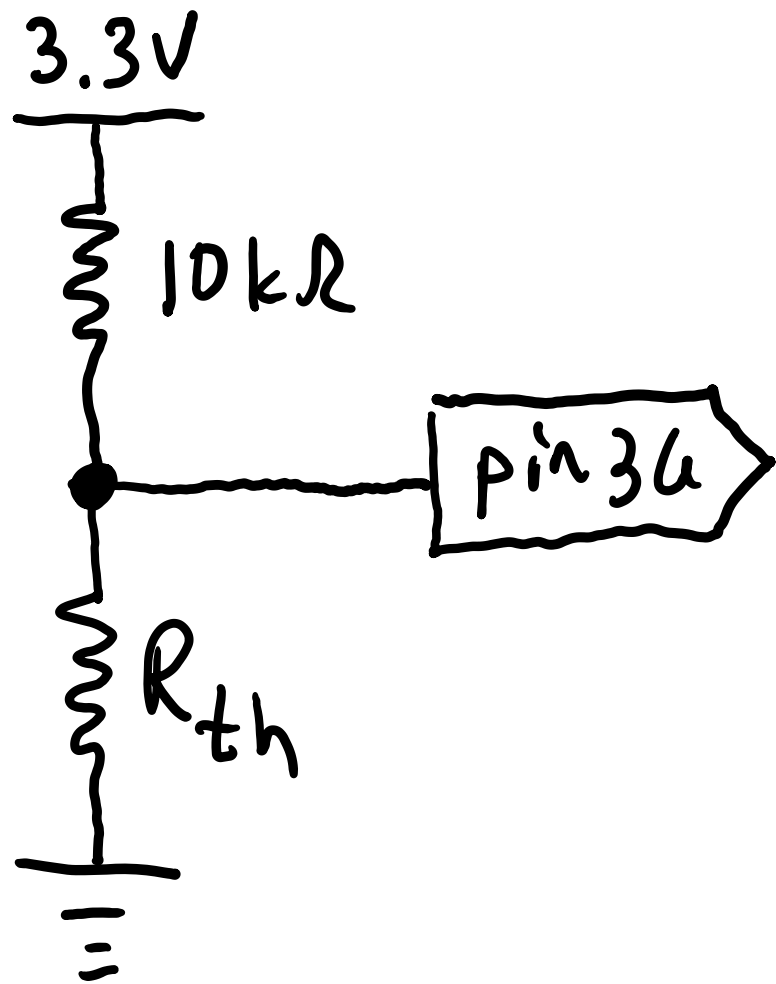
# OK, so now what?

Microcontrollers use numbers, not voltage!



$$V_{out} = \frac{R_{th}}{R_{th} + 10k\Omega} * 3.3V$$


# Analog-to-Digital Conversion (ADC)

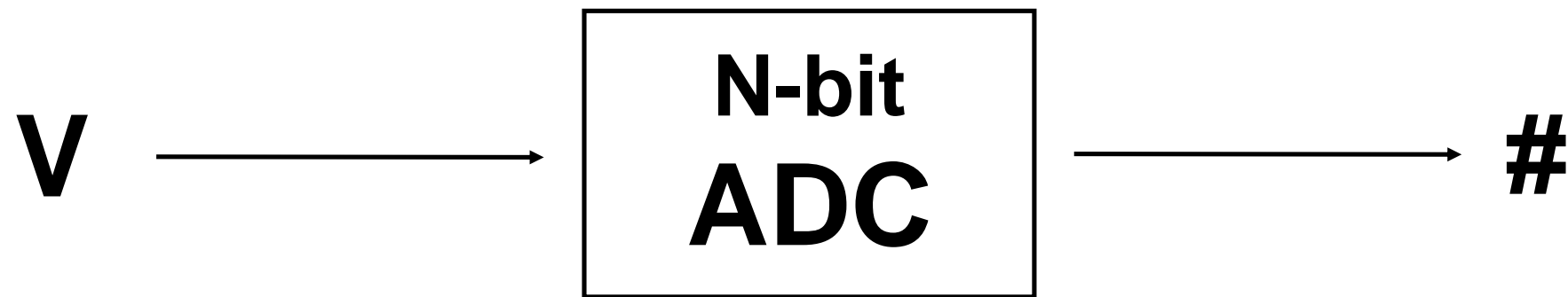

$$\text{result} = \text{floor}\left[\frac{V}{V_{ref}} \times 2^N\right]$$

With one caveat: if  $V = V_{ref}$ , the result can't be  $2^N$ . Why?

# Analog-to-Digital Conversion (ADC)

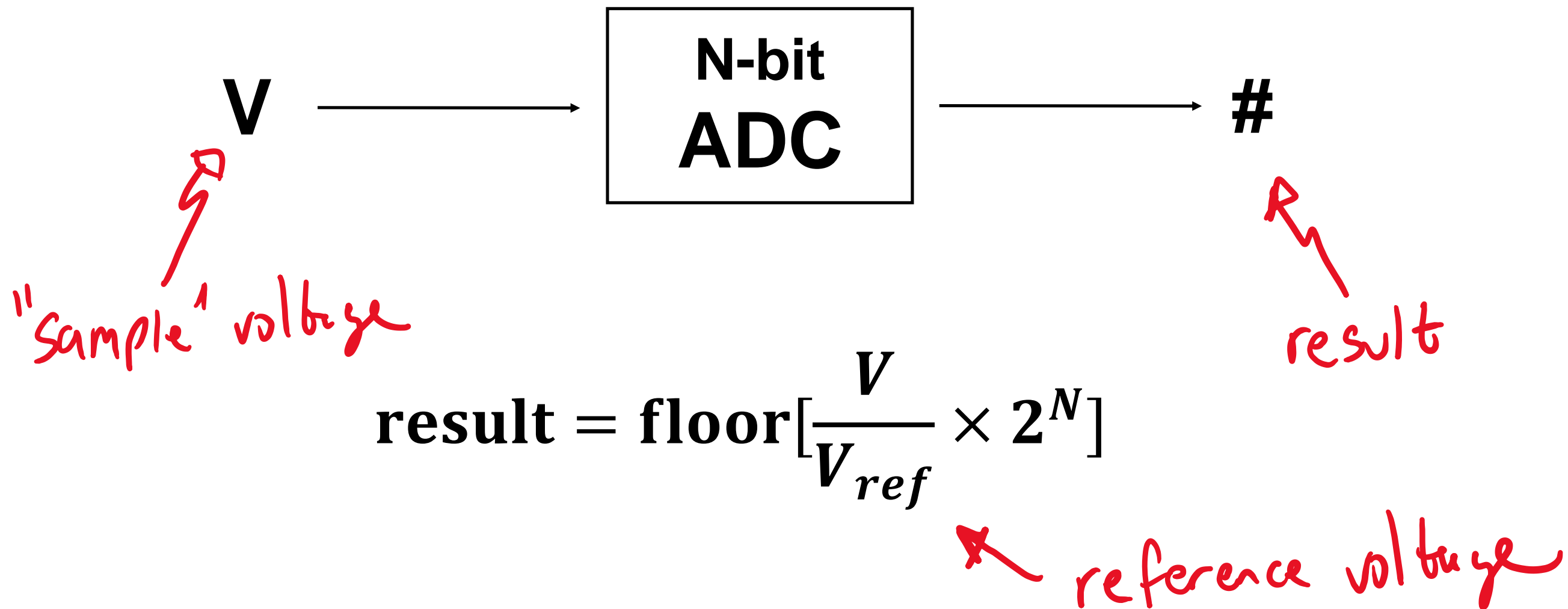


With one caveat: if  $V = V_{ref}$ , the result can't be  $2^N$ . Why?



# ADC: What magic is this?

$$\text{result} = \text{floor}\left[\frac{V}{V_{ref}} \times 2^N\right]$$


Let  $N=2$ ;  $V_{ref} = 5V$

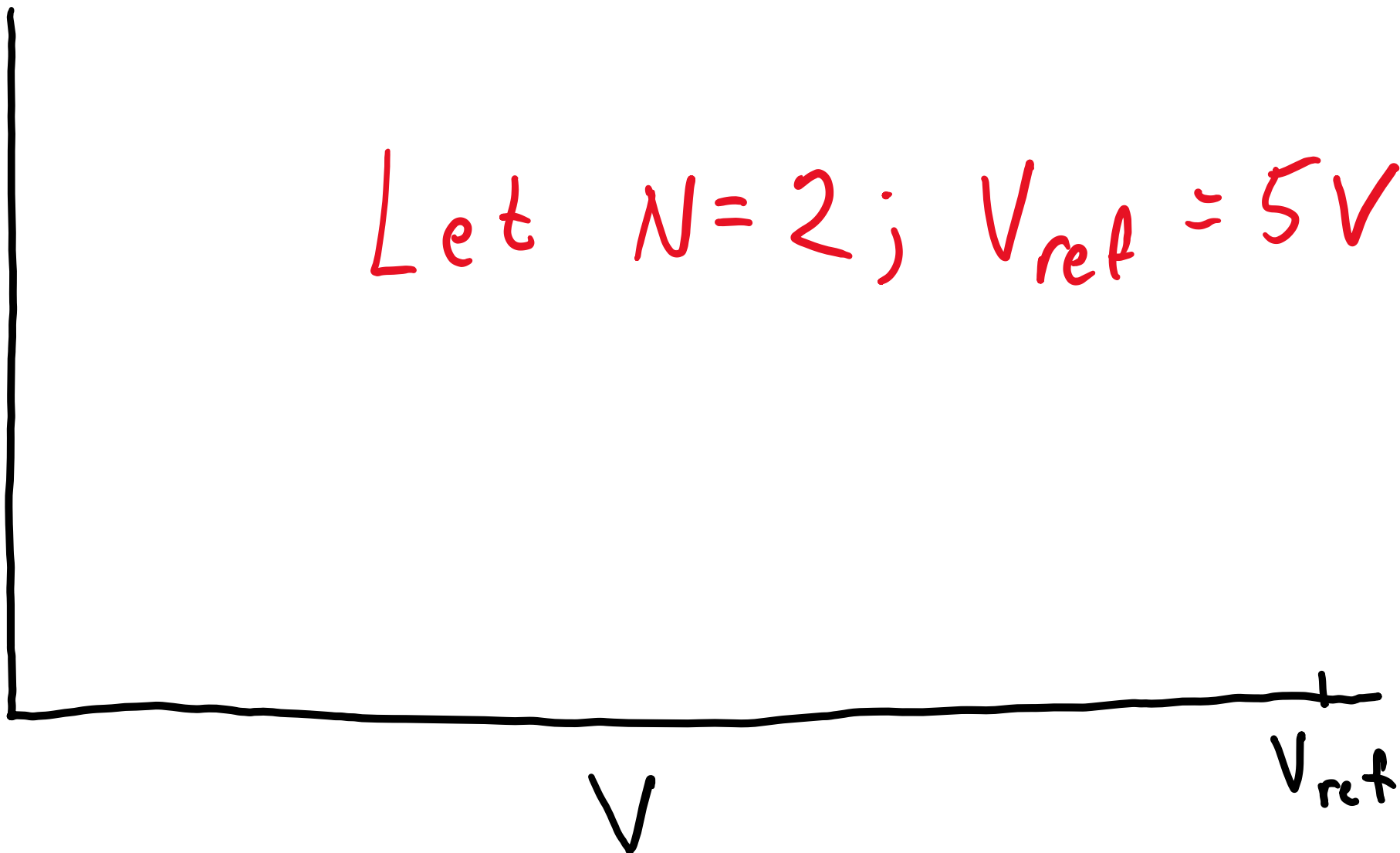
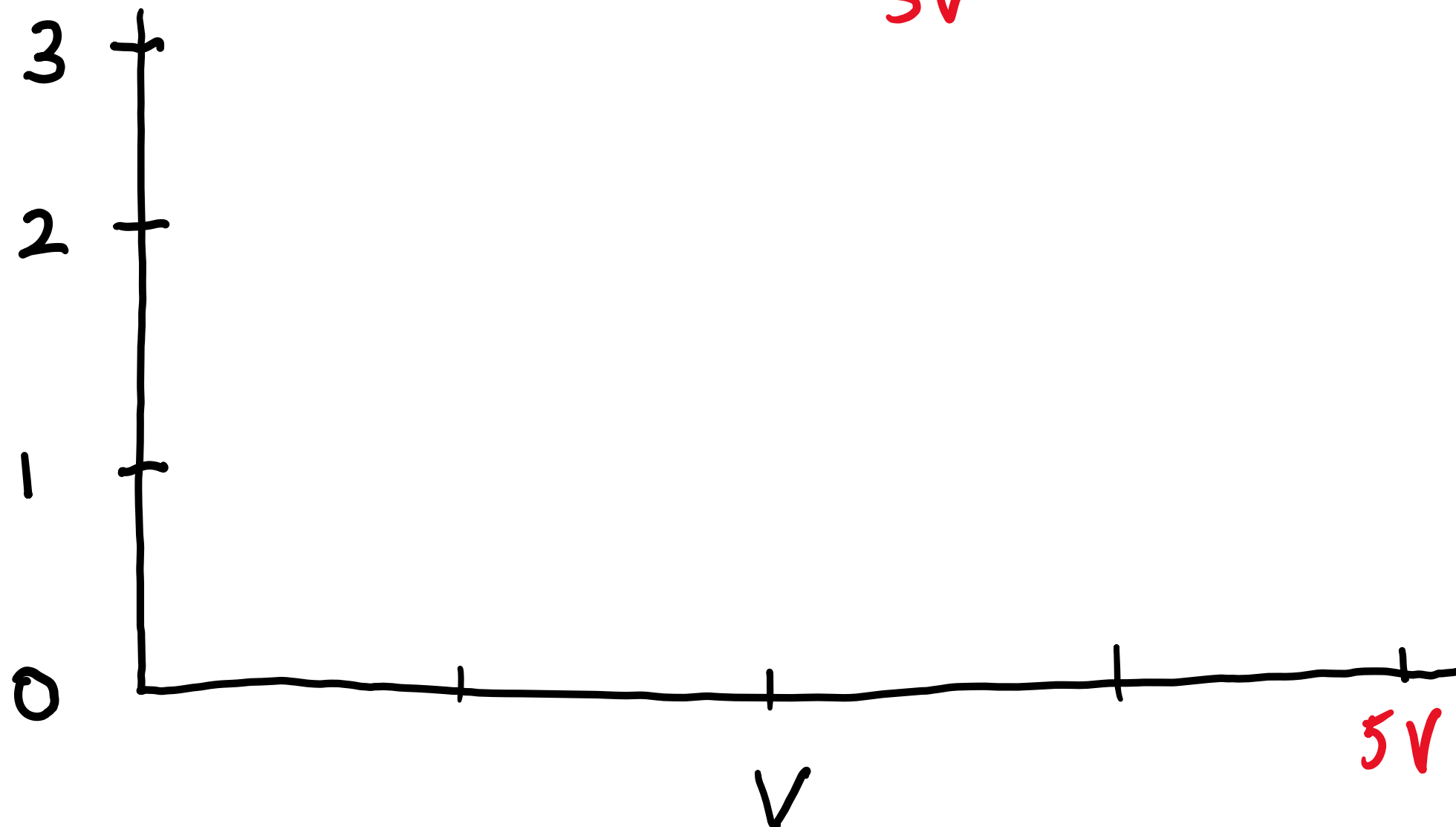
# ADC: What magic is this?


$$\text{result} = \text{floor}\left[\frac{V}{V_{\text{ref}}} \times 2^N\right]$$

~~$V_{\text{ref}}$~~  5V       ~~$2^N$~~  4



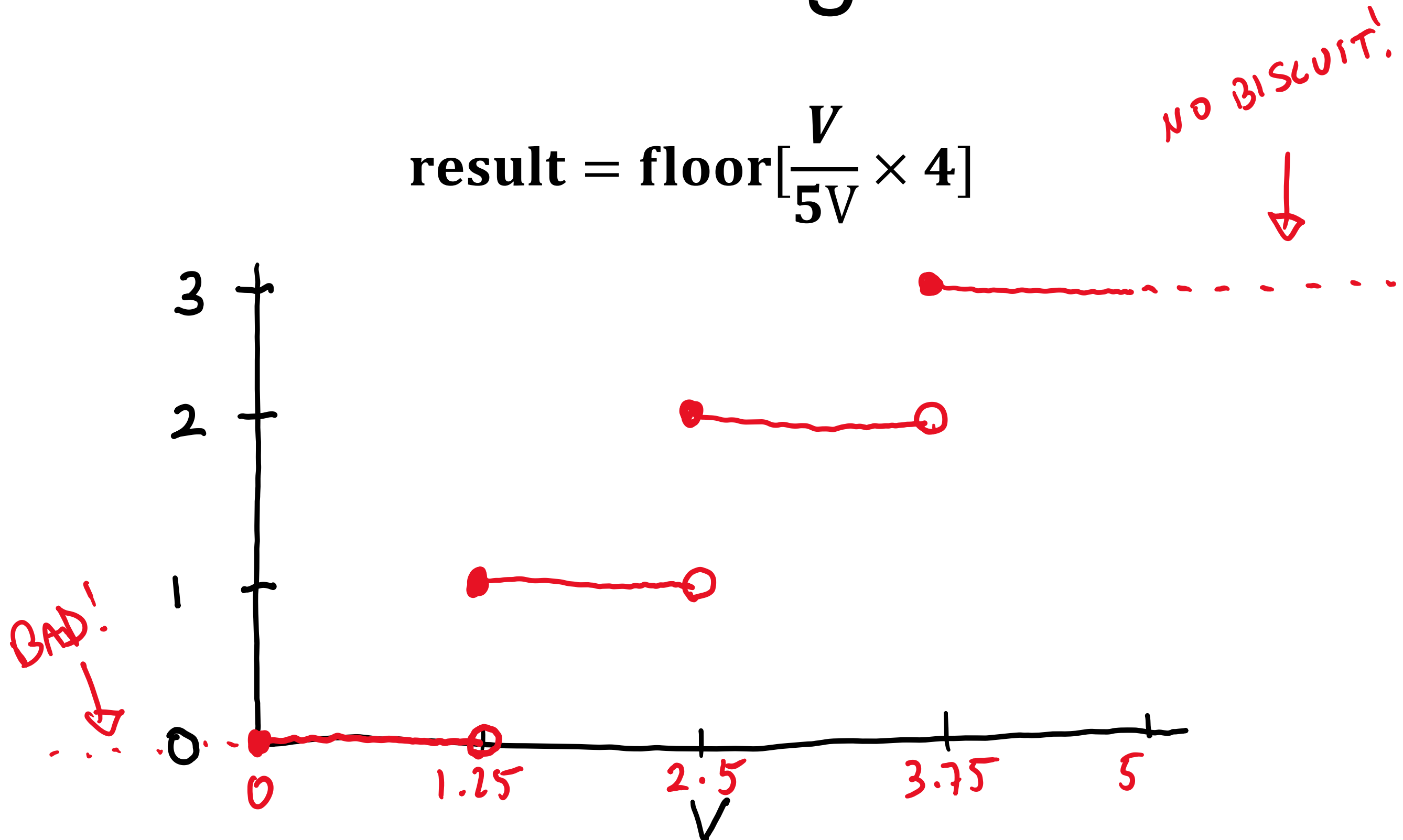
# ADC: What magic is this?

$$\text{result} = \text{floor}\left[\frac{V}{5V} \times 4\right]$$



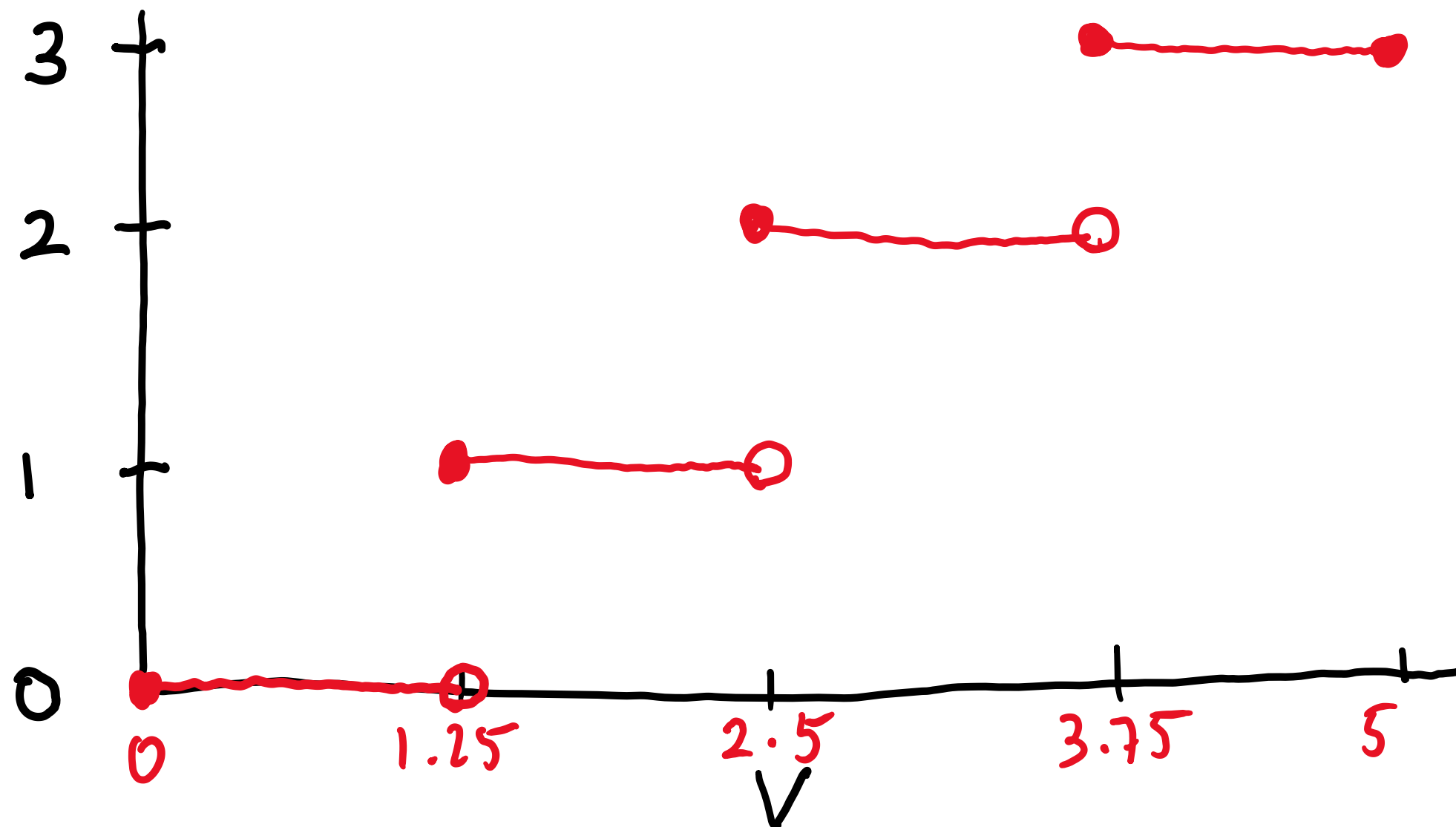
# Working backwards

$$\text{result} = \text{floor}\left[\frac{V}{5V} \times 4\right]$$



# Now it's your turn: 2173

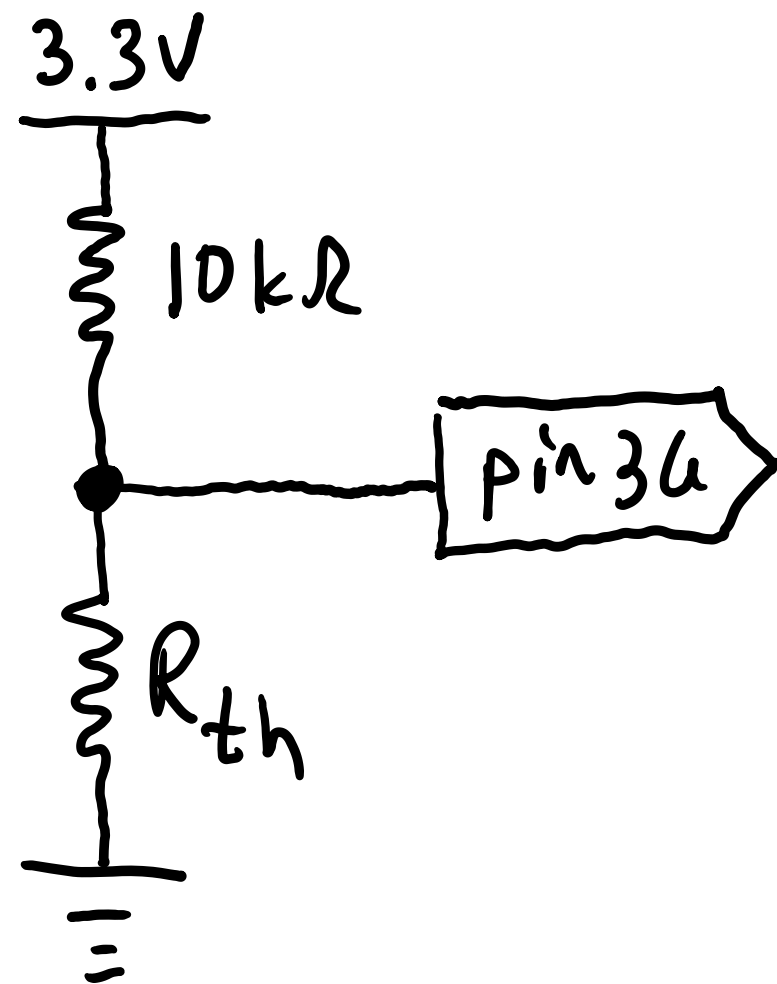

$$V_{out} = \frac{R_{th}}{R_{th} + 10k\Omega} * 3.3V$$

Temperature (C)	Resistance (ohms)
17.5	14514
20	12792
22.5	11298
25	10000
27.5	8869
30	7881
32.5	7017

$$\text{result} = \text{floor}\left[\frac{V}{V_{ref}} \times 2^N\right]$$