

Quiz 3

⚠ This is a preview of the published version of the quiz

Started: Feb 8 at 8:27am

Quiz Instructions

You may use notes, books, and canvas resources. You may not use online calculators or any simulation tools.

Write your answer in reasonable units, e.g., 2 mA instead of 0.002 A (but as always, you won't get marked off if you don't, so long as the answer is correct). Include units! **You will use lose points for missing units.**

The number of significant digits is the number of digits after the first non-zero digit.

The following are to three significant digits:

- 0.0456 A
- 45.6 mA

The following are not to three significant digits:

- 0.045 A (it only has two significant digits)
- 45.673 mA (it has five significant digits)

As always, canvas will give you a nominal score that I will manually adjust on saturday.

Question 1

1 pts

Which of the following expressions is an accurate way to calculate the power dissipated by a resistor? Select all that apply.

☒ $P = IV$

☐ $P = I(R^2)$

I^2R , but not IR^2

☐ $P = (V^2)R$


V^2/R , but not V^2R

☐ $P = V / I$

$R = V/I$, but not $P = V/I$

Question 2

1 pts

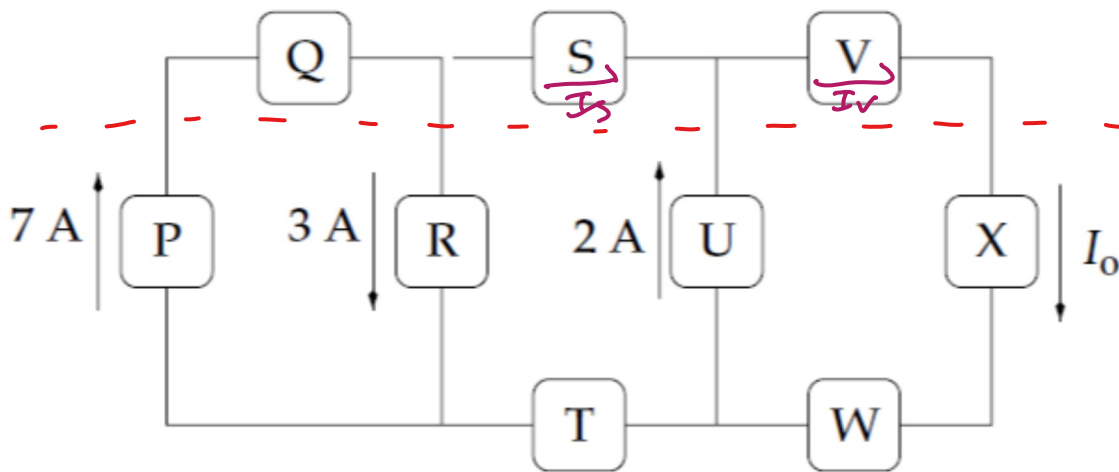In the figure, what is the current, I_o ?

$$\underbrace{7A + 2A}_{\text{"up"}} = \underbrace{3A + I_o}_{\text{"down"}} \Rightarrow \boxed{I_o = 6A}$$

longer version

$$I_s = 7A - 3A = 4A$$

$$I_v = I_s + 2A = 6A$$

$$I_x = I_v = \boxed{6A}$$

Question 3


1 pts

What is the current, I_o , through the 10kOhm resistor?

should be 10k

$$I_{10k} = \frac{\Delta V}{R} = \frac{12V - 10V}{10k} = \boxed{0.2A}$$

(if you used 10k to get 0.2mA, that's fine.)

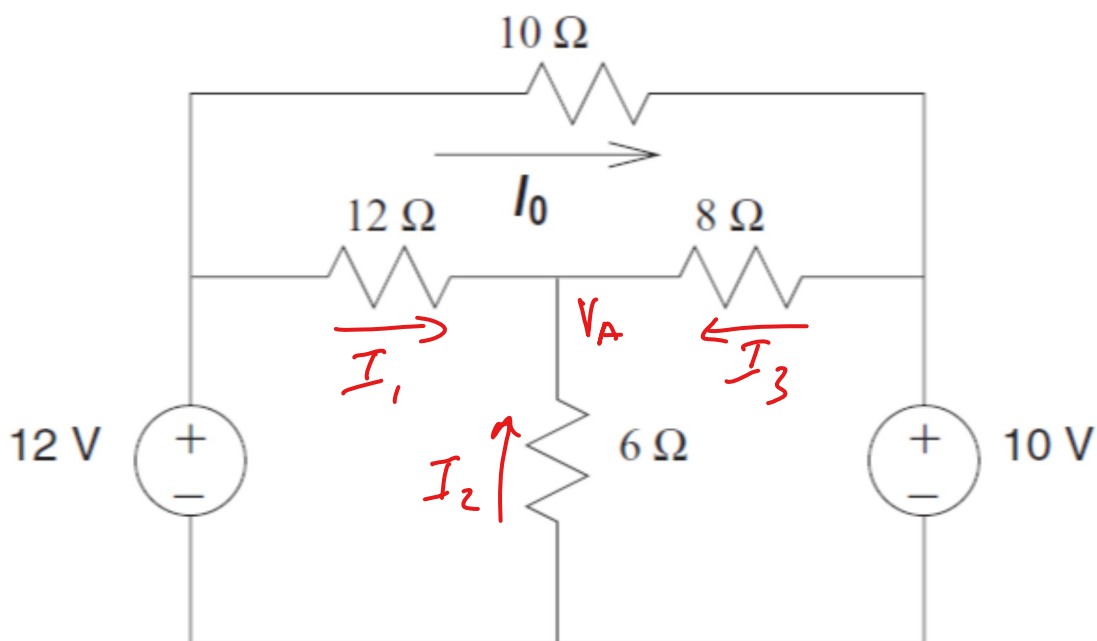

Question 4

1 pts

In the figure in the previous problem, what is the voltage at the junction of the 6, 8, and 12 Ohm resistors?

☐ 2V

☐ 4V

☒ 6V

☐ a dollar...

$$\frac{12 - V_A}{12\Omega} + \frac{0 - V_A}{6\Omega} + \frac{10 - V_A}{8\Omega} = 0$$

$$\Rightarrow \frac{12V}{12\Omega} + \frac{10V}{8\Omega} = \left[\frac{1}{12\Omega} + \frac{1}{6\Omega} + \frac{1}{8\Omega} \right] V_A$$

$$\frac{9}{4} \left(\frac{V}{\Omega} \right) = \left[\frac{2 + 4 + 3}{24\Omega} \right] V_A$$

$$V_A = \frac{24 \cdot 9}{4 \cdot 9} V = \boxed{6V}$$

Question 5

1 pts

What sized resistor, R , would be needed to make $V_A = 3.3$ V. Write your answer to the nearest kOhm.



$$V_A = \frac{20k\Omega}{20k\Omega + R} \cdot 5V$$

$$\Rightarrow R + 20k\Omega = \frac{5V}{3.3V} \cdot 20k\Omega$$

$$R = \frac{5}{3.3} \cdot 20k\Omega - 20k\Omega = 10,303\Omega$$

ROUNDS TO $10k\Omega$

Question 6


1 pts

Given the circuit below, how much power does the 6 kOhm resistor dissipate? Write your answer to three significant digits.


$$P = I^2 R \text{ or } \frac{V^2}{R}. \text{ In this case}$$

$$V_A = 10V \cdot \frac{3||6}{2+3||6} = 10V \cdot \frac{2}{2+2} = 5V$$

$$\text{So } P = \frac{(5V)^2}{3||6k\Omega} = \frac{(5V)^2}{4k\Omega} = 0.0041666...W = \boxed{4.17mW}$$

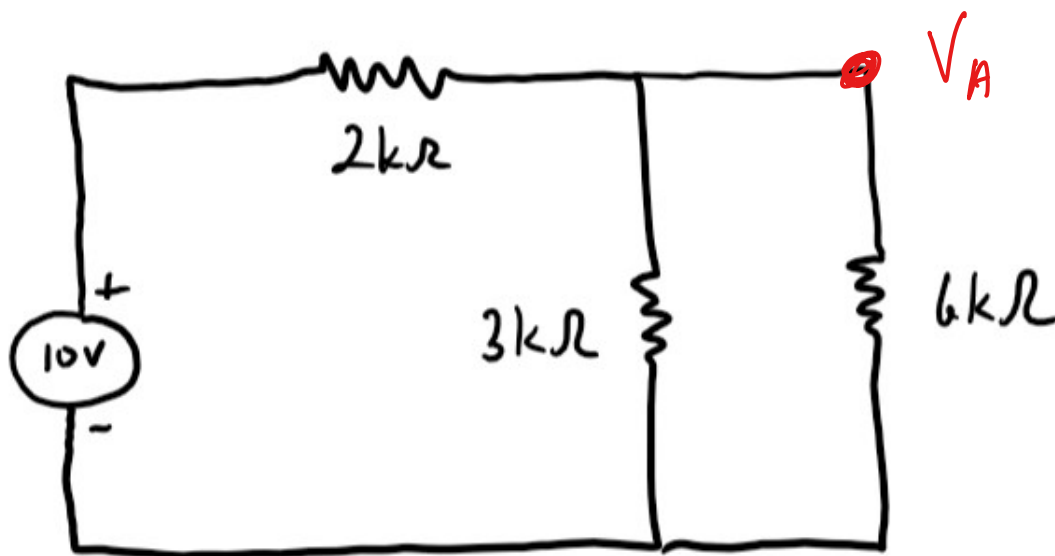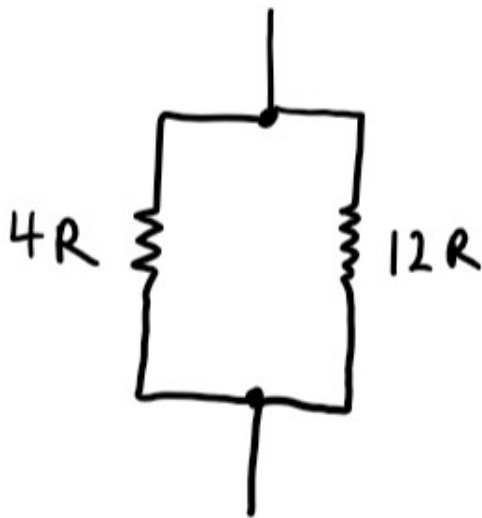**Question 7****1 pts**

What is the equivalent resistance of the two resistors, which are wired in parallel?



$$R_{eq} = \frac{4R \cdot 12R}{4R + 12R} = \frac{48R^2}{16R} = \boxed{3R}$$


(You really should have $3R$, but I accepted " $3R$ ")

Question 8

1 pts

What is the voltage, V_A , at the junction of the voltage divider?

$$V_A = 5V \cdot \frac{4k\Omega // 4k\Omega}{2k\Omega + 4k\Omega // 4k\Omega} = 5V \cdot \frac{2k\Omega}{2k\Omega + 2k\Omega} = \boxed{2.5V}$$

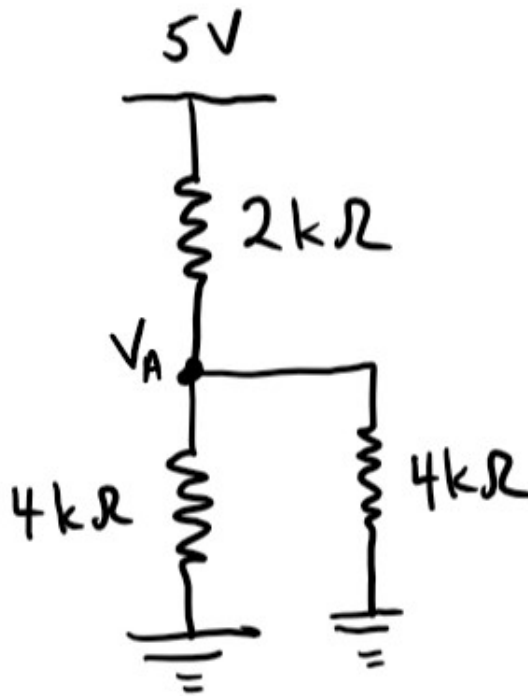


Question 9

1 pts

The circuit shown is from your microcontroller homework. How much current is flowing through the diode? Write your answer to three significant digits.

$$I_{LED} = I_{resistor} = \frac{\Delta V_R}{R} = \frac{3.3V - 1.1V}{330\Omega}$$

$$= \frac{2.2V}{330\Omega} = \boxed{6.67\text{ mA}}$$

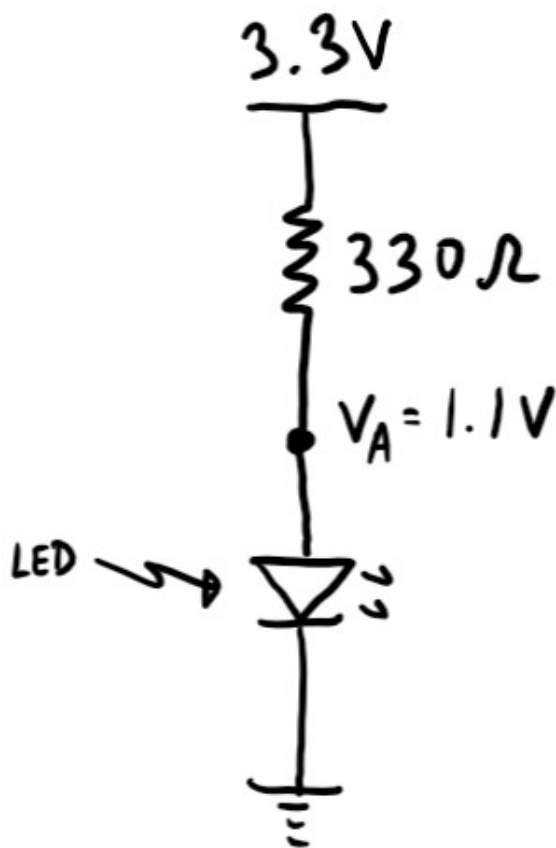**Question 10****1 pts**

How much power is dissipated by the resistors (total) in the following circuit? Write your answer to three significant digits.

long way

$$P_{\text{total}} = P_{600} + P_{400}$$

$$= I_{600} \cdot \Delta V_{600} + I_{400} \cdot \Delta V_{400}$$

but $I_{600} = I_{400} = I$

and $\Delta V_{400} + \Delta V_{600} = 5V$

so $P_{\text{total}} = I [\Delta V_{600} + \Delta V_{400}]$

$$= I \cdot 5V$$

$$I = \frac{5V}{1000\Omega} \Rightarrow P = \frac{(5V)^2}{1000\Omega}$$

$$= \boxed{25 \text{ mW}}$$

Not saved

Submit Quiz

