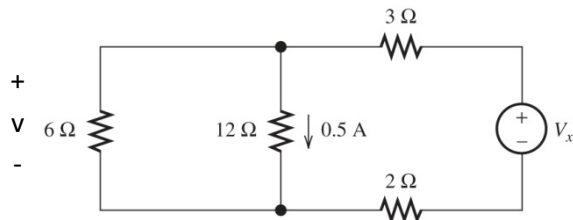


1. Consider the circuit shown below.
- Find  $V_x$ . (ans  $\sim 12\text{V}$ )
  - Find the total power absorbed by the resistors. (ans  $\sim 20\text{W}$ )




**Ohm's Law:**  $v = 0.5 \times 12 = 6 \text{ V}$

**Ohm's Law:** Current through the  $6 \Omega = 6/1 = 1\text{A}$

$v_s = 3 \Omega \times 1.5 \text{ A} + 6 \text{ V} + 2 \Omega \times 1.5 \text{ A} = 13.5 \text{ V}$

**Power**  $= i v_s = 1.5 \text{ A} \times 13.5 \text{ V} = 20.3 \text{ W}$

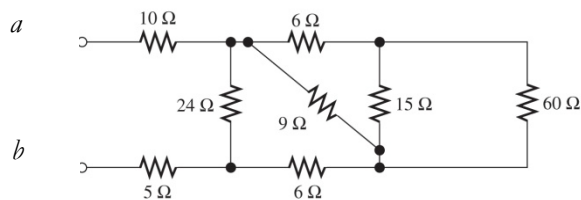2. Find the equivalent resistance between terminals  $a$  and  $b$  in both of the following circuits: (ans  $\sim 20\Omega$ ;  $10\Omega$ )



**Working from right  $\rightarrow$  left:**

$60 \parallel 15 = 12 \Omega$


$12 + 6 = 18 \Omega$

$18 \parallel 9 = 6 \Omega$

$6 + 6 = 12 \Omega$

$12 \parallel 24 = 8 \Omega$

$10 + 8 + 5 = 23 \Omega$

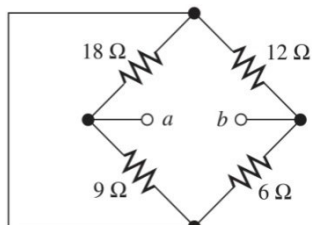


$12 \parallel 6 = 4 \Omega$

$18 \parallel 9 = 6 \Omega$

$4 + 6 = 10 \Omega$

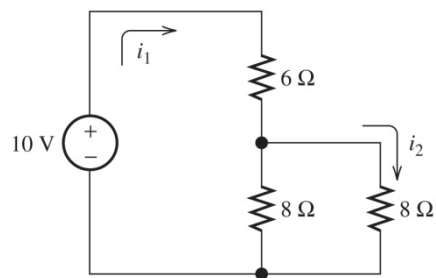3. Find  $i_1$  and  $i_2$  in the circuit below. (ans  $i_1 = 1\text{ A}$ )




$$8 \parallel 8 = 4 \Omega$$

$$6 + 4 = 10 \Omega$$

$$i_1 = 10 \text{ V} / 10 \Omega = 1 \text{ A}$$

$$i_2 = 4 \text{ V} / 8 \Omega = 0.5 \text{ A}$$

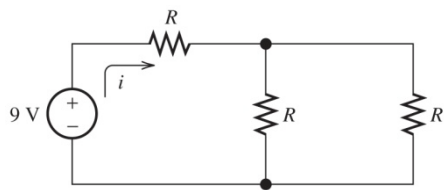4. The 9-V battery in the circuit below is delivering 2.43 W of power to three robot sensors represented by the resistors. All the sensors are identical with resistance  $R$ . Find the value of  $R$ . (ans:  $\sim 20\Omega$ )



$$R \parallel R = R/2$$

$$R + R/2 = 1.5R$$


$$i = 9 \text{ V} / 1.5R$$

$$p = 9 \text{ V} i = 81 \text{ V}^2 / 1.5R = 2.43 \text{ W}$$

$$R = 81 \text{ V}^2 / (1.5 \times 2.43 \text{ W}) = 22 \Omega$$

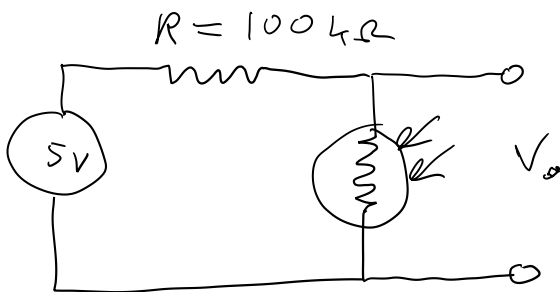5. You may want to review the class notes to solve this problem. A robot line-following sensor uses a photo resistor whose resistance changes from  $10\text{ k}\Omega$  (LIGHT) to  $250\text{ k}\Omega$  (DARK). Design an electronic circuit (with a  $5\text{ V}$  source for all circuits) such that the output voltage is  $0\text{ V}$  on WHITE and  $5\text{ V}$  on BLACK. For purposes of limiting the current in the photo resistor loop, you decide to use a  $100\text{ k}\Omega$  resistor in series with it. For similar current considerations, you pick a  $100\text{ k}\Omega$  variable resistor ("potentiometer") for the reference circuit. Clearly draw your complete circuit diagram (to include the photo resistor, the op amp, the reference voltage loop with  $100\text{ k}\Omega$  potentiometer, and the  $100\text{ k}\Omega$  series resistor). Specify and explain the reference voltage selected. (ans  $\sim 2\text{V}$ )

First find the voltage variation of the photo resistor.



$$\text{DK: } V_o = \left( \frac{250(\text{k}\Omega)}{250(\text{k}\Omega) + 100(\text{k}\Omega)} \right) 5\text{V} = 3.6(\text{V})$$

$$\text{LT: } V_o = \left( \frac{10(\text{k}\Omega)}{10(\text{k}\Omega) + 100(\text{k}\Omega)} \right) 5\text{V} = 0.5(\text{V})$$

Note that the average is  $\sim 2(\text{V})$

We want to choose a reference voltage that gives as much swing as possible between light and dark.

